

A  $2\mu\text{F}$  capacitor is charged to 12V and then connected across a resistor of  $100\Omega$ .

- (a) Determine the initial energy stored in the capacitor
- (b) Determine the energy stored in the capacitor after two time constants have elapsed