

Problem HH 1.26

Find the frequency response (V_{out}/V_{in} versus angular frequency ω) for the series LC trap circuit below.

