

Design a circuit to drive a speaker producing sound of frequency proportional to the intensity of white light.