

A 4-bit shift register is shifted six times to the right. If the initial content was 1101, find the content of the register after each shift if the serial input pattern is 101101.