

Draw logic circuits to simulate each of the Boolean expressions below.

(a) $F = A + \bar{B} \bullet C$

(b) $F = (A + B) \bullet \bar{C}$

(c) $F = \overline{A + B} \bullet \bar{A} \bullet \bar{B} + \overline{A \bullet B}$