



In the half-wave rectifier above, the input voltage is 10 V (rms) and $R_L = 30\Omega$. Find the peak output voltage for each of the V-I diode characteristics shown in the graph below.

