



Find the voltage V_d and current I_d for the diode in the circuit above. Assume a perfect diode.