



Plot V_o vs. V_i for the circuit above. Assume that the diode is perfect, the input voltage varies in the range $-10\text{V} < V_i < 10\text{V}$ and $R_1 = 10 R_2$.