

A doorbell is connected to a transformer whose primary contains 3000 turns and which is connected to 120V AC. If the doorbell requires 0.2A at 10V, find the number of turns necessary for the secondary winding and the current that flows in the primary.