



Resistor  $R_L$  is connected to the circuit shown at terminals a and b.

- (a) Find the value  $R_L$  for maximum power delivery to  $R_L$ .
- (b) What is the maximum power? What is the power delivered to  $R_L$  when  $R_L = 10\Omega$ .