

### **Problem HH 1.27**

Design a full-wave bridge rectifier circuit to deliver 10 volts dc with less than 0.1 volt (pp) ripple into a load drawing up to 10 mA. Choose the appropriate ac input voltage (by means of a transformer) assuming 0.6 volt diode drops. Be sure to use the correct ripple frequency in your calculation.