

Problem T10

Using logic gates, show how to make a two-input multiplexer. The truth table for your circuit should be:

A	Out
0	D_0
1	D_1