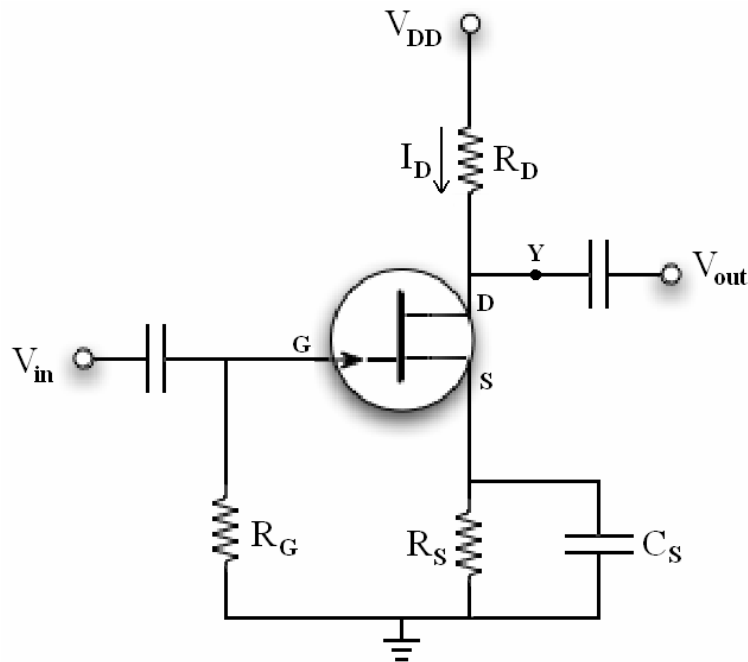


Problem T4

Consider the following common source JFET amplifier circuit. Assume that $V_{DD} = 10\text{ V}$ and that the average value of I_D is 4.0 mA . Moreover, assume that the voltage difference between the gate and source is $V_{GS} = -1.5\text{ V}$ and that the transconductance under these conditions is $g_m = 1.5\text{ mhos}$.



- Calculate the value of R_D that will result in gain of $|\Delta V_D / \Delta V_G| = 500$.
- Assume that R_G is sufficiently small so that the average voltage at the gate is approximately zero. Find the value of R_S necessary to give $V_{GS} = -1.5\text{ V}$.
- Calculate an appropriate value for C_S if the minimum operating frequency is 100 Hz .
- Given your values of R_D and R_S , what is the average voltage at point Y.
- Assume that the input and output capacitors are sufficiently large to pass 100% of the AC signal at $\omega = 1000\text{ radians/s}$. Given that $V_{in} = 0.002 \cos \omega t$, plot V_{out} and I_D as a function of time t (using your values of R_D and R_S).