

**DH12.3** Analyze operation of the shown flip-flop circuit and identify which sets of gates play the role of master and which the role of slave. Note: The enabling conditions for standard operation are  $SET = RESET = 1$ . The overriding conditions of  $SET = RESET = 0$  yield  $Q = 1$ .

