

DH1.5 Compute the current through R_3 in the circuit below.

