

DH2.6 A designer wishes to replace the circuit shown below with an RC circuit that exhibits the same voltage V_{out} vs. time characteristics, when V_{in} is changed abruptly between two constant values. Design an acceptable RC circuit.

