

DH3.11 In the shown circuit the component values are $C = 2.0 \mu\text{F}$, $R = 1.0 \text{k}\Omega$ and $L = 1.0 \text{H}$. Determine the resonance frequency in Hz.

