

DH3.8 In the shown circuit, the component values are $R = 10\text{ k}\Omega$ and $C = 0.20\ \mu\text{F}$. Plot the ratio V_o/V_i as a function of driving frequency f . Also plot the logarithm of V_o/V_i vs the logarithm of f .

