

Sketch the output waveforms expected when a 100Hz sine wave ( $V_p=5V$ ) is applied to each of the following circuits:

