

The circuit below shows a four-bit Digital to Analog Converter (DAC) using an R-2R network. Find the output current, I , in terms of V_{ref} , R and R_f when the inputs are 0101, as shown.

