

**P5.20** (a) Find the equivalent resistance of the circuit below. (b) Suppose a 25 V battery is connected across the terminals. Calculate the current in the 10  $\Omega$  resistor.

