

Sketch a graph of V_{out}^+ vs. V_{in} and V_{out}^- vs. V_{in} for the circuit shown in Figure 1. $R_1=10k$, $R=27k$, A_1 is the 347 op-amp, diode=1N4148.

