

Problem T13

Using logic gates, show how to make a two-input multiplexer. The truth table for your circuit should be:

| A | Out |
|---|----------------|
| 0 | D ₀ |
| 1 | D ₁ |