

**DH1.3** What is the maximum allowable current through a  $10\text{ k}\Omega$ ,  $10\text{ W}$  resistor? Through a  $10\text{ k}\Omega$ ,  $1/4\text{ W}$  resistor?