

**DH1.6** Compute the currents through  $R_1$  and  $R_2$  in the circuit below.

