

DH2.1 Calculate the effective capacitance of the circuit below.

