

DH2.2 Calculate the effective capacitance of the circuit below.

