

T2:

Complete the following table:

	Resistor	Capacitor	Inductor
General v-i relationship			$v = L \frac{di}{dt}$
DC v-I relationship		I=0	
Phasor v-i relationship		$v = i \frac{1}{j\omega C}$	