

**DH12.9** Determine the truth table and modulus for the synchronous counter displayed in the figure. Assume  $J = K = 1$  for the first FF. Start the table with  $Q_A = Q_B = Q_C = Q_D = 0$ . How is such a counter called?

