

P3.20 Draw a flip-flop circuit out of a couple of NOR gates and explain its operation.