

**DH11.16** Using logic gates, design an alarm system which lights an LED when any of 5 doors is open.