

DH5.3 In the shown circuit, what would happen if the load resistor were shortened? What would happen if the load resistor were removed? *Hint: Think in terms of power ratings.*

