

TI - 40400 Standard Control Loop Setup

TI Example Design

V_{in} = 12 Volts
 V_{out} = 1.2 Volts
 Max Output = 20 Amps

Inductor = 0.75 μ H

$R1$ = 10k Ohm
 $R2$ = 10k Ohm
 $C1$ = 820 pFd
 $R3$ = 2.74k Ohm
 $C3$ = 680 pFd
 $C2$ = 2.2 nFd
 $R4$ = 4.99k Ohm

$$V_{out} = V_{ref} \times \frac{R1 + R2}{R2}$$

$$R2 = R1 \times \frac{V_{ref}}{V_{out} - V_{ref}}$$

TI Datasheet Pin Names & Reference Designators

- TPS40400 Chip Pin

