

LArTPC Electronics Meeting

Current Work at MSU

http://www.pa.msu.edu/~edmunds/LArTPC/Talks/Talk_Feb_2010/


History of the MSU LArTPC Electronics Work

- Built a small warm DAQ system for the Bo LArTPC
- Built a warm DAQ system with cold Bias Voltage distribution for the ArgoNeuT LArTPC
- About one year ago Stephen Pordes ask us to work on a small multiplexed readout DAQ system that would operate cold in LArTPC test cryostats

Motivation and Goals of Our Current Work

- Test this DAQ system in the Bo LArTPC
- Provide a DAQ system for the “no pump out” long drift LAPD LArTPC at Fermi
- Gain experience with multiplexed readout and cold electronics in a LArTPC DAQ system
- Gain experience with digital signals inside the LArTPC cryostat
- Work on ideas to reduce the cost of the DAQ system for a big detector (3 box to 2 box system)


3 Box LArTPC DAQ System

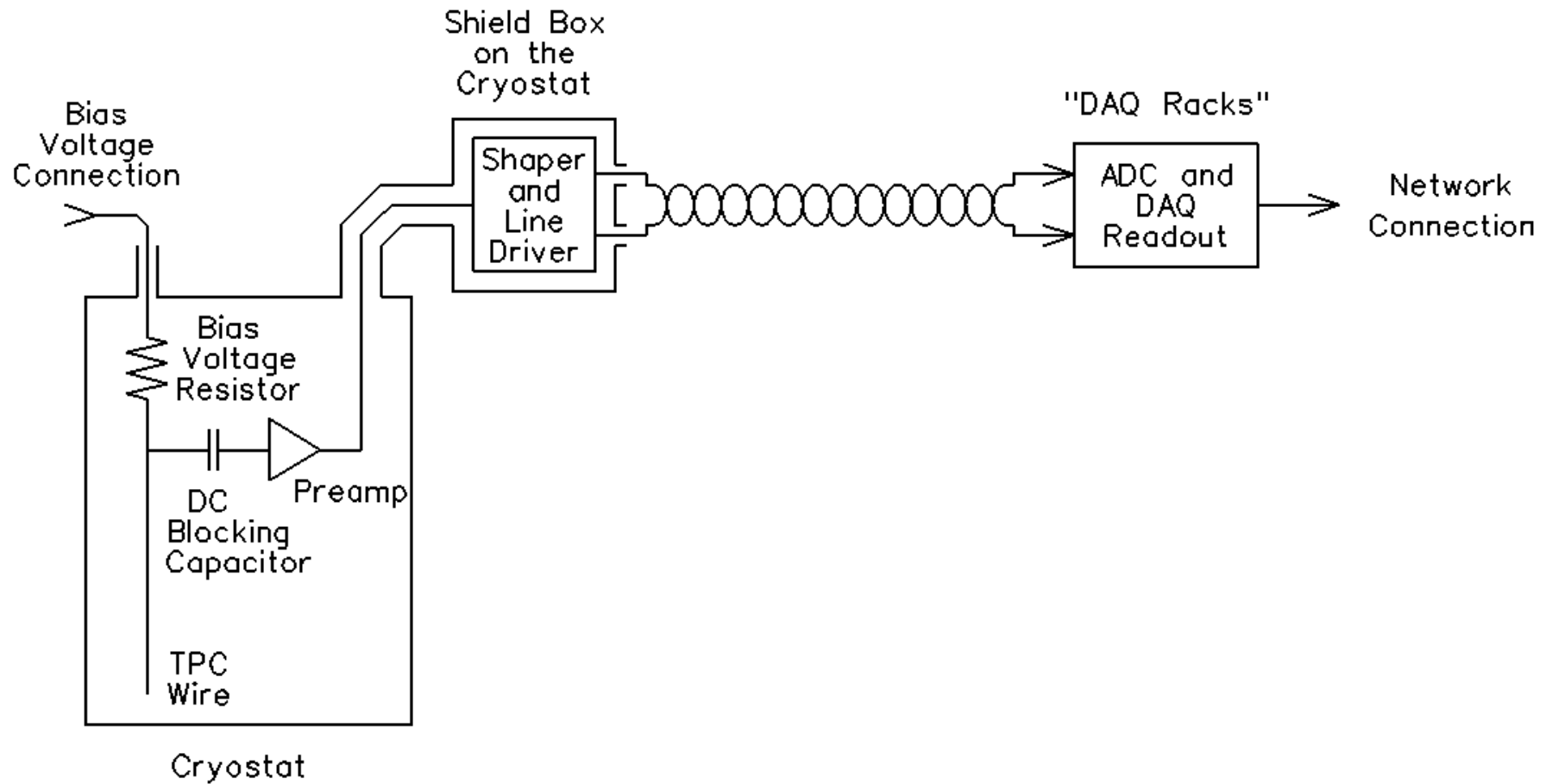

Project Sections of our Current Work:

1. Characterize components at LN2 temperature
2. Inside the cryostat
 - Preamplifier
 - Filter
 - Multiplexer
 - Line Driver
 - Digital Control of the Multiplexer
3. At the Cryostat Feedthrough
 - Passive Noise Filters: power supply, analog common mode, digital control signal coupling transformers
4. In the DAQ Rack
 - Back of the backplane card: power supply regulators, analog signal receivers, digital control signal drivers
 - Firmware for the ADF-2 VME Readout Card
5. DAQ system software

2 Box LArTPC DAQ System

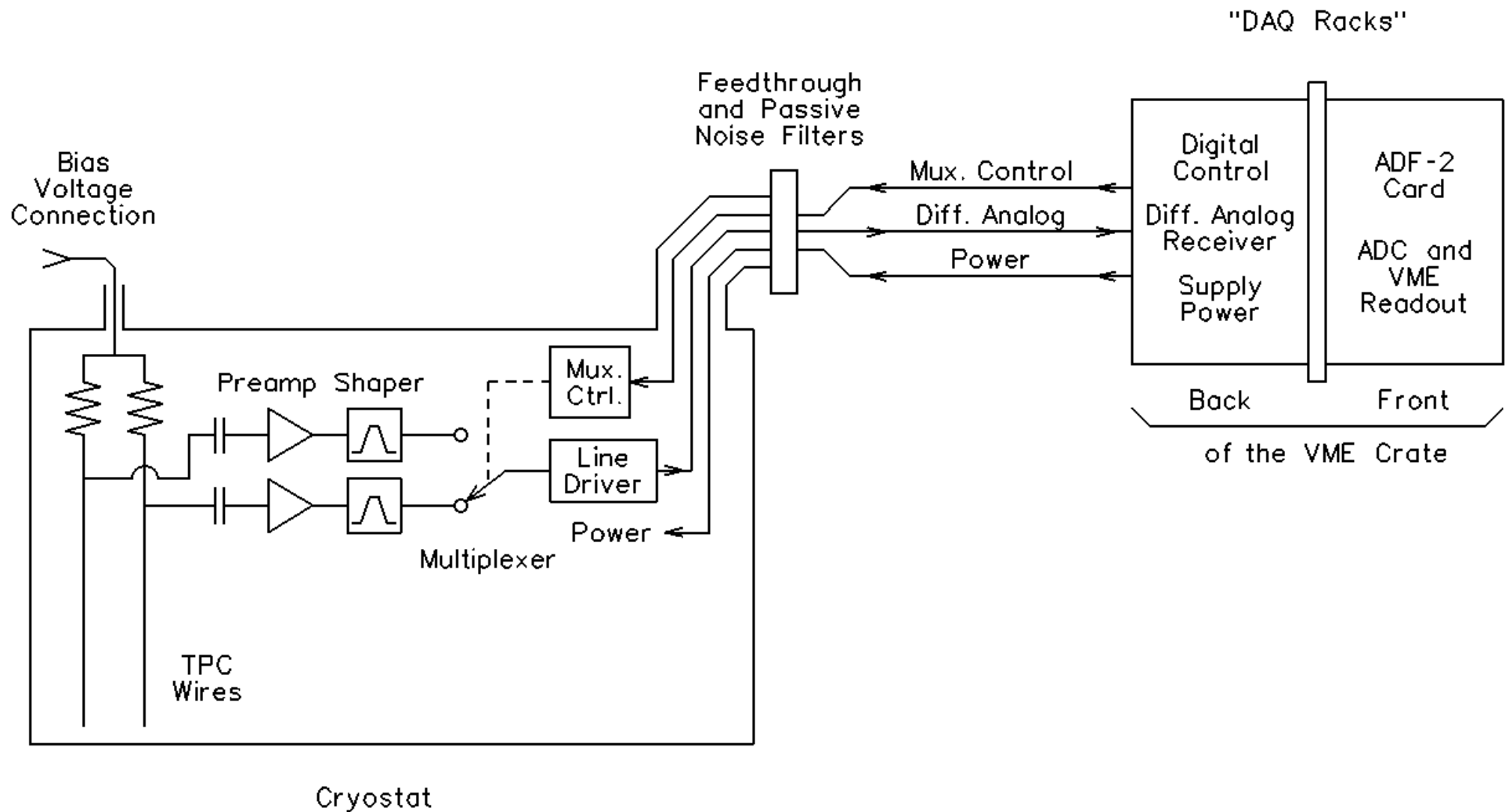


Design Considerations:


- Operate at RT or LN2 temperature without significant adjustment
- Per readout card have a single twist-flat cable running inside:
 - 4 differential analog signals
 - 2 differential digital control signals
 - 3 power supplies (6 conductors)
 - 8 grounds (16 conductors)
 - 50 – 100 mV signal levels
- Control electrical noise inside the cryostat

Cold MOSFET Preamplifier

- | | |
|-------------------------|------------------------|
| R1 = 100M Ohm | C1 = 1.8 pFd |
| R2 = 375 Ohm | C2 = 10 nFd |
| R3 = 18.6k Ohm | C3 = 10 nFd |
| R4 = 100k Ohm | C4 = 47 nFd |
| R5 = 27k Ohm | C5 = 47 nFd |
| R6 = 1.0k Ohm | C6 = 47 nFd |
| R7 = 2.0k Ohm | C7 = 47 nFd |
| R8 = 100 Ohm | C8 = 47 nFd |
| R9 = 100 Ohm | C9 = 47 nFd on CMB-16 |
| R10 = 100 Ohm | C10 = 47 nFd on CMB-16 |
| R11 = 100 Ohm on CMB-16 | |
| R12 = 10 Ohm on CMB-16 | |

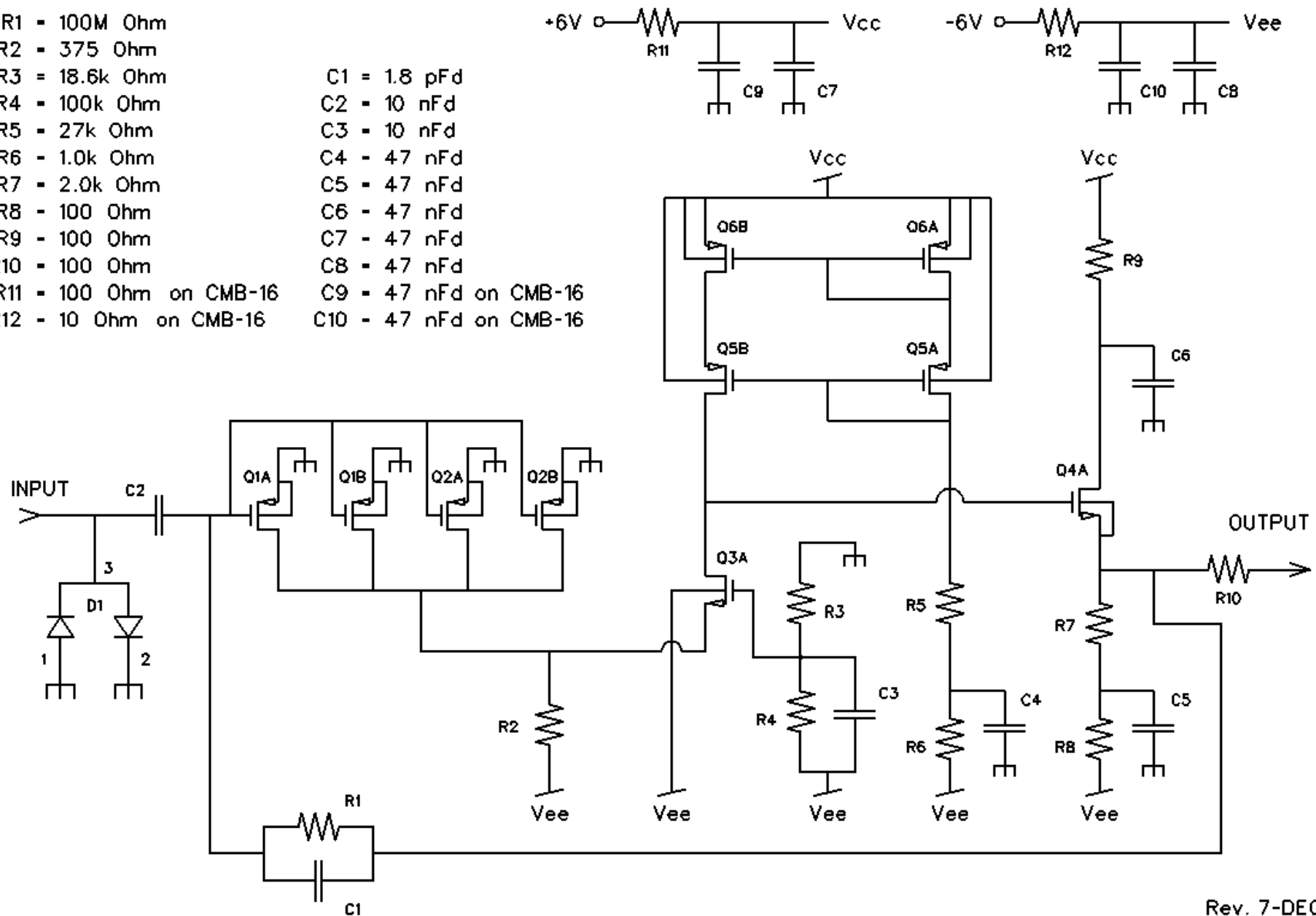

Cold 3-Pole Filter

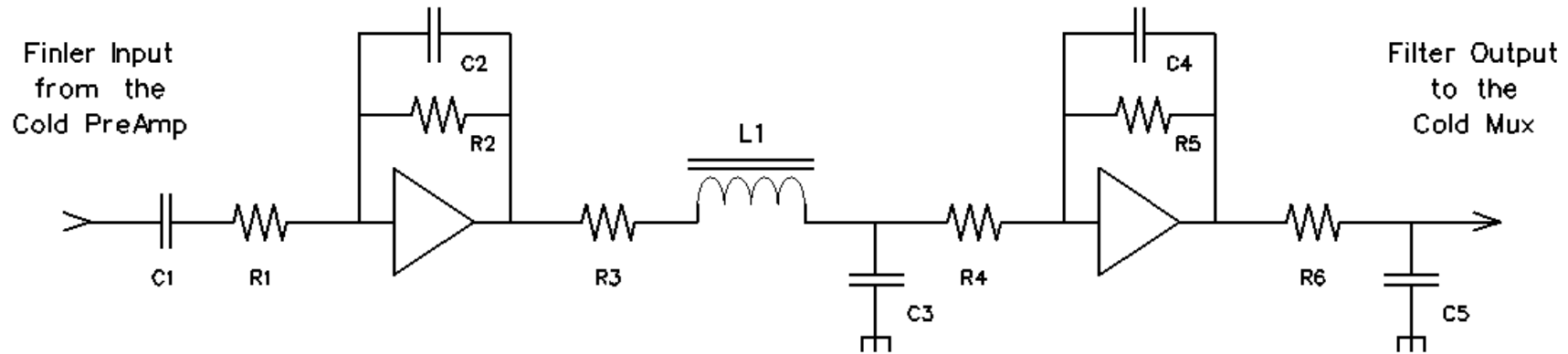

The Drift Velocity is 1.5 mm/usec in a 500 V/cm field.
 For a 3 to 5 mm plane spacing the risetime will be 2 to 3.3 usec.
 For now pick a 2.5 usec peaking time or about 64 kHz.

R1C1 Tau 1.64 usec
 R1 - 2k Ohm
 C1 - 820 pFd

R2C2 Tau 560 nsec
 R2 - 10k Ohm
 C2 - 56 pFd

R3 - 845 Ohm
 L1 - 560 uH
 C3 - 2.2 nFd
 R4 - 10k Ohm

R5C4 Tau 500 nsec
 R5 - 49.9k Ohm
 C4 - 10 pFd

R6C5 Tau 110 nsec
 R6 - 499 Ohm
 C5 - 220 pFd

See the Cold
 Mux Circuit

$$R2/R1 = 5.0$$

$$1/\text{SQRT}(L1 C3) = 901\text{k}$$


$$R5/R4 = 5.0$$

$$R3/(2 \times L1) = 754\text{k}$$


$\omega_0 > \nu \rightarrow$ underdamped

Cold 3-Pole Filter

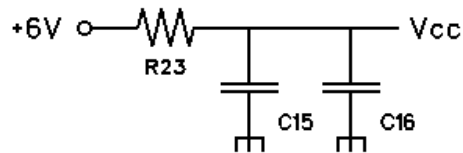R13 = 6.8k Ohm
 R14 = 800 Ohm
 R15 = 6.8k Ohm
 R16 = 800 Ohm



C15 = 47 nFd
 C16 = 47 nFd

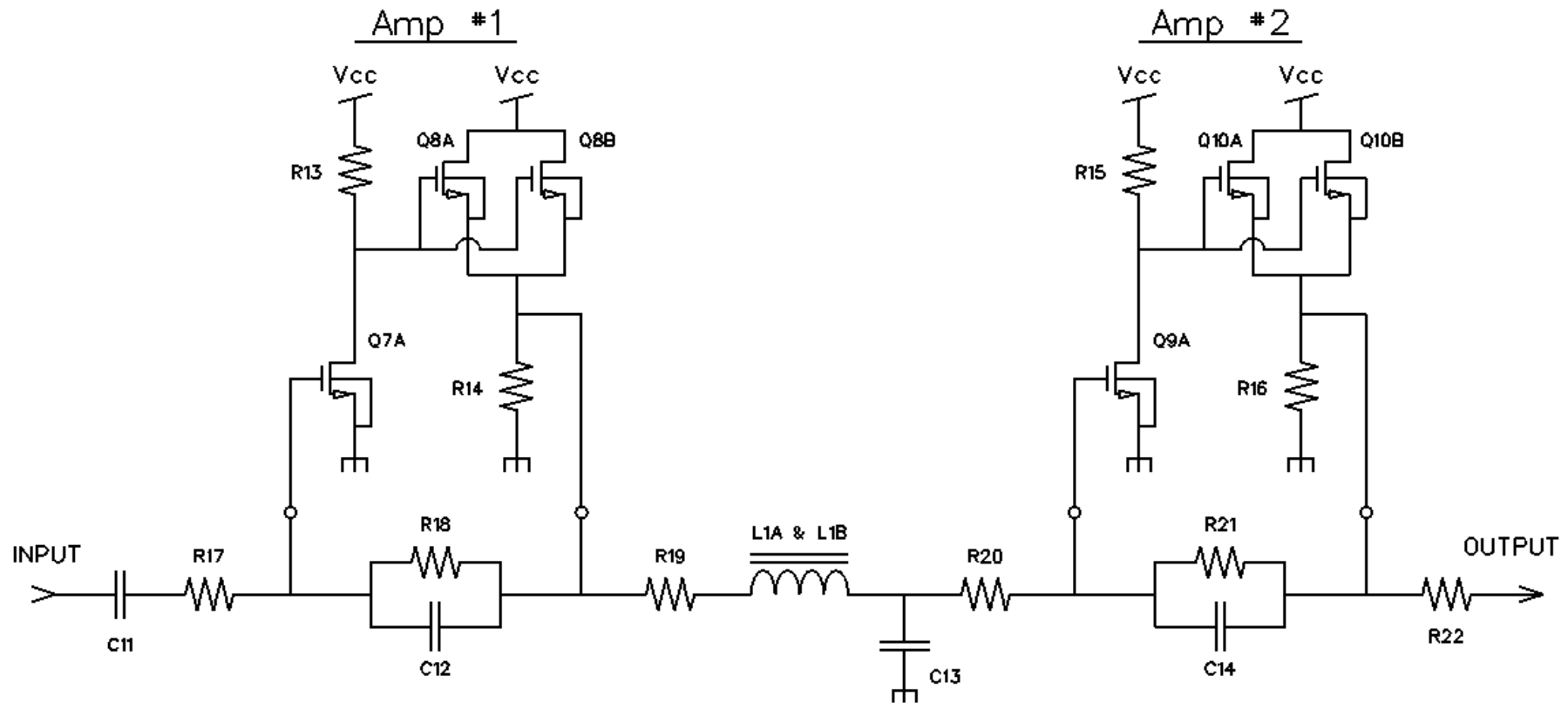

R17C11 1.64 usec
 R17 = 2k Ohm
 C11 = 820 pFd

R18C12 560 nsec
 R18 = 10k Ohm
 C12 = 56 pFd


R19 = 845 Ohm
 L1 = 560 uH
 C13 = 2.2 nFd
 R20 = 10k Ohm

R21C14 500 nsec
 R21 = 49.9k Ohm
 C14 = 10 pFd


R22 = 100 Ohm

Rev. 15-DEC-09


Filter Step Response

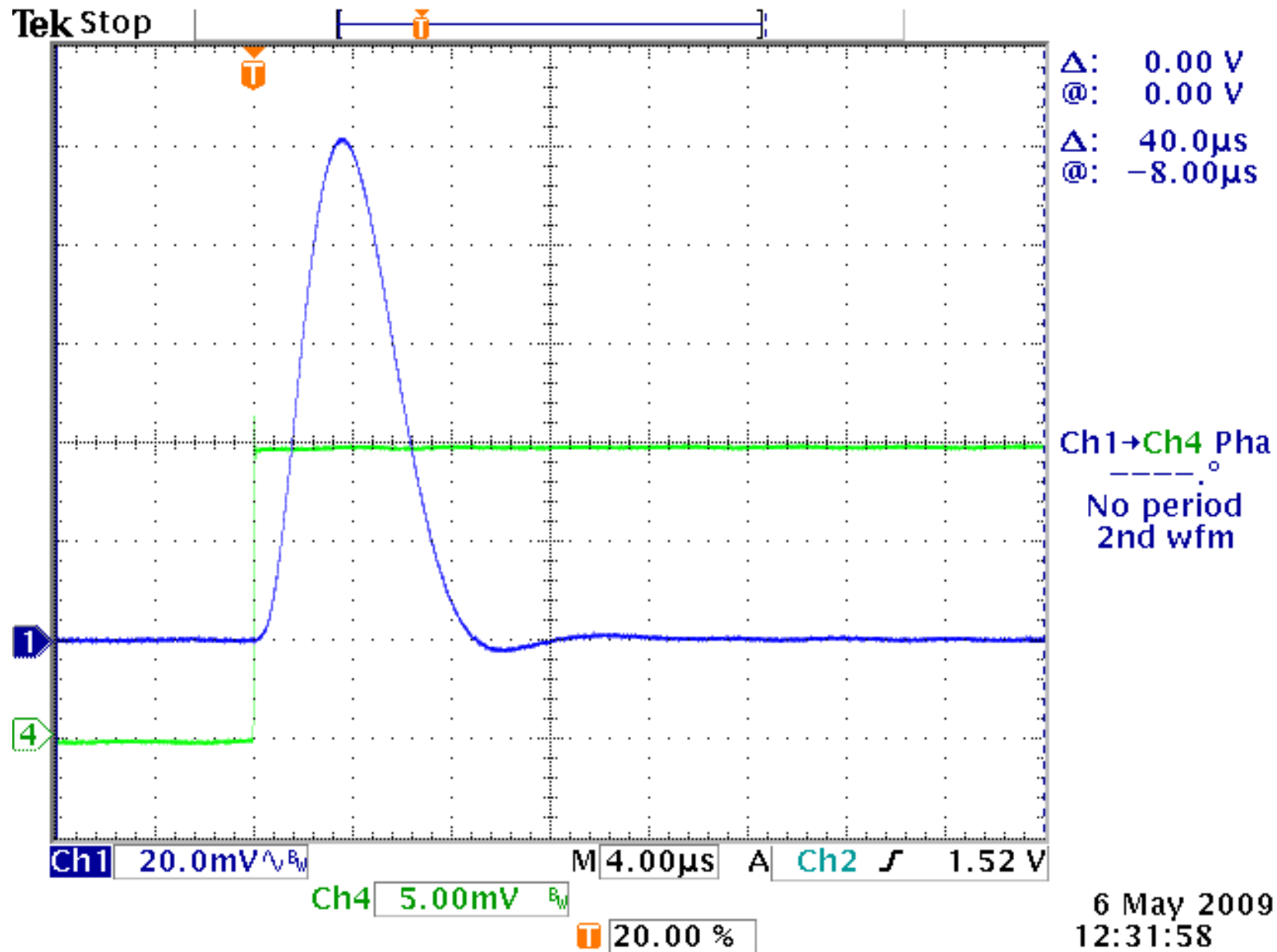

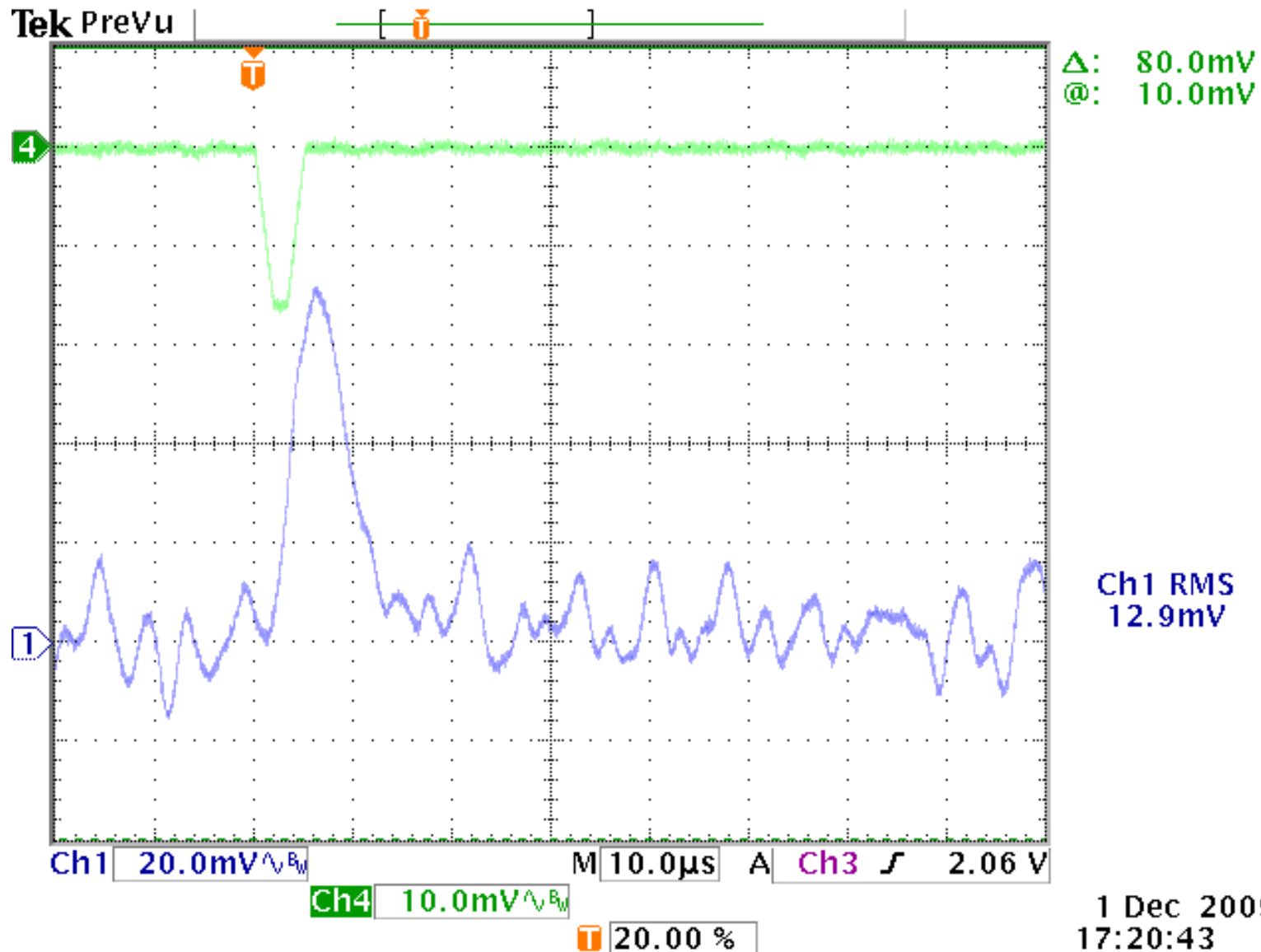
Collection Plane Signal Preampl and Filter




Cold Analog Multiplexer

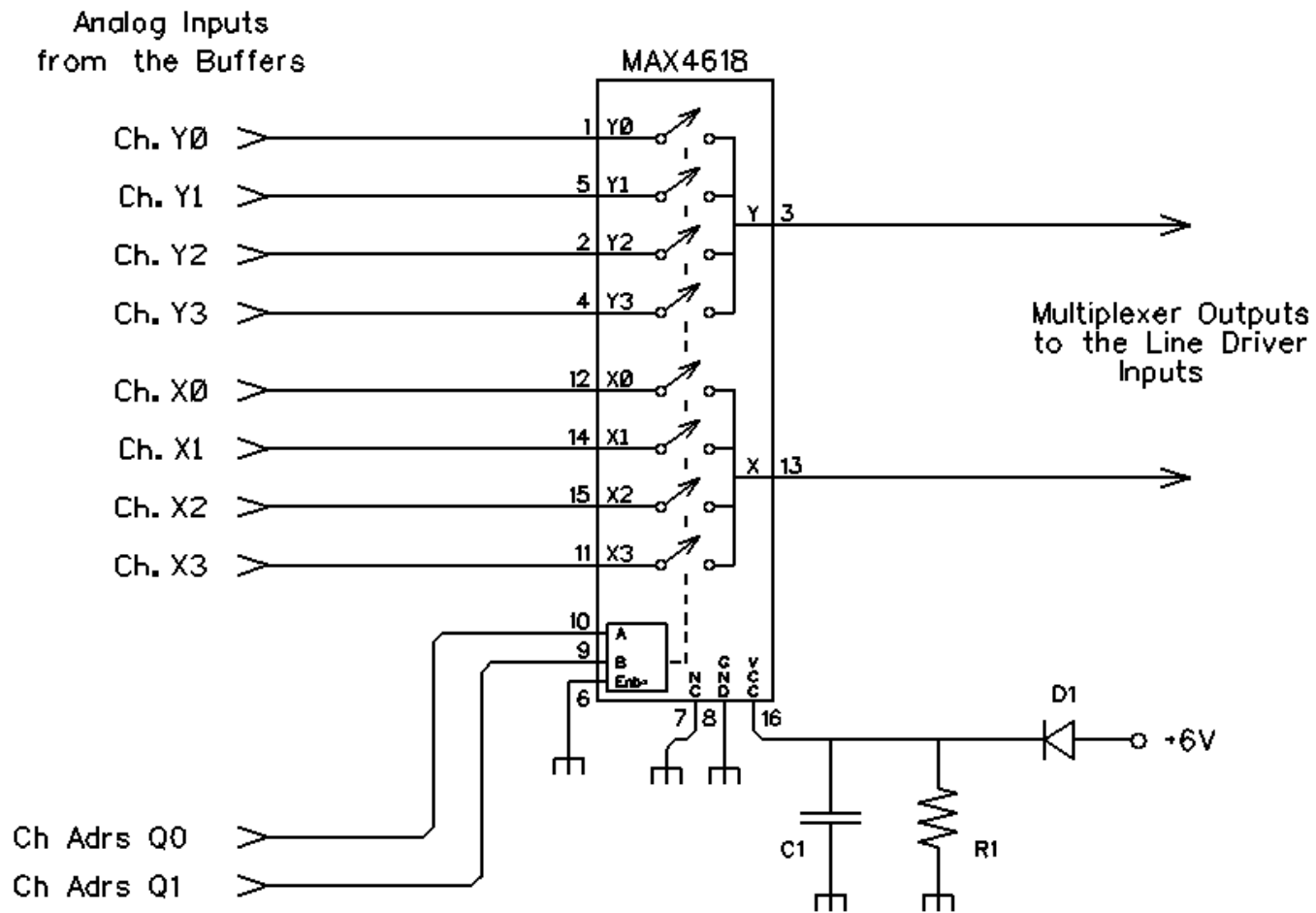


Cold MOSFET Line Driver

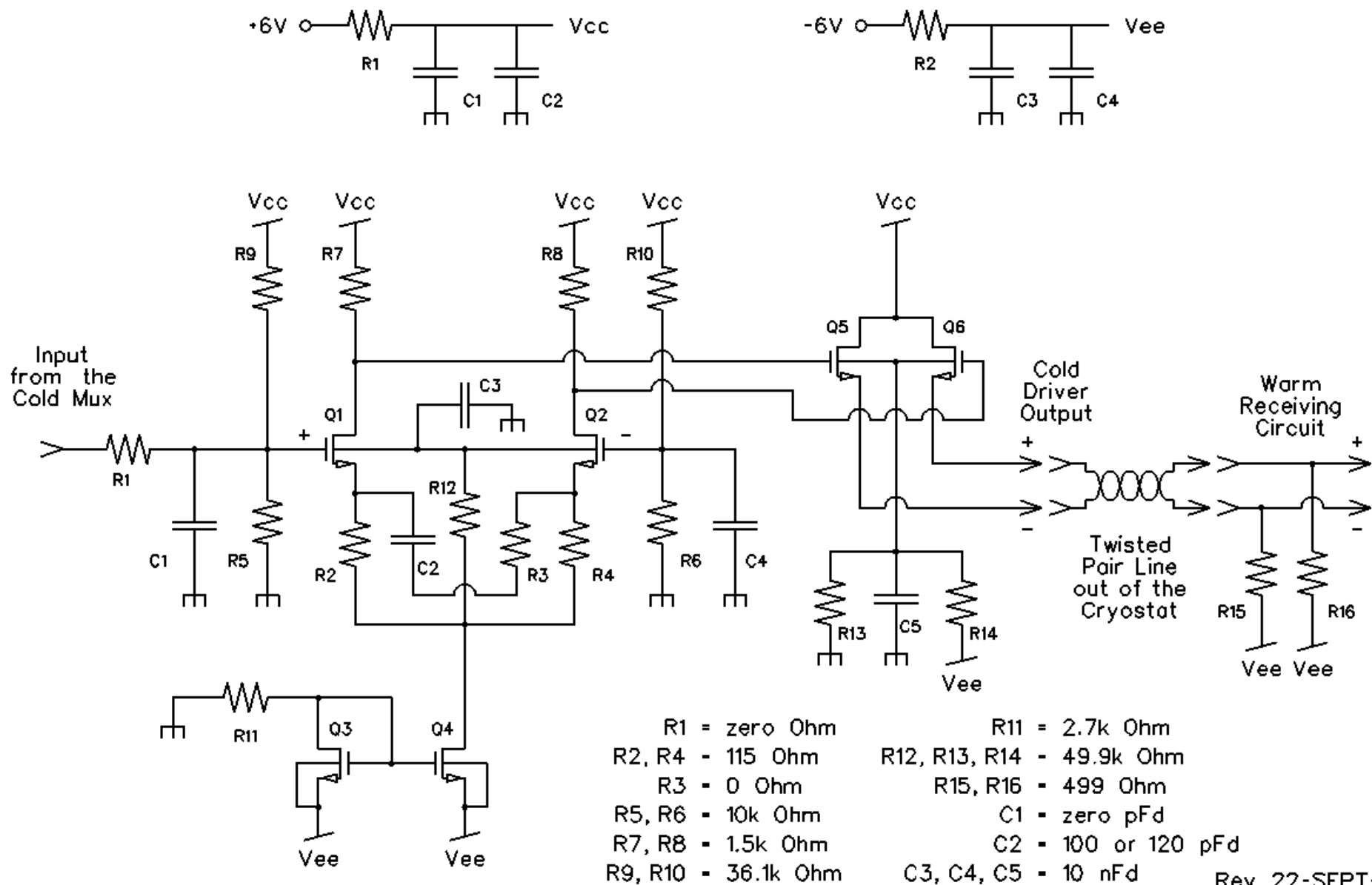


Line Driver and Cable Response

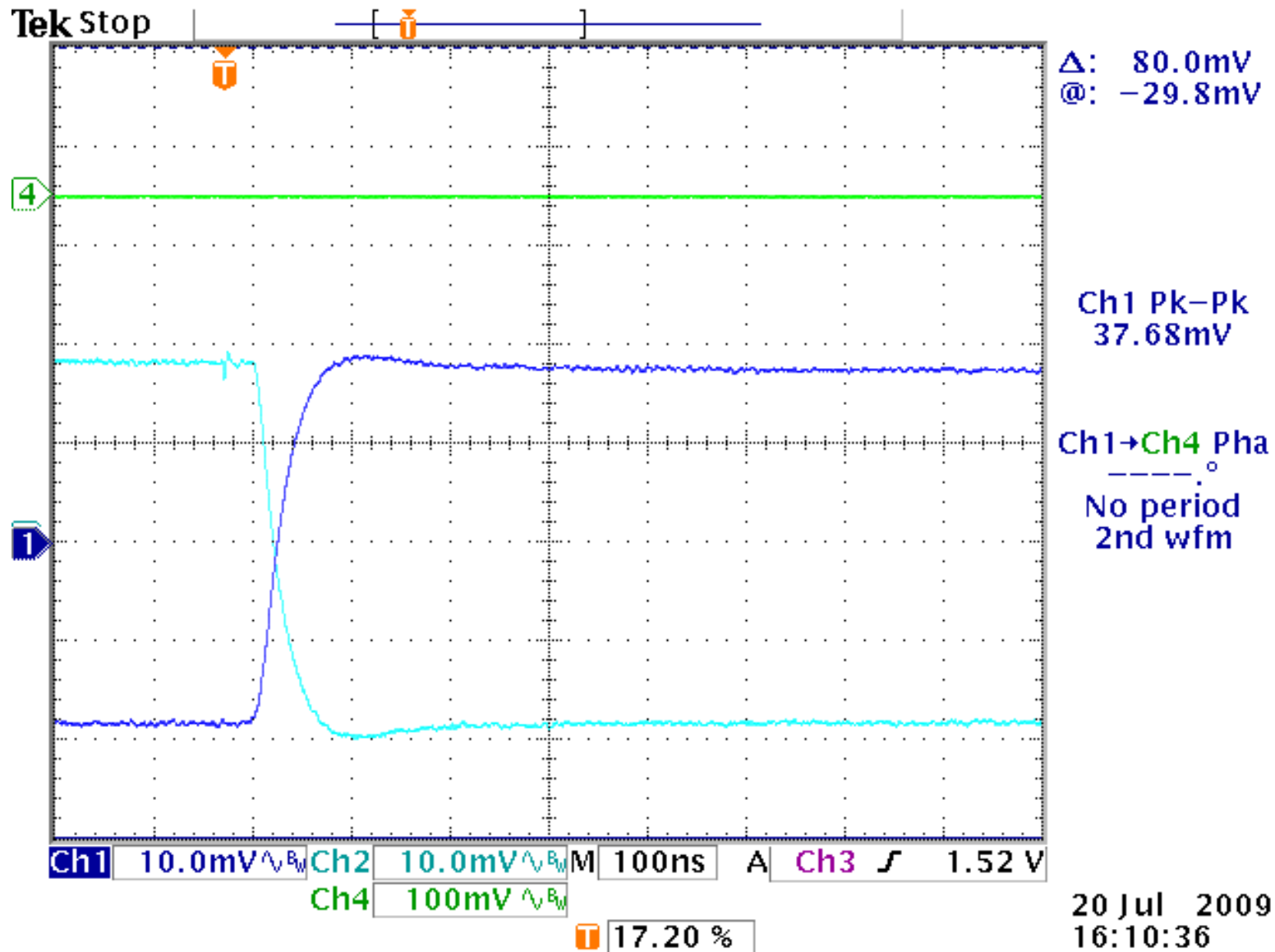


Cold Digital Control Signal Receiver

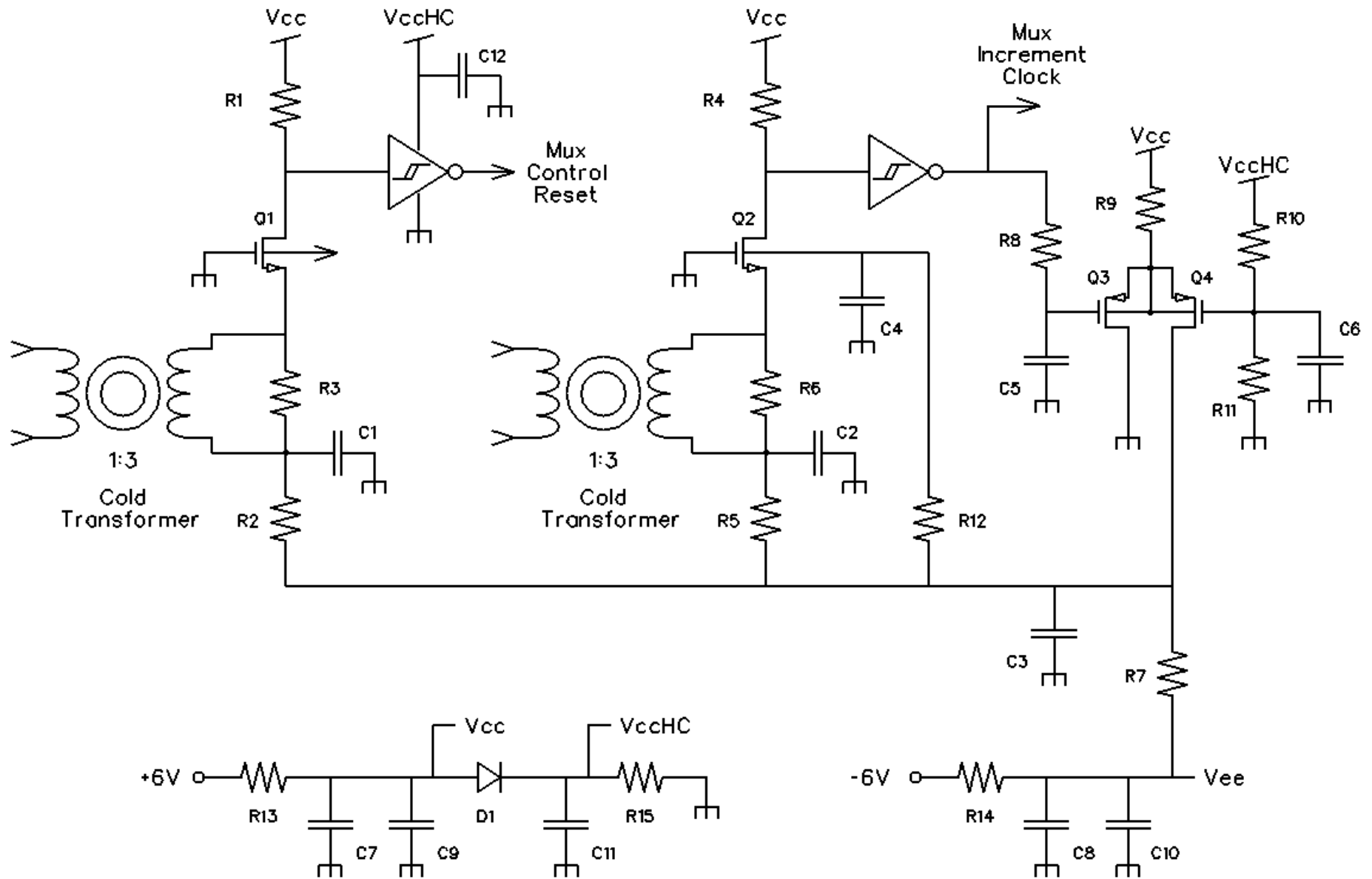

Cold Multiplexer Digital Control

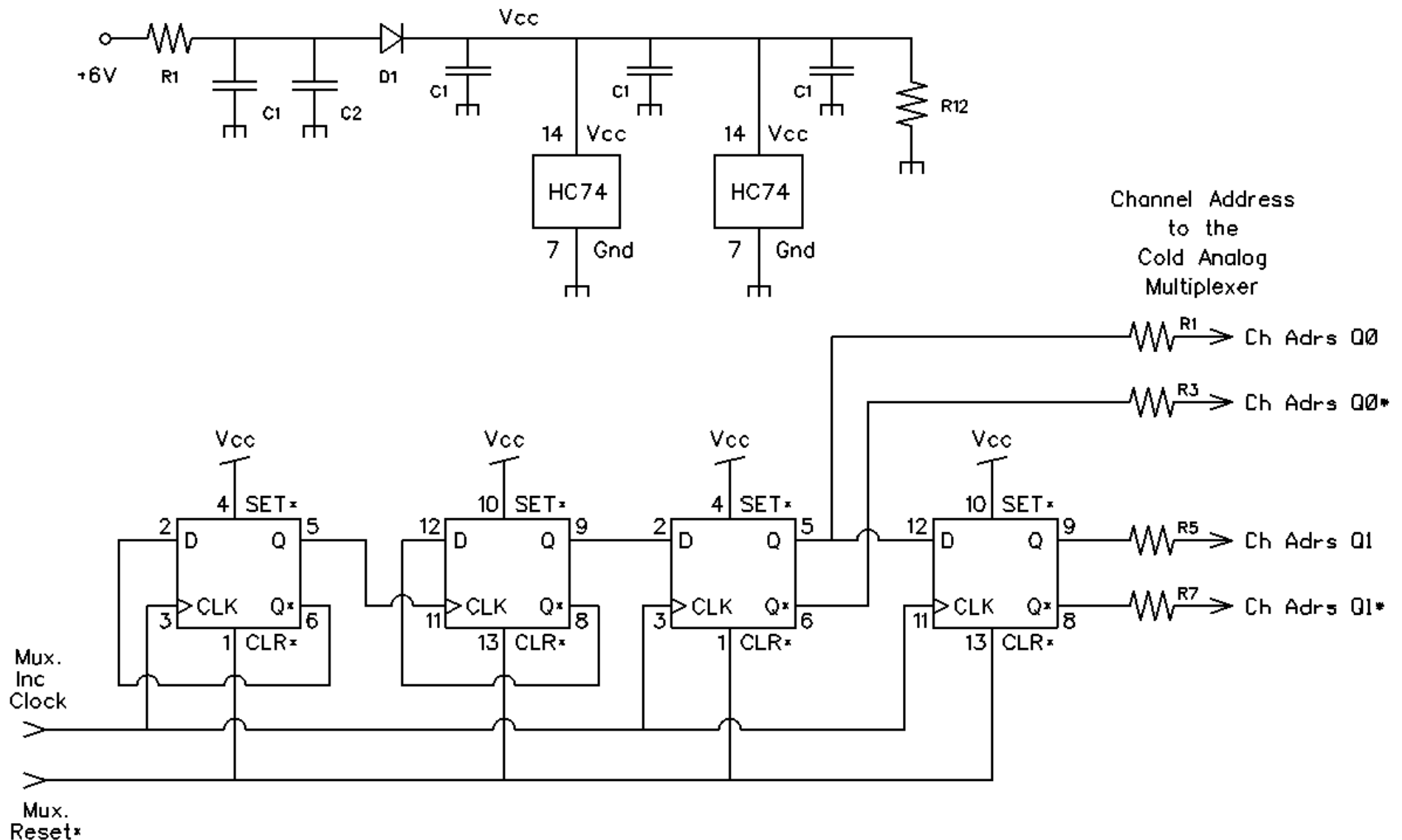


Warm Digital Control Signal Driver

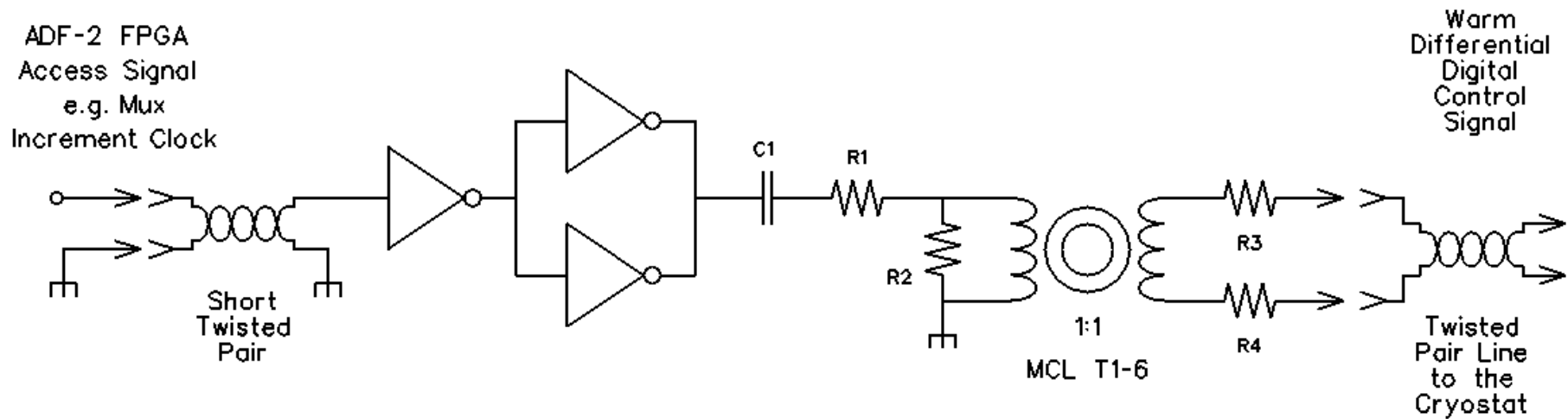


R1 - 412 Ohm
R2 - 51 Ohm
R3, R4 - 25 Ohm
C1 - 10 nFd

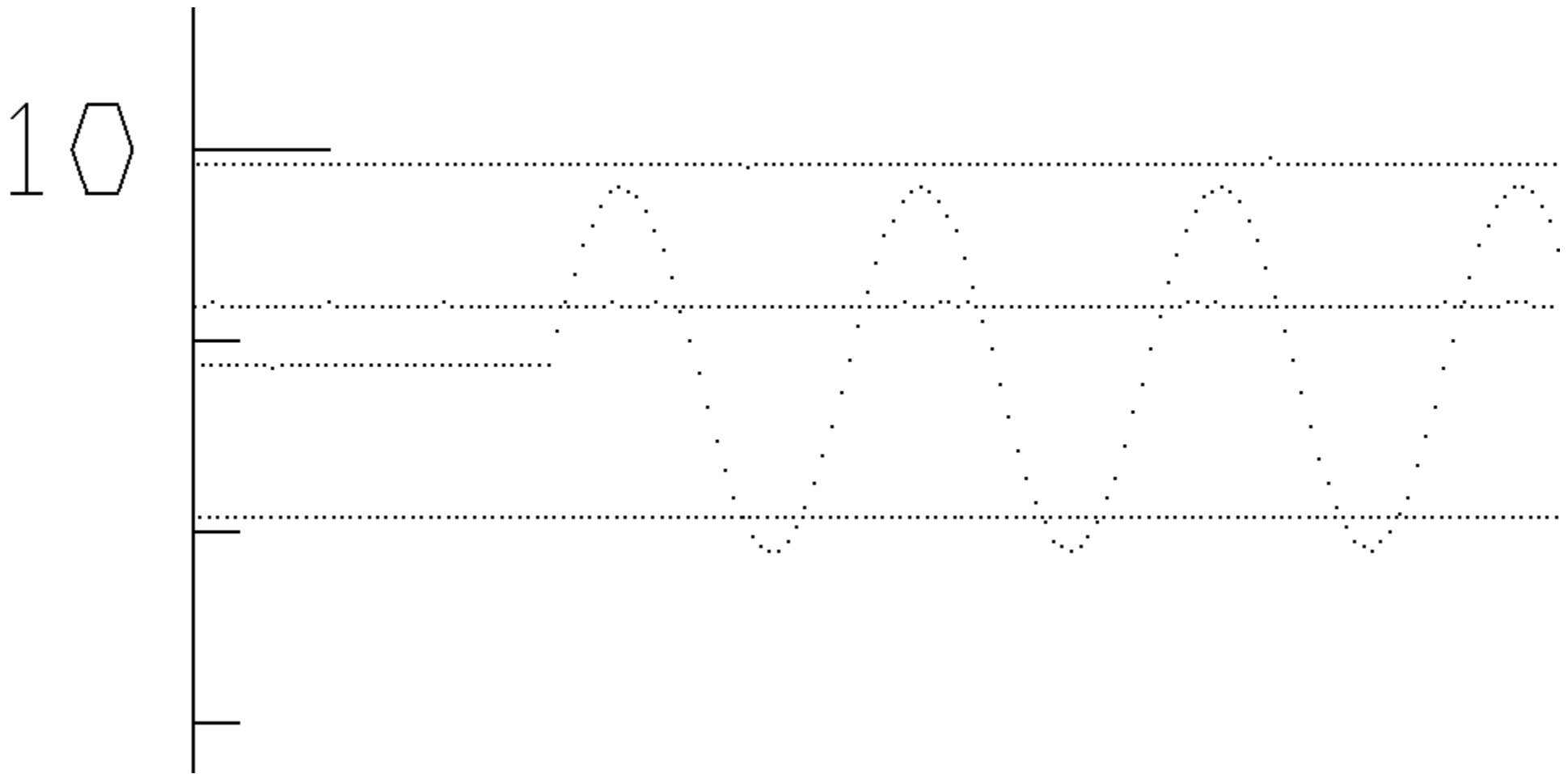Output from the Chain: Buffer, Multiplexer, Line Driver, Cable, and VME ADF-2 (ADC) Card Checking for Crosstalk




2 Channel Preamp-Filter Card

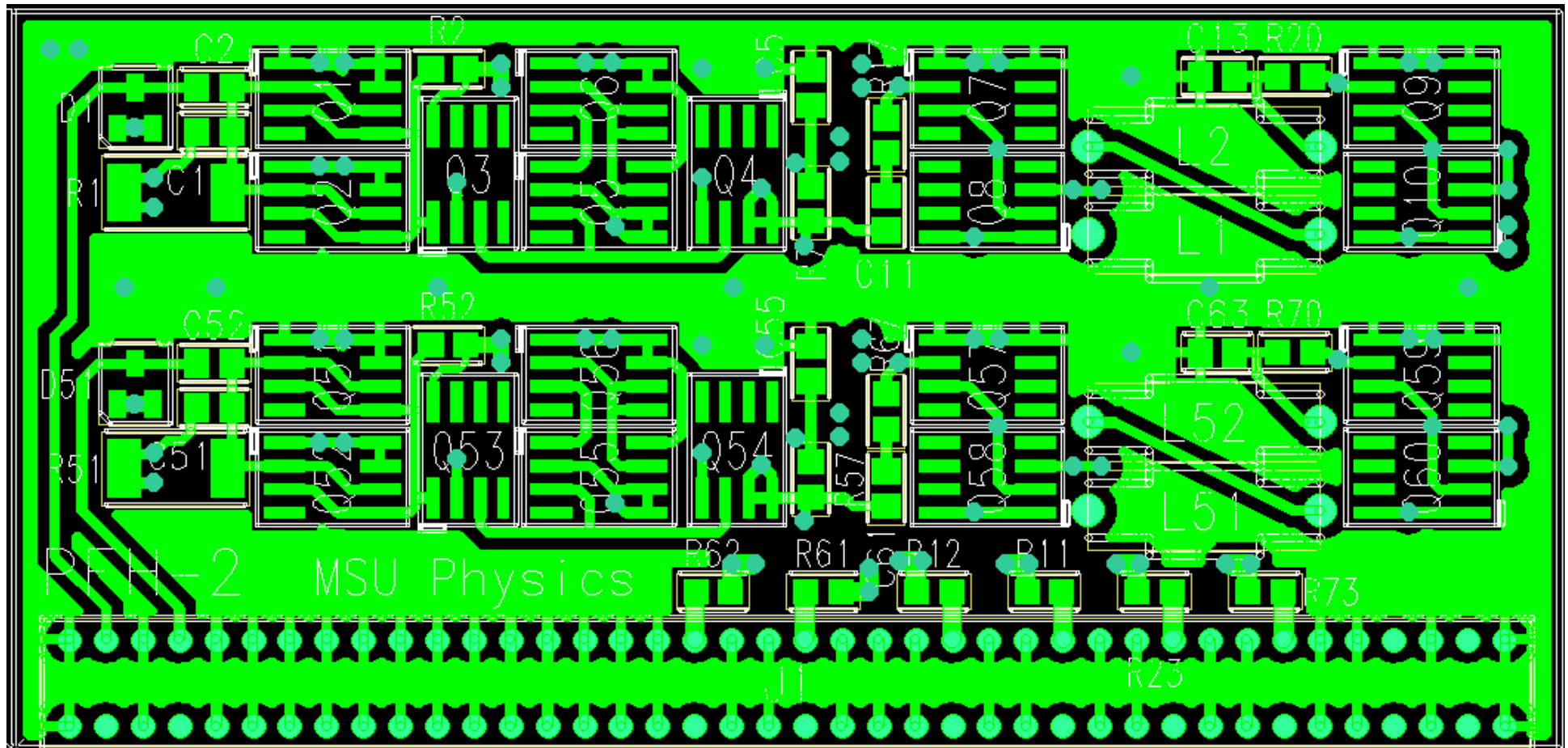- 4 layer with ground fill on all layers
- double via connections
- relieved ground plane under Hi Z traces
- compromise between size and ease of modification



16 Channel Mother Board

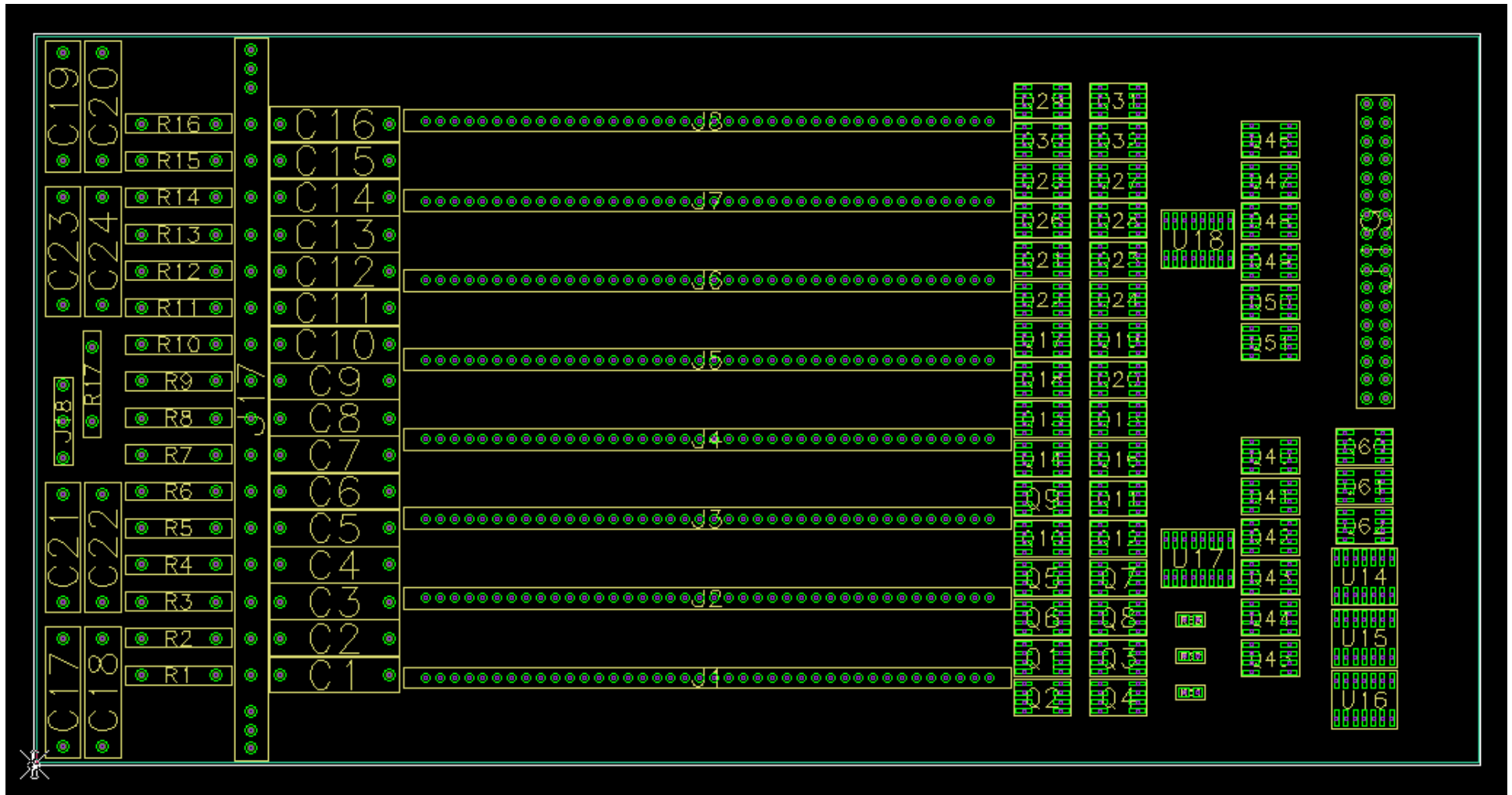

Engineering Comments:

If Fermi is going to be involved with the DAQ system for a large LArTPC detector (e.g. LBNE) then the electrical engineering work for that system should start soon.

- Technical Challenges
- Cost Control
- Remote Assembly and Operation

DAQ system engineering needs to be integrated with the mechanical and cryogenic engineering.

We should “prove” that a fully thought out warm electronics system will not work before committing to put “all” of the electronics inside.

As far as I know the HEP community has no examples of a large system operating for 10 or 20 years without needing to work on its electronics.

This is a one detector experiment, i.e. it must work.

A thin wall stainless steel vessel will not shield electrical noise. There is no “ground” inside and there is no shield inside.

Need a respected “Noise Czar” early (e.g. now).

Lots of room for DAQ design work:

- Filtering of the hit data
 - Inline Digital and Offline
 - Slope dependent hit filtering
 - Raw data beauty vs information content
- Data Compression: Coding, ROI Readout
- Triggering: Beam Spill vs Continuously Alive

Low Temperature Components:

- Some just don't work.
- Subtle problems.
- Circuit implications.

Backup

2 Box LArTPC DAQ System

