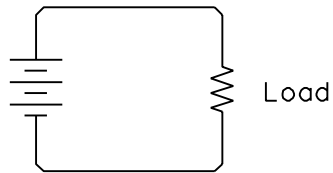



# Voltage Source vs Current Source

Voltage  
Source



The Voltage Source forces a fixed Voltage across the Load independent of the Resistance of the Load.

Current  
Source

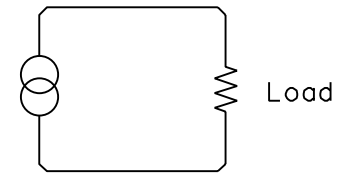

The Current Source forces a fixed Current through the Load independent of the Resistance of the Load.