

# PHY294H

---

- Professor: Joey Huston
- email: [huston@msu.edu](mailto:huston@msu.edu)
- office: BPS3230
- Homework will be with Mastering Physics (and an average of 1 hand-written problem per week)
  - ◆ **Help-room hours: 12:40-2:40 Tues; 3:00-4:00 PM Friday**
- Quizzes by iclicker (sometimes hand-written)
- Average on exam is around 65; will pass back tomorrow
- Course website: [www.pa.msu.edu/~huston/phy294h/index.html](http://www.pa.msu.edu/~huston/phy294h/index.html)
  - ◆ lectures will be posted frequently, mostly every day if I can remember to do so

# Conductivity and resistivity

**TABLE 30.2** Resistivity and conductivity of conducting materials

Material	Resistivity ( $\Omega \text{ m}$ )	Conductivity ( $\Omega^{-1} \text{ m}^{-1}$ )
Aluminum	$2.8 \times 10^{-8}$	$3.5 \times 10^7$
Copper	$1.7 \times 10^{-8}$	$6.0 \times 10^7$
Gold	$2.4 \times 10^{-8}$	$4.1 \times 10^7$
Iron	$9.7 \times 10^{-8}$	$1.0 \times 10^7$
Silver	$1.6 \times 10^{-8}$	$6.2 \times 10^7$
Tungsten	$5.6 \times 10^{-8}$	$1.8 \times 10^7$
Nichrome*	$1.5 \times 10^{-6}$	$6.7 \times 10^5$
Carbon	$3.5 \times 10^{-5}$	$2.9 \times 10^4$

\*Nickel-chromium alloy used for heating wires.


# Temperature dependence of resistivity

- Before we just quoted a value of resistivity for each material
- However, the resistivity has a temperature dependence, with most materials obeying the formula

$$\rho = \rho_0 [1 + \alpha(T - T_0)]$$

- ...where  $\rho_0$  is the resistivity at  $T_0$  (room temperature), and  $\alpha$  is the temperature coefficient.
- Note that  $\alpha$  is positive, i.e. the resistivity increases as the temperature increases and decreases as the temperature decreases
- At some point, it looks like the resistivity would go to zero

Material	Resistivity $\rho$ at 20°C $\mu\Omega \cdot \text{cm}$	Temperature coefficient $\alpha$ at 20°C, $^{\circ}\text{C}^{-1}$
Aluminum	2.83	0.0039
Brass	6.4–8.4	0.0020
Copper		
Hard-drawn	1.77	0.00382
Annealed	1.72	0.00393
Iron	10.0	0.0050
Silver	1.59	0.0038
Steel	12–88	0.001–0.005

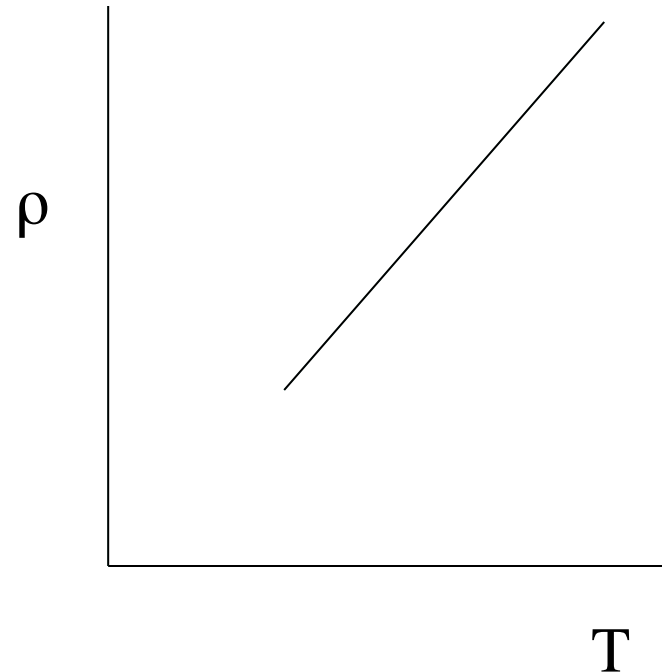

# Rules

- Potential decreases in going from + terminal to - terminal


◆  $\Delta V = -\varepsilon$

- And increases in going from - terminal to + terminal

- Potential decreases in going across resistor in direction of current flow

◆  $\Delta V = -IR$

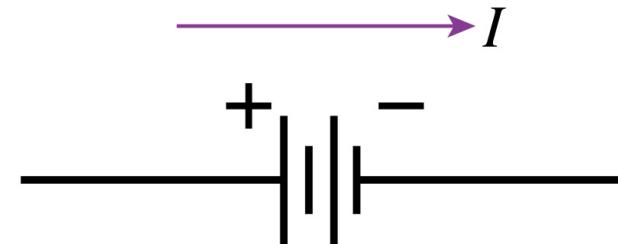- And increases when going across resistor against the direction of current flow



Potential decreases






Potential increases



Potential decreases

# Simple circuit

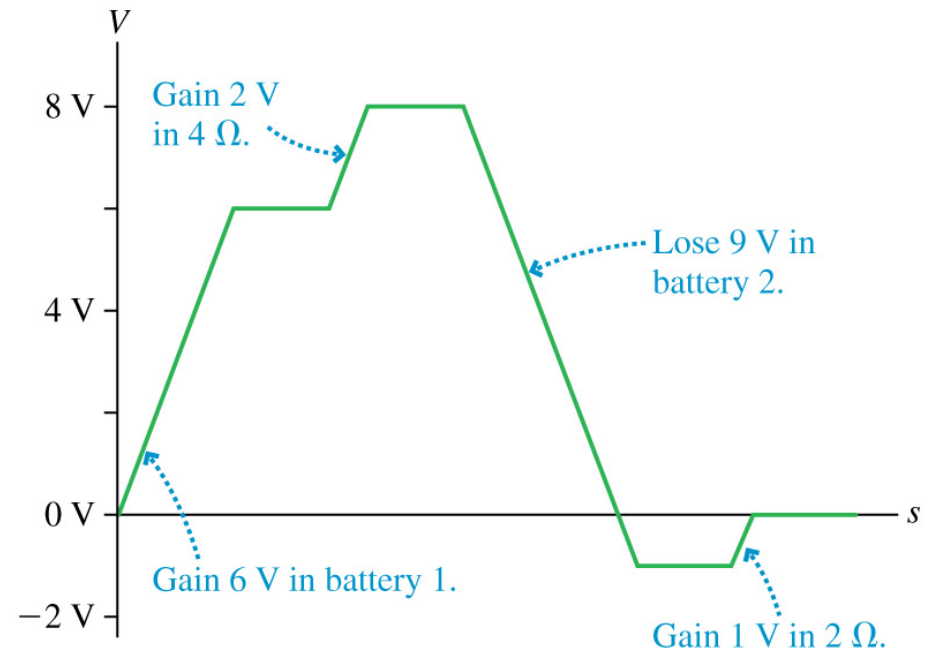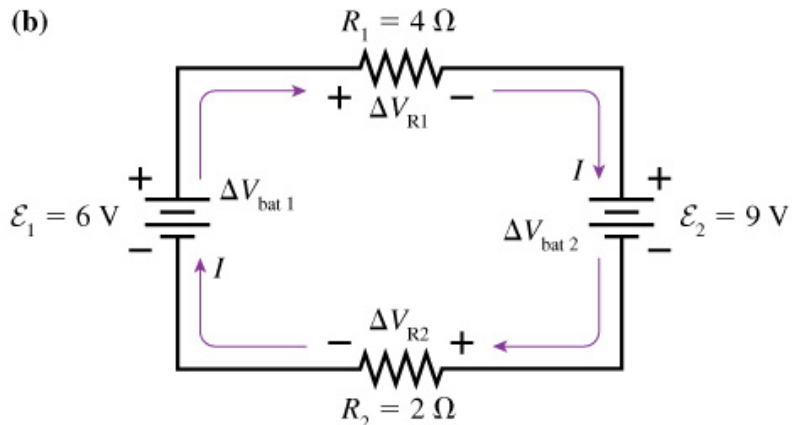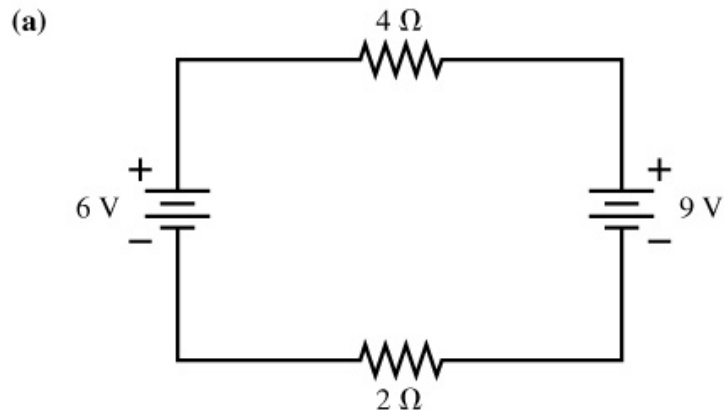





$$\sum_{\text{loop}} \Delta V = \varepsilon_1 - IR_1 - \varepsilon_2 - IR_2 = 0$$

$$I = \frac{\varepsilon_1 - \varepsilon_2}{R_1 + R_2} = \frac{6V - 9V}{4\Omega + 2\Omega} = -0.5A$$

current is opposite direction of what we drew
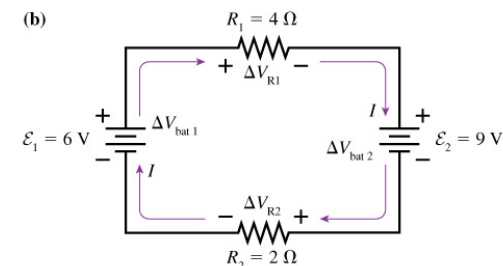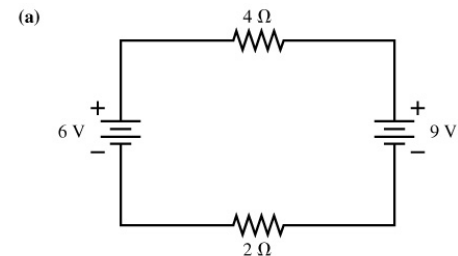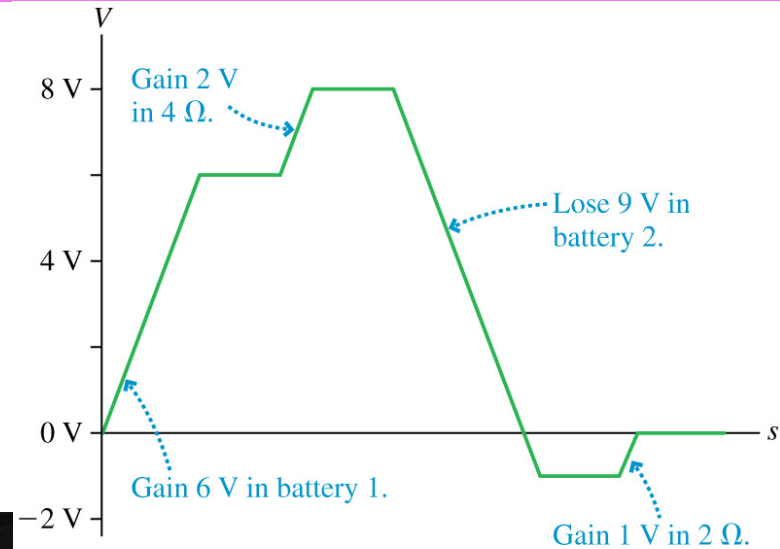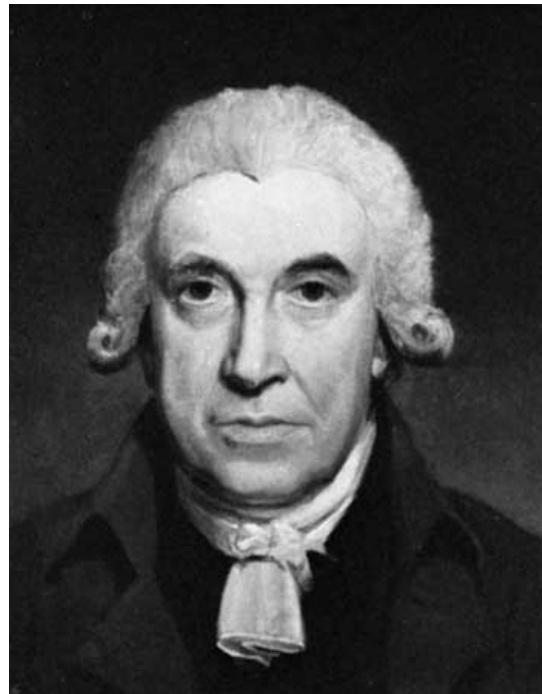
# Energy considerations

- When charge  $+q$  goes from - terminal of battery to + terminal it gains a potential energy of  $\Delta U = q\varepsilon$
- The rate at which energy is gained is given by  $P = \Delta U / dt = dq/dt(\varepsilon) = I\varepsilon$  with units of J/s = W (atts)




# Energy gained is energy lost

- Energy added by battery is lost by electrons during their collisions with atoms and eventually ends up as heat
  - ◆ i.e. the resistor gets warm
- Consider the work done by the electric field for an electron travelling a distance  $d$

$$W = F \Delta s = qEd$$

- The energy transferred to the lattice when the electron collides with an atom then is
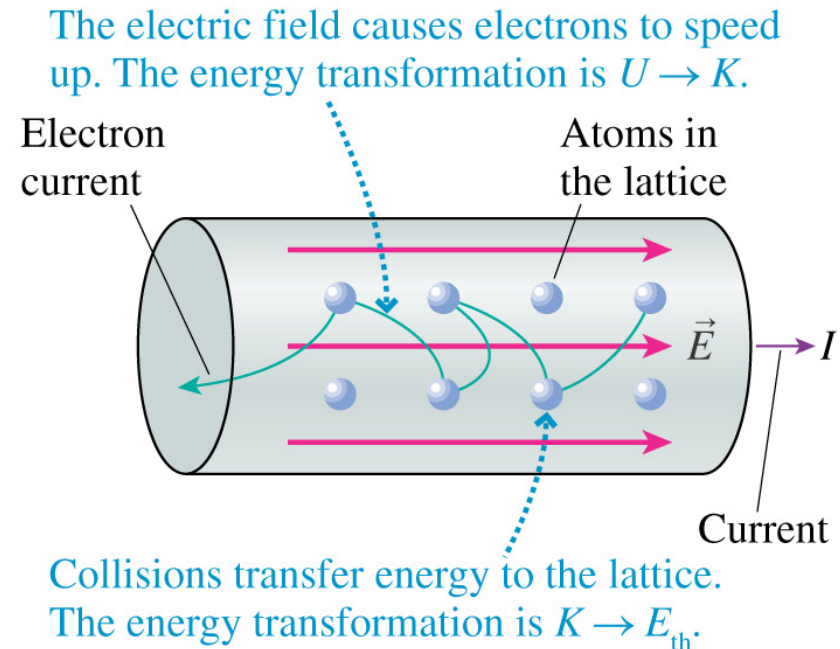
$$\Delta E_{\text{collision}} = \Delta K = qEd$$



- In a length  $L$ , the energy transferred is  $\Delta E = qEL = q\Delta V_R$
- The power dissipated in the resistor then can be written as

$$P_R = \frac{dE}{dt} = \frac{dq}{dt} \Delta V_R = I \Delta V_R = P_{\text{battery}}$$



# Power in electrical circuits

- Can write the power in the following forms

$$P = I\Delta V_R = I^2 R = \frac{\Delta V_R^2}{R}$$

- If I integrate power over time, I have units of energy

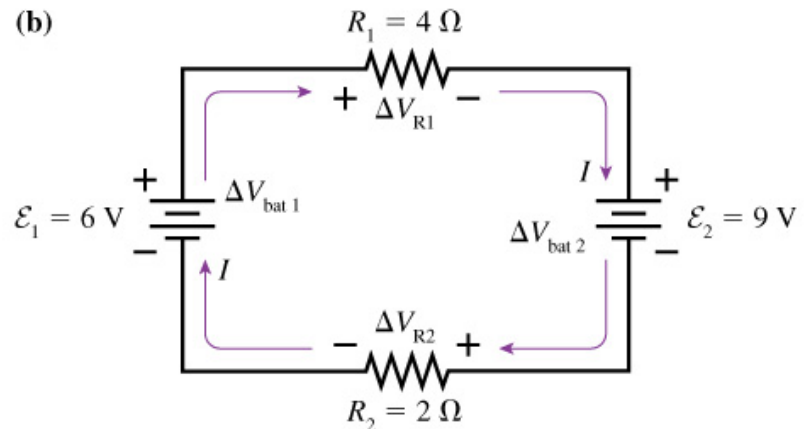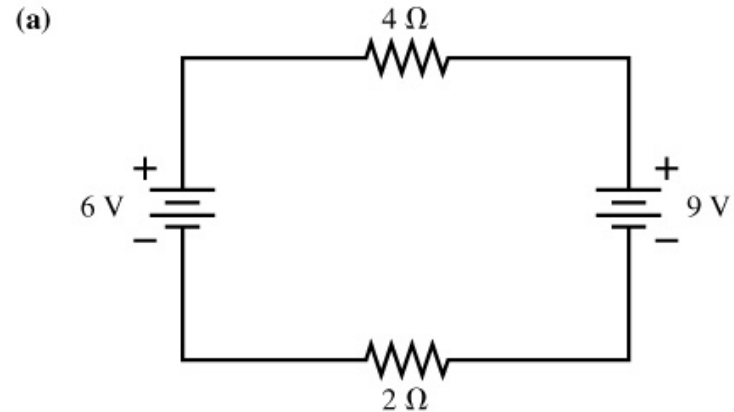- ◆ kW-hr
- ◆  $1000 \text{ J/s} \cdot 3600 \text{ s} = 3.6 \times 10^6 \text{ J/kW-hr}$






# Example

---

- A 100 W (120V) lightbulb contains a 7.0 cm long tungsten filament. The high-temperature resistivity of tungsten is  $9.0 \times 10^{-7} \Omega\text{m}$ . What is the diameter of the filament?
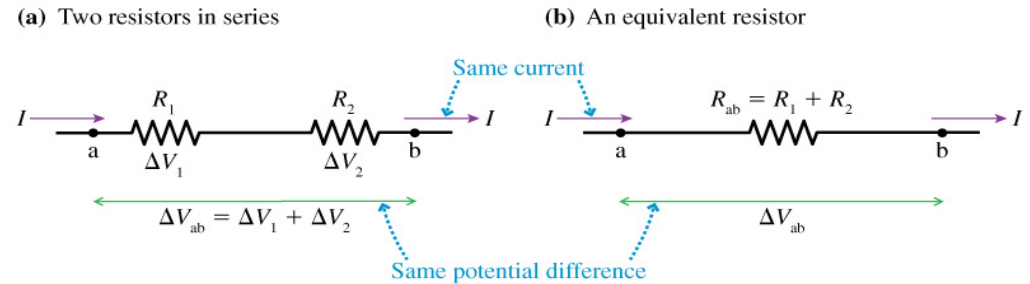
# Resistors in series

- Consider two (or more) resistors in series
- The same current passes through both resistors
- The total voltage drop across the two resistors is the sum of the voltage drops across each resistor
- We'd like to find an equivalent resistance for which the current would be the same given the same voltage drop



$$\Delta V_{ab} = \Delta V_a + \Delta V_b = IR_1 + IR_2$$

$$I = \frac{\Delta V_{ab}}{R_1 + R_2} = \frac{\Delta V_{ab}}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 (+R_3 + \dots)$$