


PHY294H

- Professor: Joey Huston
- email: huston@msu.edu
- office: BPS3230
- Homework will be with Mastering Physics (and an average of 1 hand-written problem per week)
 - ◆ **Problem 29.78 (already assigned) will be the hand-in problem for 4th MP assignment (due Wed Feb. 10)**
 - ◆ **Help-room hours: 12:40-2:40 Tues; 3:00-4:00 PM Friday**
- Quizzes by iclicker (sometimes hand-written)
- Course website: www.pa.msu.edu/~huston/phy294h/index.html
 - ◆ lectures will be posted frequently, mostly every day if I can remember to do so

Capacitance

$$Q = \Delta V_c C$$

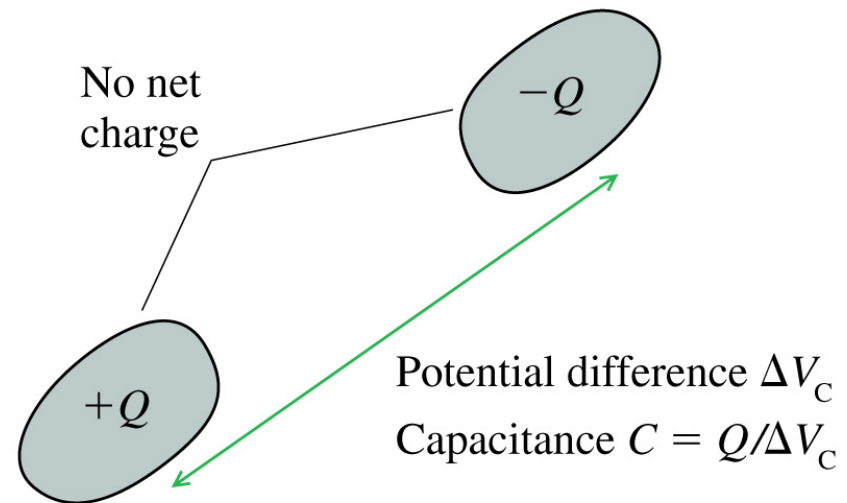- So the amount of charge stored on a capacitor depends on the voltage across the plates of the capacitor and the value of the capacitance
- The capacitance depends on geometric factors
- Simplest capacitor is a parallel plate capacitor but can have any configuration




Spherical capacitor

- Here I've stored a charge $-Q$ on a conducting sphere of radius R_1 placed inside a conducting shell of radius R_2 , which has a charge of $+Q$
- It's a capacitor; what's the capacitance?
- Use the definition of capacitance

$$C = \frac{Q}{\Delta V_c}$$

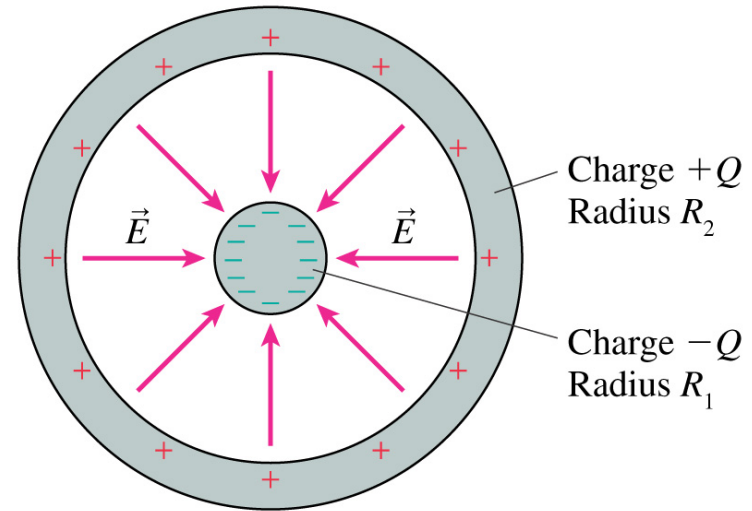- The numerator is easy; it's the denominator that's harder
 - ◆ we have to calculate ΔV_c , but that's something we know how to do; the electric field between the two conductors is that of a point charge of value $-Q$



Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

$$\Delta V_c = - \int_{si}^{sf} E_s ds = - \int_{R_1}^{R_2} \frac{-Q}{4\pi\epsilon_o r^2} dr$$

$$\Delta V_c = \frac{Q}{4\pi\epsilon_o} \left[\frac{1}{R_1} - \frac{1}{R_2} \right]$$


Spherical capacitor

- The capacitance is the charge stored per voltage

$$C = \frac{Q}{\Delta V_c} = \frac{Q}{\frac{Q}{4\pi\epsilon_o} \left[\frac{1}{R_1} - \frac{1}{R_2} \right]} = 4\pi\epsilon_o \frac{R_1 R_2}{R_2 - R_1}$$

- Note that the capacitance depends on ϵ_o and on the geometry of the conductors
- What if R_2 goes to infinity?

$$C = 4\pi\epsilon_o R_1$$

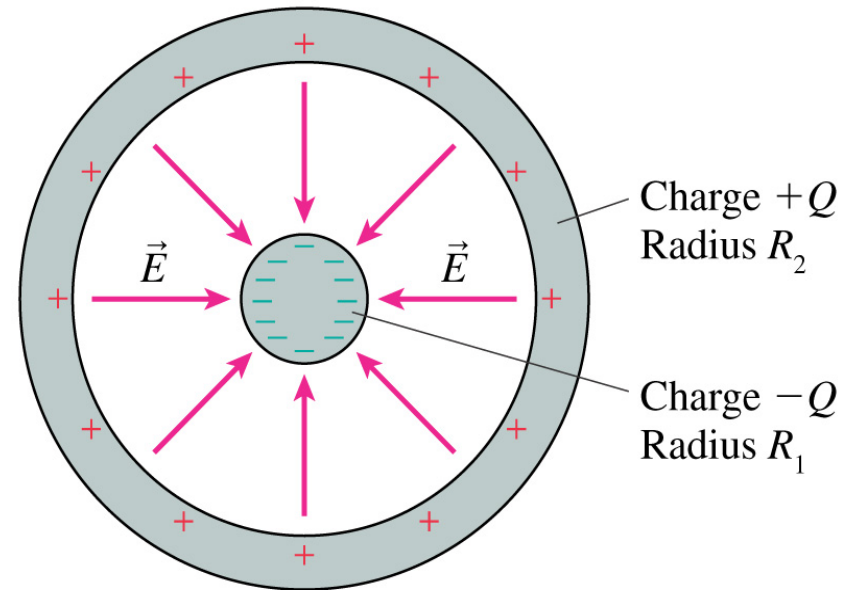


Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley


Capacitors in combination

- Often, we encounter more than one capacitor in a circuit, either joined in series or in parallel
- We would like to answer the question as to what the equivalent capacitance of these combinations is

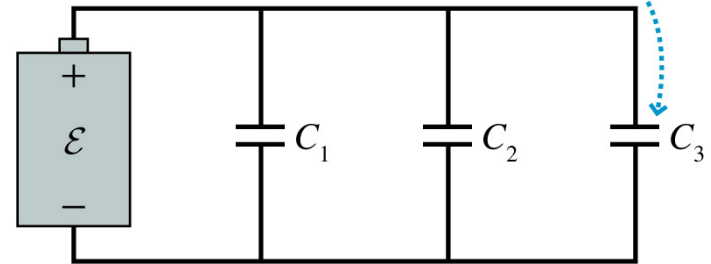The circuit symbol for a capacitor is two parallel lines.





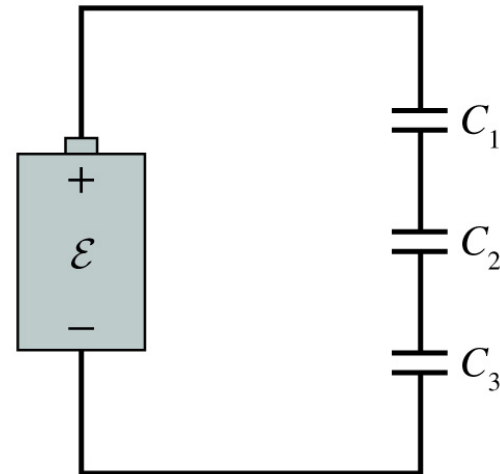Parallel capacitors are joined top to top and bottom to bottom.



Series capacitors are joined end to end in a row.

Capacitors in parallel

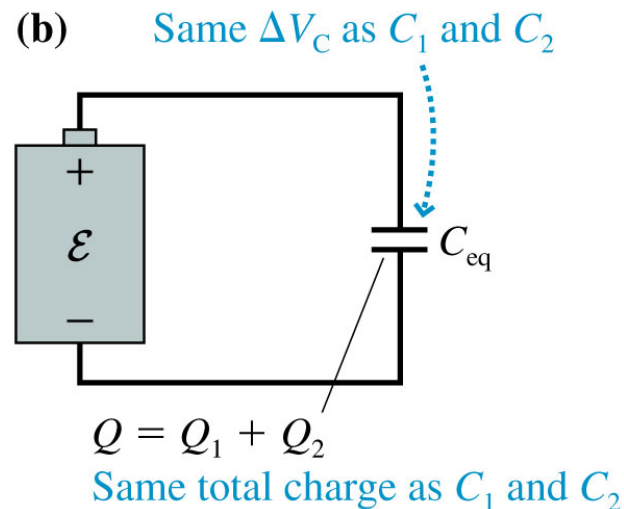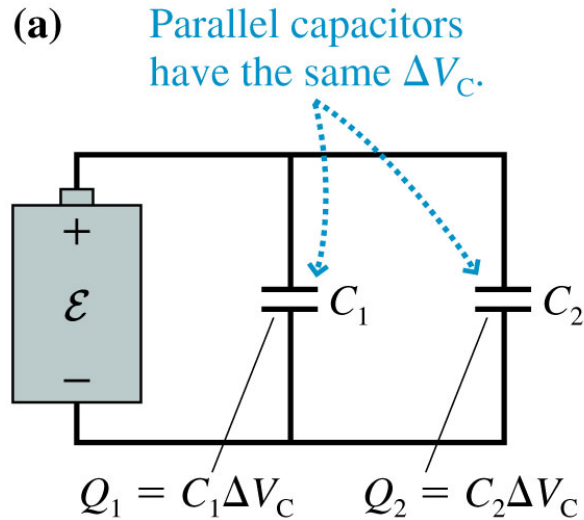


- Consider two capacitors C_1 and C_2 connected in parallel.
- The total charge drawn from the battery is $Q = Q_1 + Q_2$.
- In figure (b) we have replaced the capacitors with a single “equivalent” capacitor:

$$C_{\text{eq}} = \frac{Q}{\Delta V_C} = \frac{Q_1 + Q_2}{\Delta V_C} = \frac{Q_1}{\Delta V_C} + \frac{Q_2}{\Delta V_C}$$

$$C_{\text{eq}} = C_1 + C_2$$

If capacitors C_1 , C_2 , C_3 , ... are in parallel, their equivalent capacitance is:
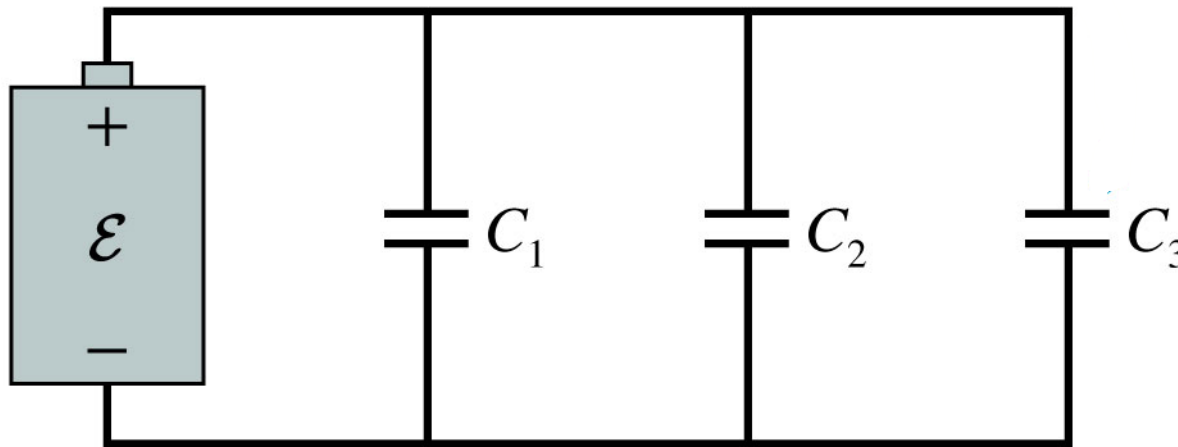
$$C_{\text{eq}} = C_1 + C_2 + C_3 + \cdots \quad (\text{parallel capacitors})$$




Capacitors in series


- Same idea; replace two or more capacitors in series with one capacitor able to store the same charge (given a voltage)
- In this case, we know that the two capacitors store the same amount of charge, but that the voltage is not necessarily the same
- But we also know that the sum of the voltages across C_1 and C_2 must equal the total voltage provided by the battery

$$\Delta V = \varepsilon = \Delta V_1 + \Delta V_2$$

(a) Series capacitors have the same Q .

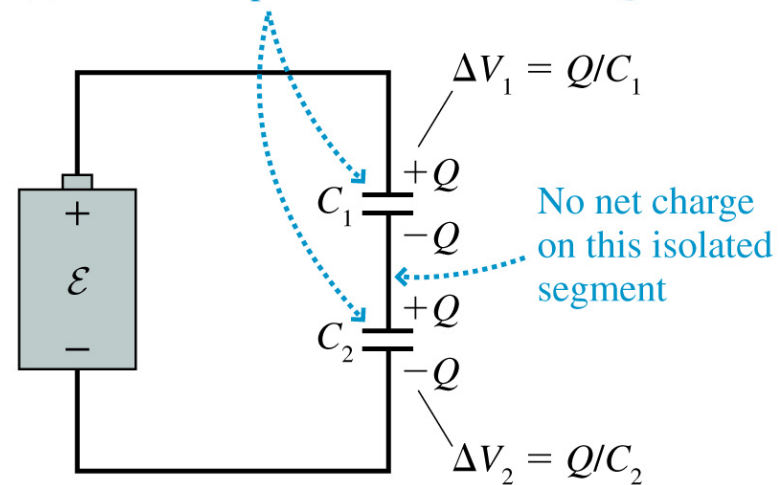

(b) Same Q as C_1 and C_2

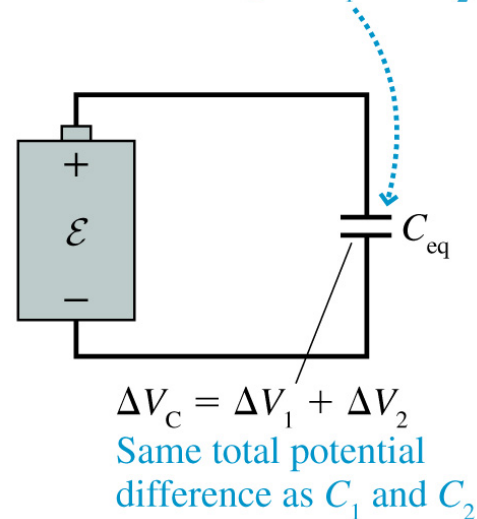

Capacitors in series


- For capacitors in series, you add the reciprocals of the individual capacitances to find the reciprocal of the equivalent capacitance

$$\Delta V = \varepsilon = \Delta V_1 + \Delta V_2 = \frac{Q}{C_1} + \frac{Q}{C_2}$$


$$\Delta V = \frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \left(+ \frac{1}{C_3} + \dots \right)$$


(a) Series capacitors have the same Q .

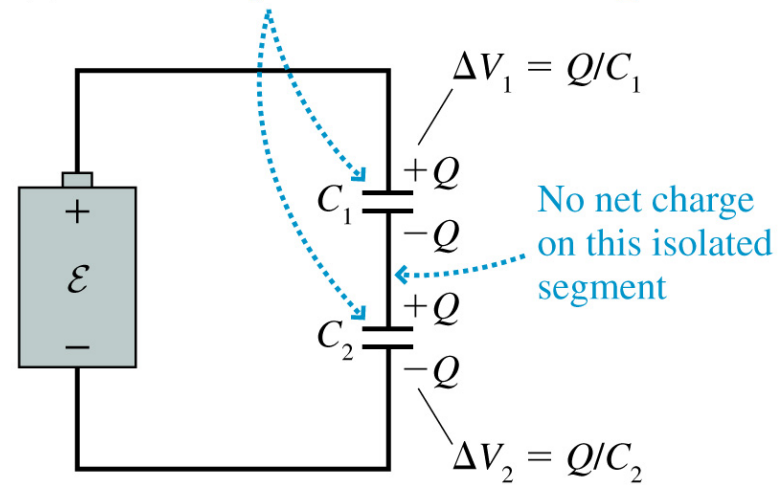


(b) Same Q as C_1 and C_2

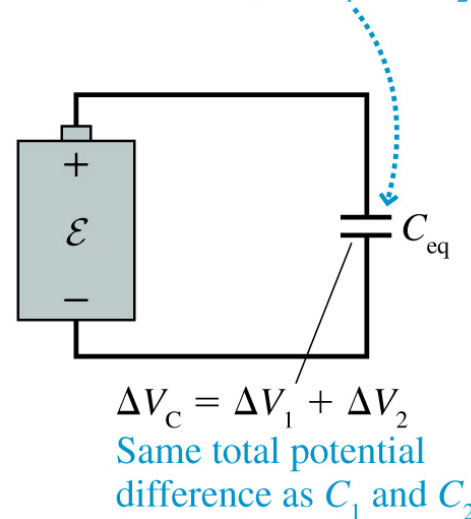

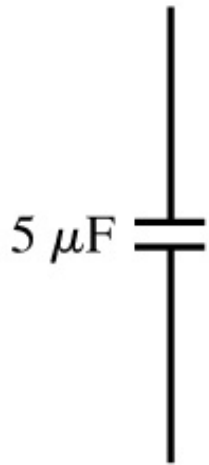
Which combination has the highest capacitance?




(a)

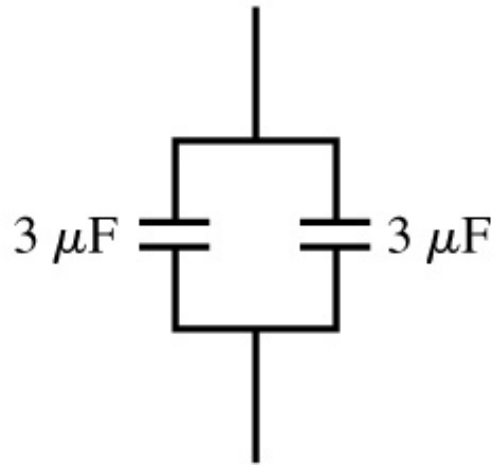

(b)

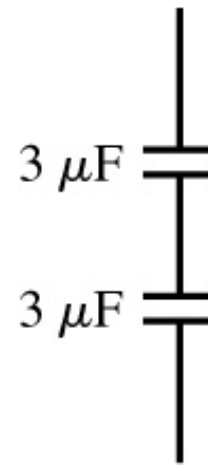


(c)

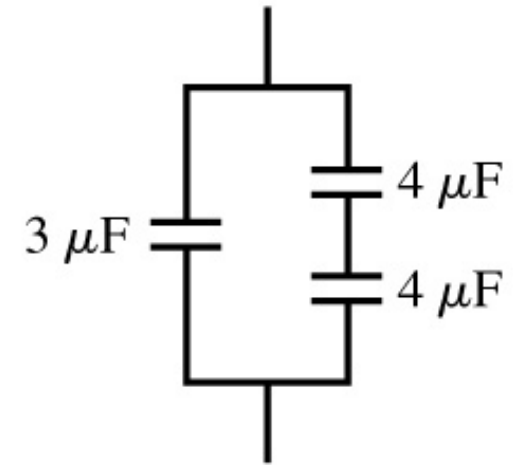

(d)

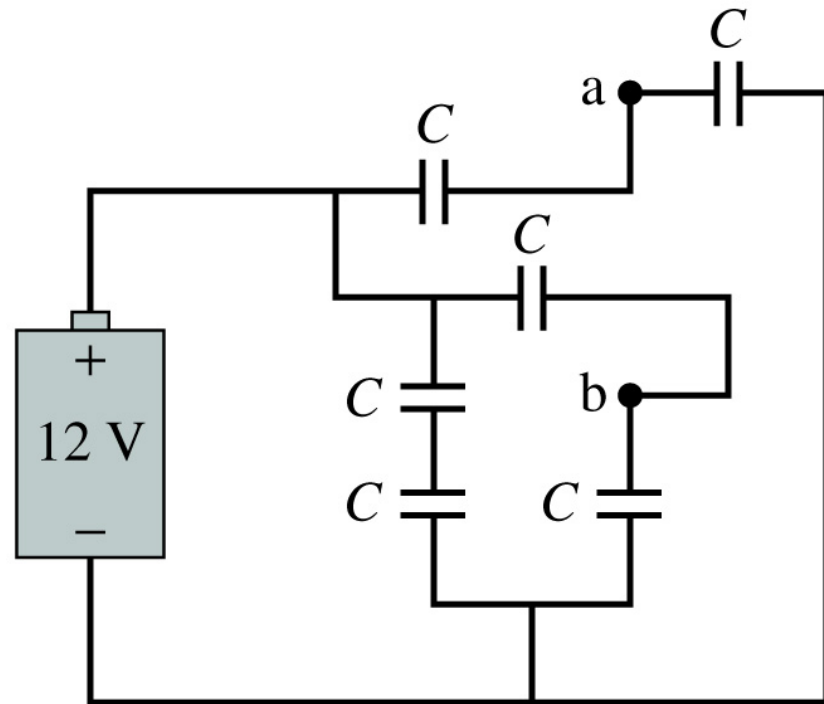Example

- What is the equivalent capacitance of these six capacitors?
- What is the voltage between a and b?



Energy stored in capacitor


- When the battery moves a charge dq from the bottom plate to the top plate, it represents an increase of potential energy stored in the capacitor

$$dU = dq\Delta V = \frac{q dq}{C}$$

- We can calculate the total potential energy stored in the capacitor when it becomes fully charged

$$U_C = \int dU = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C} = \frac{1}{2} C (\Delta V_C)^2$$

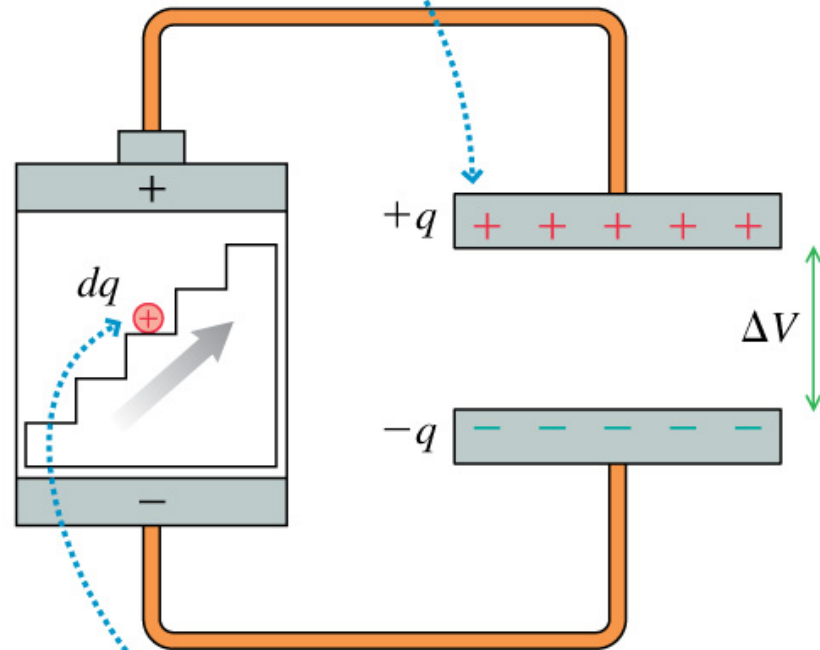The instantaneous charge on the plates is $\pm q$.



The charge escalator does work $dq \Delta V$ to move charge dq from the negative plate to the positive plate.

Uses for energy stored in capacitor

- Defibrillator



- Flashlamp



Uses for energy stored in capacitor



A capacitor charged to 1.5 V stores 2.0 mJ of energy. If the capacitor is charged to 3.0 V, it will store

- A. 1.0 mJ.
- B. 2.0 mJ.
- C. 4.0 mJ.
- D. 6.0 mJ.
- E. 8.0 mJ.

A capacitor charged to 1.5 V stores 2.0 mJ of energy. If the capacitor is charged to 3.0 V, it will store

A. 1.0 mJ.

B. 2.0 mJ.

C. 4.0 mJ.

D. 6.0 mJ.

✓ E. 8.0 mJ.

$$U_C \propto (\Delta V)^2$$

Energy in electric field


- You can think of the energy stored in the capacitor as being stored in the electric field created between the two plates of the charged capacitor
- Take a parallel plate capacitor for convenience

$$U_C = \frac{1}{2} C (\Delta V_C)^2 = \frac{1}{2} \frac{\epsilon_o A}{d} (Ed)^2$$

$$U_C = \left(\frac{1}{2} \epsilon_o E^2 \right) (Ad)$$


$$u_E = U_C / Vol = \frac{1}{2} \epsilon_o E^2 \quad (\text{energy density})$$

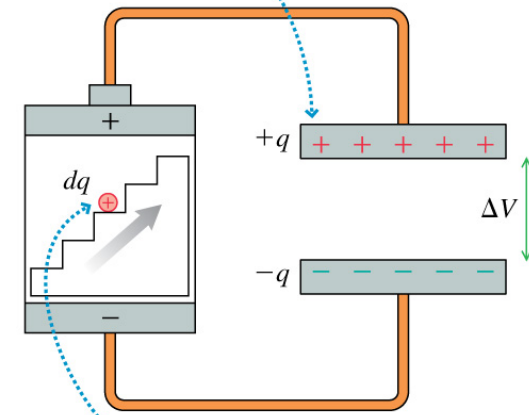The instantaneous charge on the plates is $\pm q$.



The charge escalator does work $dq \Delta V$ to move charge dq from the negative plate to the positive plate.

Capacitor plate with area A

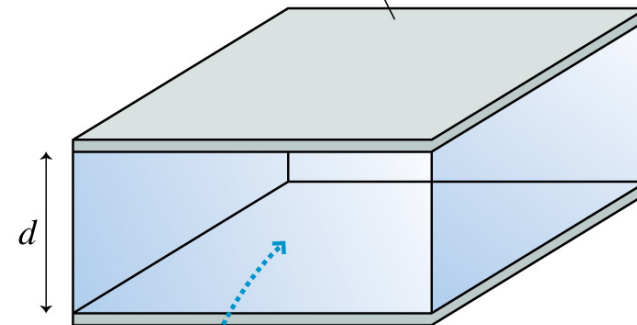

The capacitor's energy is stored in the electric field in volume Ad between the plates.

Example

- What is the energy density in the electric field at the surface of a 1.0 cm diameter sphere charged to a potential of 1000 V?
- What is the energy stored in the capacitor?

Farad capacitor at Fermilab

