


# Physics 294H

---


- Professor: Joey Huston
- email: [huston@msu.edu](mailto:huston@msu.edu)
- office: BPS3230
- Homework will be with Mastering Physics (and an average of 1 hand-written problem per week)
  - ◆ **Help-room hours: 12:40-2:40 Monday (note change); 3:00-4:00 PM Friday**
  - ◆ **hand-in problem for Wed Mar. 23: 34.60**
  - ◆ **Note I revised Homework assignment 9 (due 3/23) adding some problems that were due a week later**
- Quizzes by iclicker (sometimes hand-written)
- 2<sup>nd</sup> exam next Thursday
- **Final exam Thursday May 5 10:00 AM – 12:00 PM 1420 BPS**
- Course website: [www.pa.msu.edu/~huston/phy294h/index.html](http://www.pa.msu.edu/~huston/phy294h/index.html)
  - ◆ lectures will be posted frequently, mostly every day if I can remember to do so
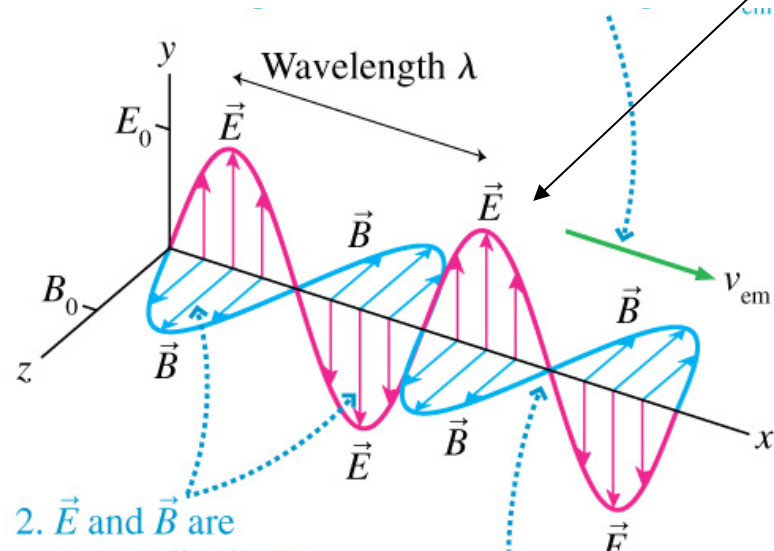
# Polarization


- the plane containing the electric field vector and the Poynting vector  $\vec{S}$  is called the plane of polarization of the EM wave



(a) Vertical polarization

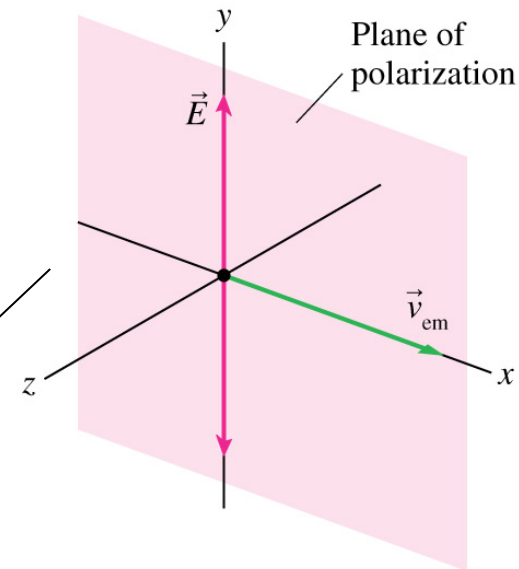


(b) Horizontal polarization

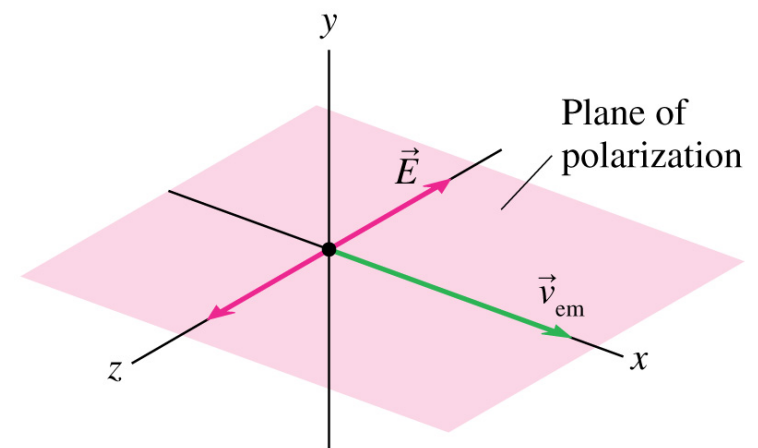
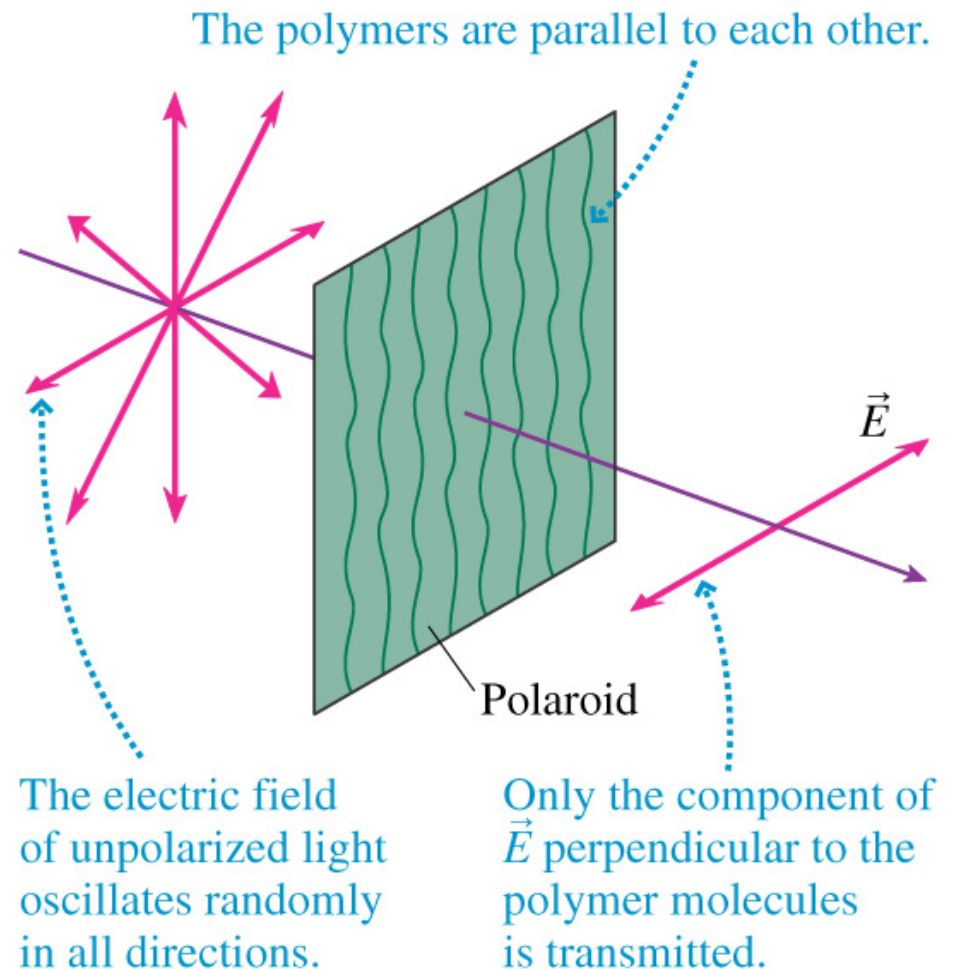
# Polarizing filter

- Ordinary electromagnetic waves are unpolarized
  - ◆ the electric field vectors for each wave are random
- A polarizing filter lets in only those EM waves with a polarization in a particular direction
  - ◆ polymer chains are treated to make them conducting
  - ◆ electrons absorb energy from EM waves whose electric fields oscillate in the direction of the chains



# Polarization

- Electric field from EM wave can be decomposed into components along x (perpendicular to polarization axis) and y directions (parallel to)

$$\vec{E}_{incident} = E_o \sin \theta \hat{i} + E_o \cos \theta \hat{j}$$



- If the filter is 100% efficient, then only component perpendicular to polarization axis is transmitted

$$\vec{E}_{transmitted} = E_o \cos \theta \hat{j}$$

- The intensity of light depends on the square of the electric field so for initial polarized light

$$I_{transmitted} = I_o \cos^2 \theta$$

(Malus' law)

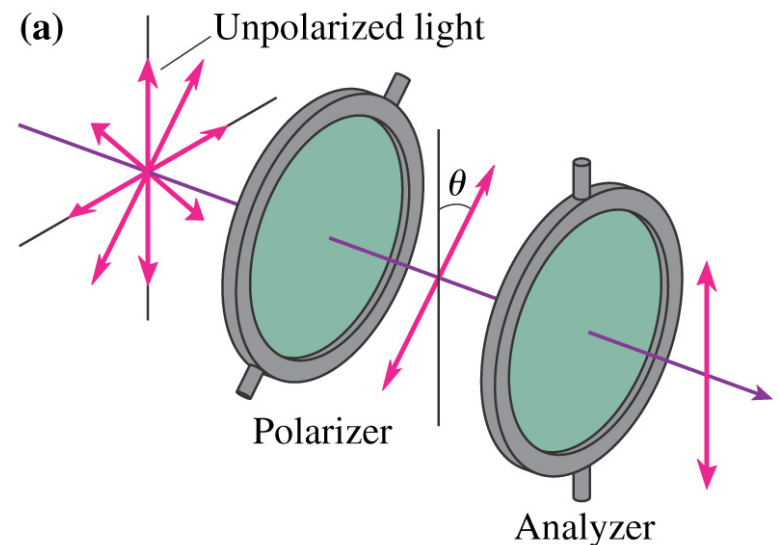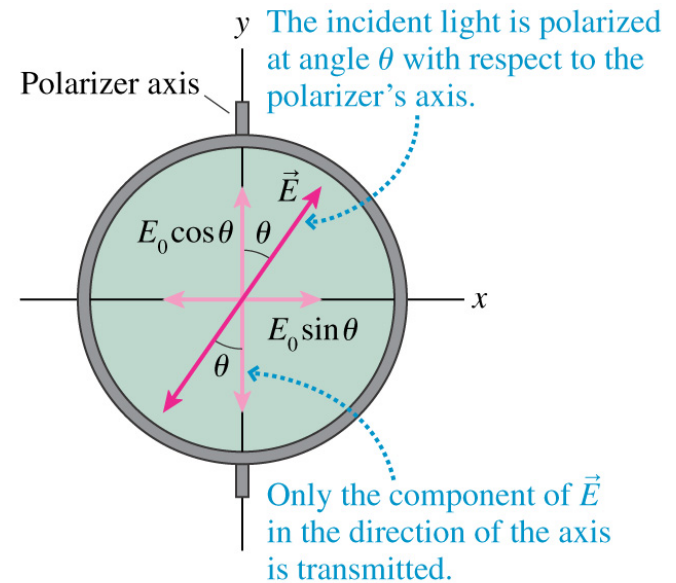


# Polarization

- If the light is initially unpolarized, then the direction of the electric field is random, and the average value of  $\cos^2\theta$  is 0.5


$$I_{\text{transmitted}} = I_o \overline{\cos^2 \theta}$$
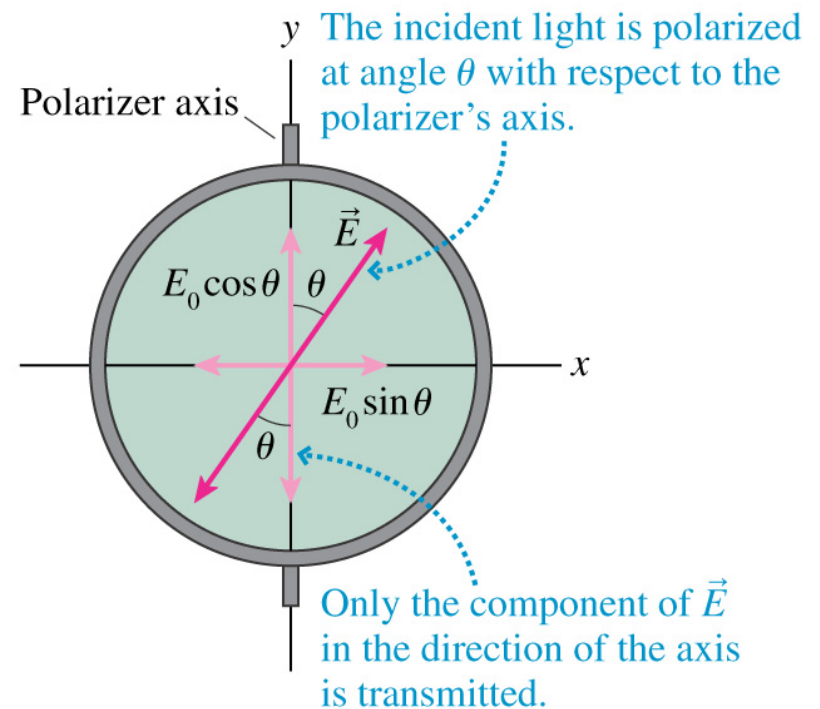
$$I_{\text{transmitted}} = I_o \left( \frac{1}{2} \right)$$



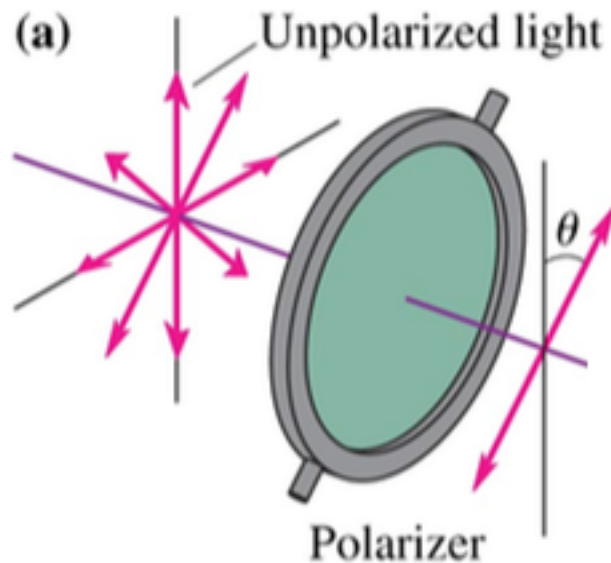
# iclicker question

Unpolarized light is incident on a polarizing filter with an intensity of  $50 \text{ W/m}^2$ . What is the intensity of the light after it passes through the polarizer?



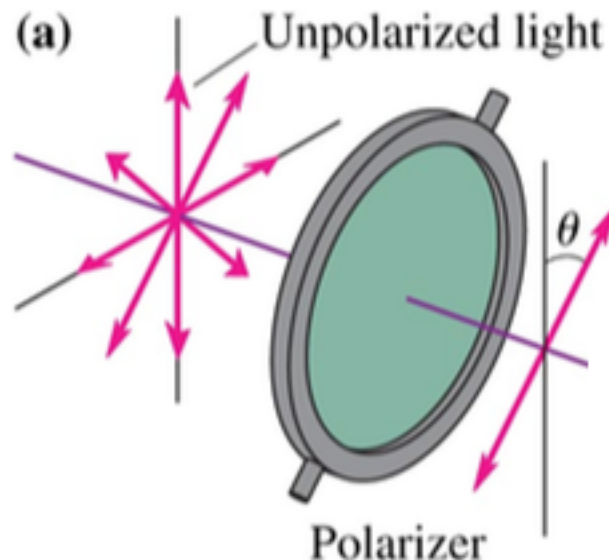- A.  $10 \text{ W/m}^2$
- B.  $25 \text{ W/m}^2$
- C.  $50 \text{ W/m}^2$
- D.  $100 \text{ W/m}^2$

Unpolarized light is incident on a polarizing filter with an intensity of  $50 \text{ W/m}^2$ . What is the intensity of the light after it passes through the polarizer?



$$I_{\text{transmitted}} = \frac{1}{2} I_{\text{unpolarized}}$$


- A.  $10 \text{ W/m}^2$
- B.  $25 \text{ W/m}^2$
- C.  $50 \text{ W/m}^2$
- D.  $100 \text{ W/m}^2$

**Answer: B, When unpolarized light strikes a polarizer you lose half of the intensity.  $I_{\text{transmitted}} = \frac{1}{2} * 50 = 25 \text{ W/m}^2$ .**



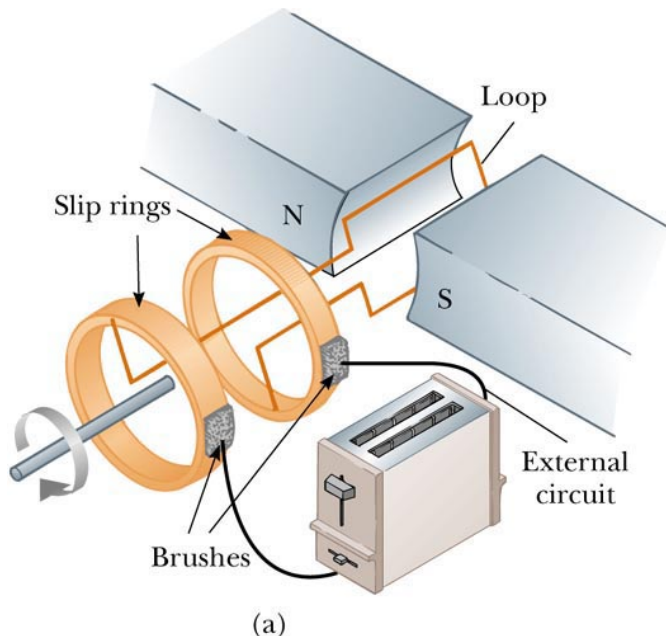
# AC circuits

- We saw earlier that an electric generator produced an alternating voltage and current



(a)  
© 2003 Thomson - Brooks Cole

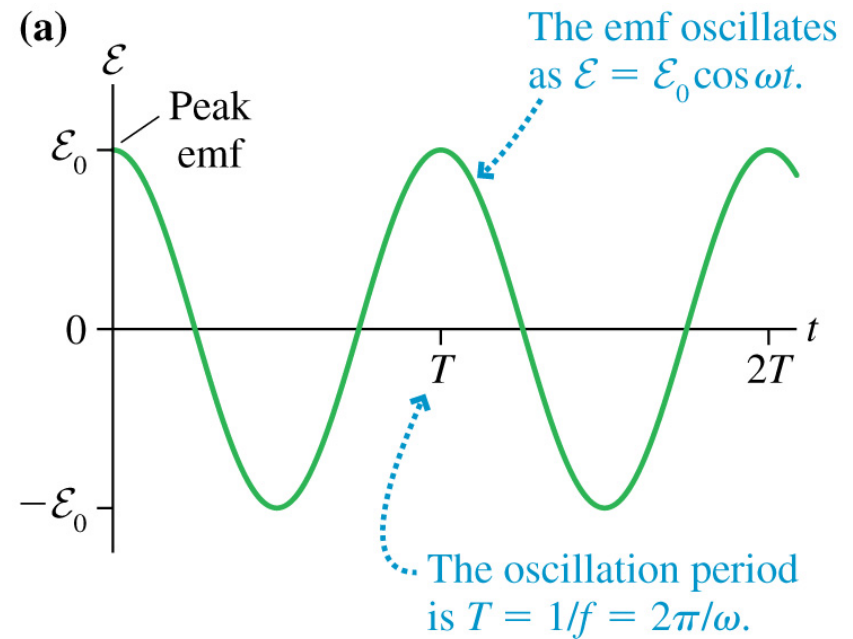


Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley



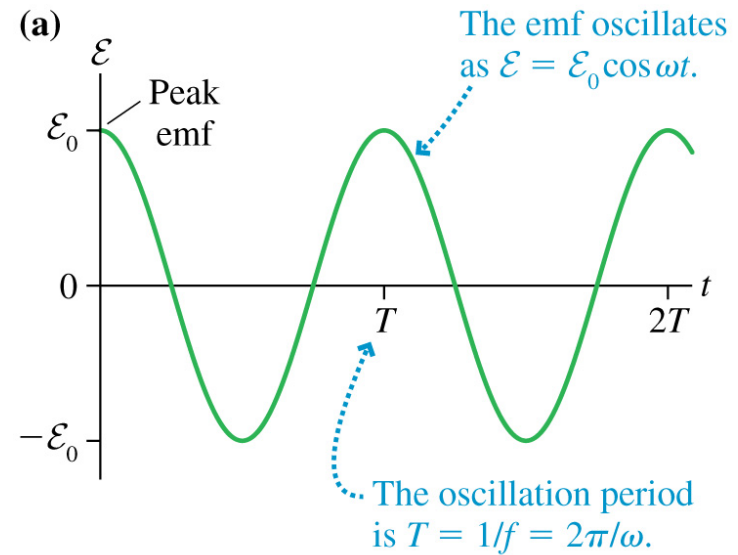
# Phasers

- It is useful to represent AC voltages and currents with phasers



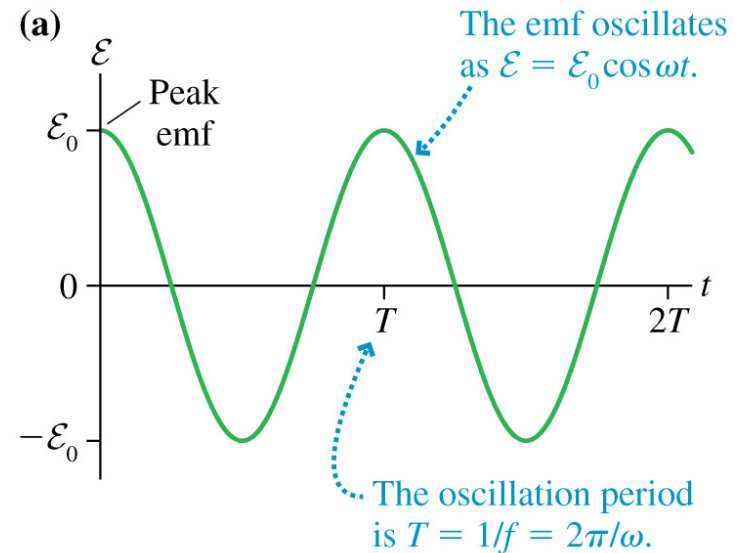
# Phasers

- It is useful to represent AC voltages and currents with phasers



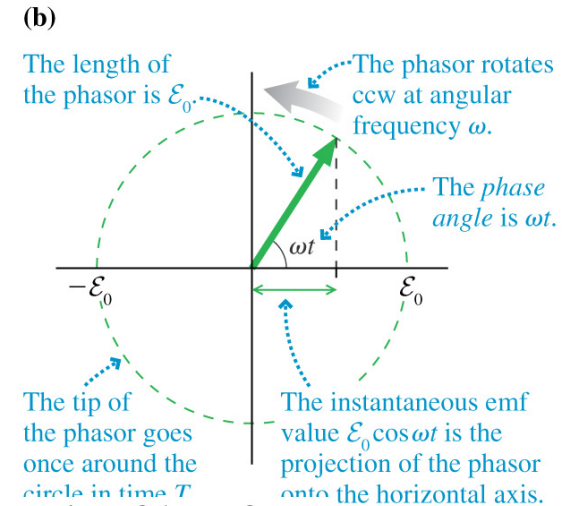
# Phasors

- Wrong spelling...sorry
- A phasor is a vector that rotates counterclockwise around the origin with an angular frequency  $\omega$ 
  - ◆ the instantaneous value of a quantity (voltage, current) is the projection of the phasor on the horizontal axis
  - ◆ sometimes it's defined with respect to the vertical axis, but that just causes a phase change
  - ◆  $\omega t$  is called the phase angle



Graphical representation of the emf

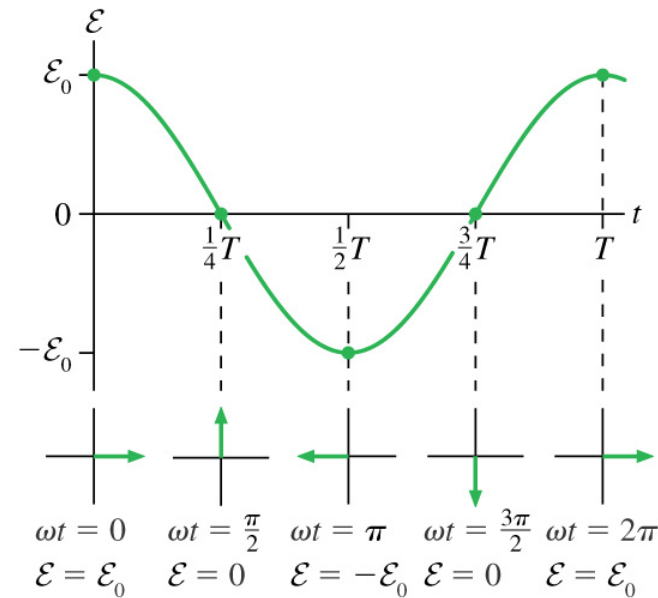

Phasor representation of the emf


# AC circuits with resistors

- Suppose I have a circuit consisting of an AC generator and a resistor
- I want to look at the currents and voltages in the circuits
- I do it the same way I did it for DC circuits, using Kirchoff's laws


$$\sum \Delta V = \Delta V_{\text{source}} + \Delta V_R = \mathcal{E} - v_R = 0$$

$$v_R = \mathcal{E} = \mathcal{E} \cos \omega t$$

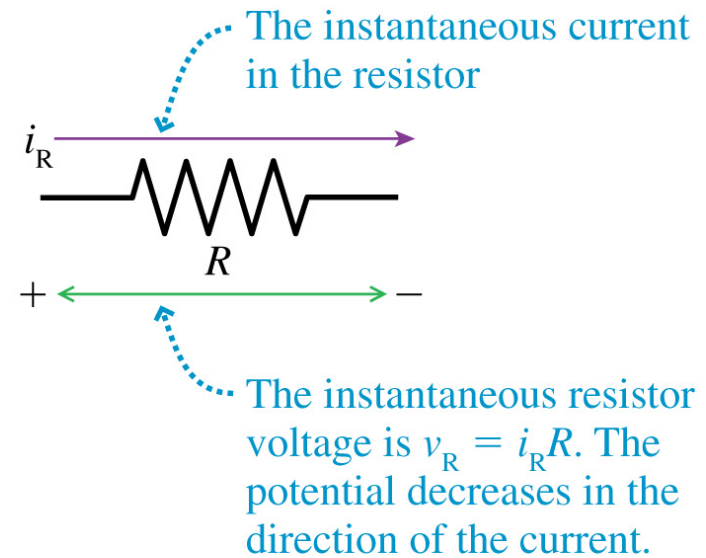- The voltage of the generator appears across the resistor, in phase



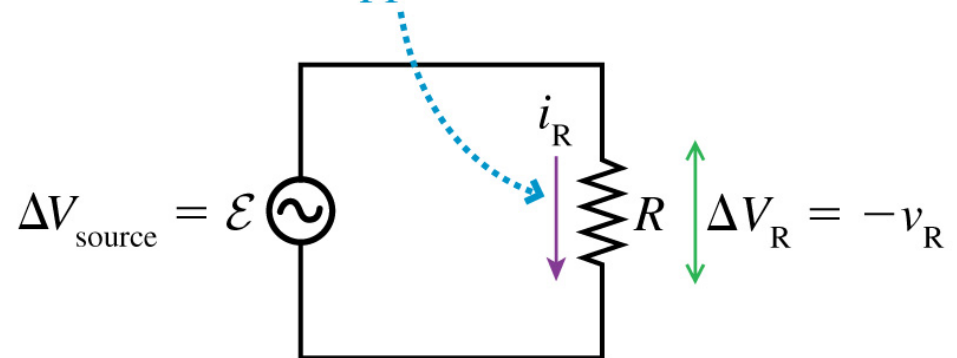This is the current direction when  $\mathcal{E} > 0$ . A half cycle later it will be in the opposite direction.



# AC circuits with resistors

- So I can write the voltage and current as

instantaneous values


$$v_R = V_R \cos \omega t$$

$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$


maximum values

- Note that the voltage and current are in phase with each other and they have the same angular velocity  $\omega$

(b)

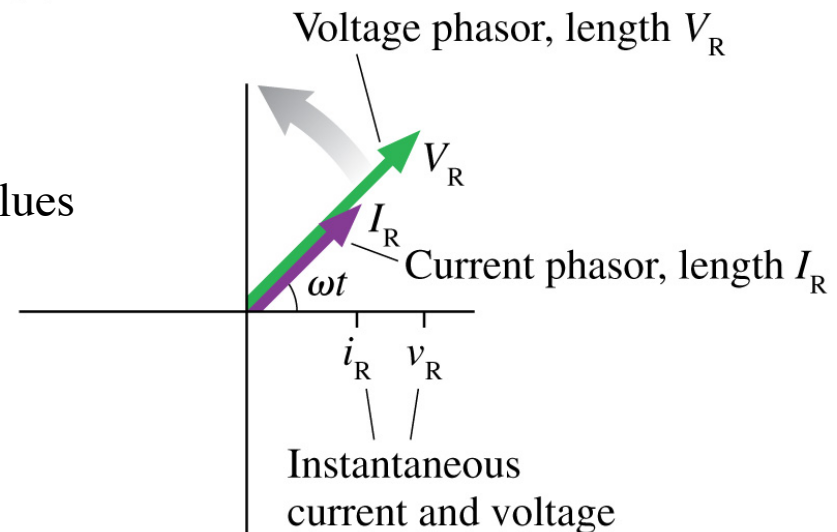

(a)

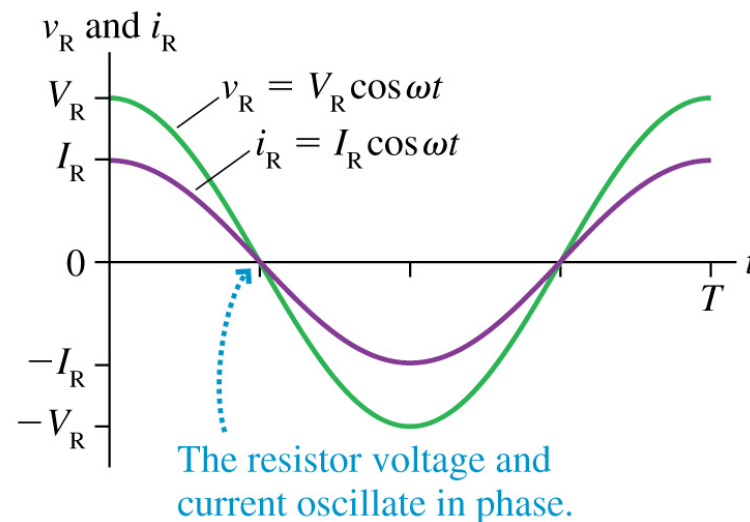

# AC circuits with capacitors

- We can write the voltage across the capacitor as

$$v_c = V_c \cos \omega t$$



$\nwarrow$   
 $\epsilon_0$

- The charge on the capacitor is

$$q = C v_c = C V_c \cos \omega t$$

- The current is
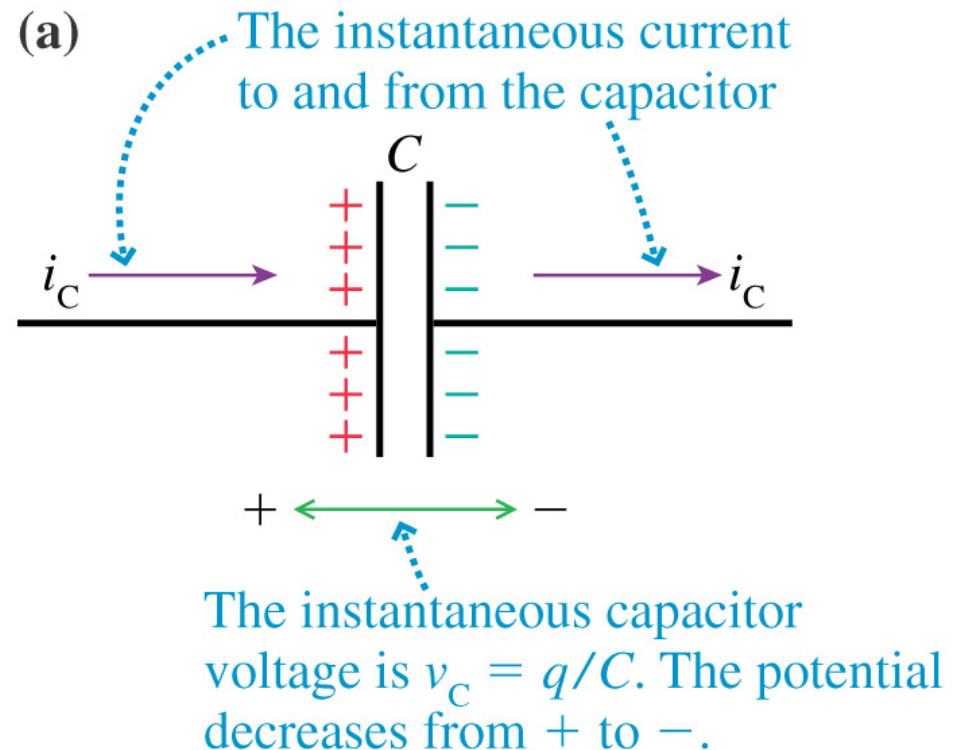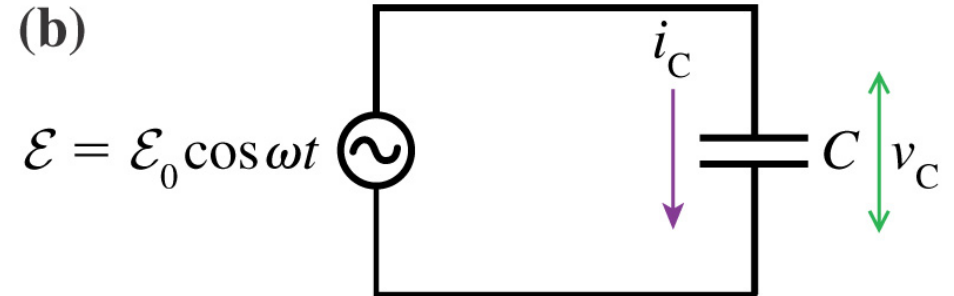
$$i = \frac{dq}{dt} = -\omega C V_c \sin \omega t$$



# AC circuits with resistors

- So I can write the voltage and current as

instantaneous values


$$v_R = V_R \cos \omega t$$

$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$


maximum values

- Note that the voltage and current are in phase with each other and they have the same angular velocity  $\omega$

(b)

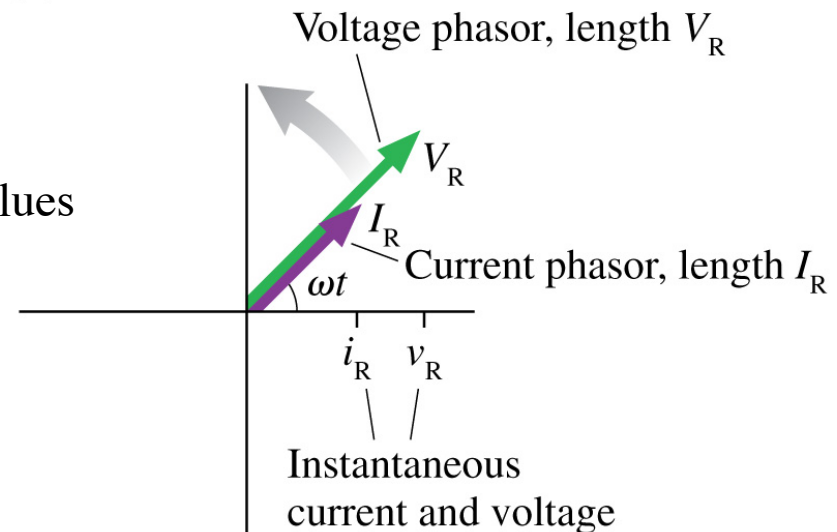

(a)

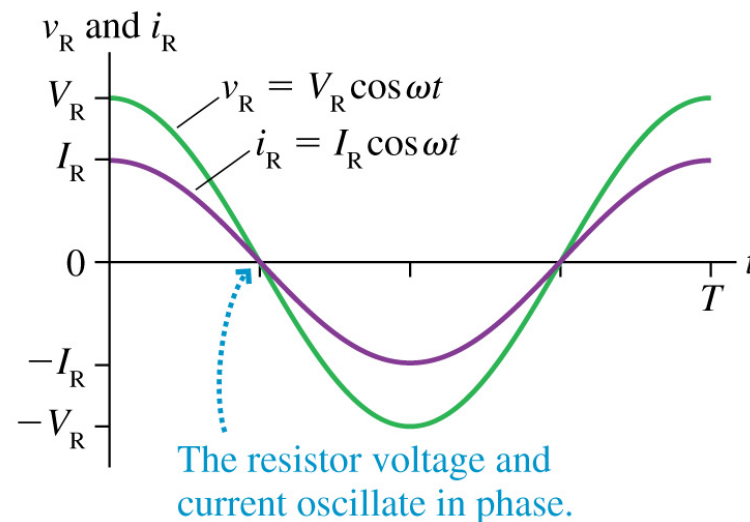



# AC circuits with capacitors

- We can write the voltage across the capacitor as

$$v_c = V_c \cos \omega t$$



$\nwarrow$   
 $\epsilon_0$

- The charge on the capacitor is

$$q = C v_c = C V_c \cos \omega t$$

- The current is
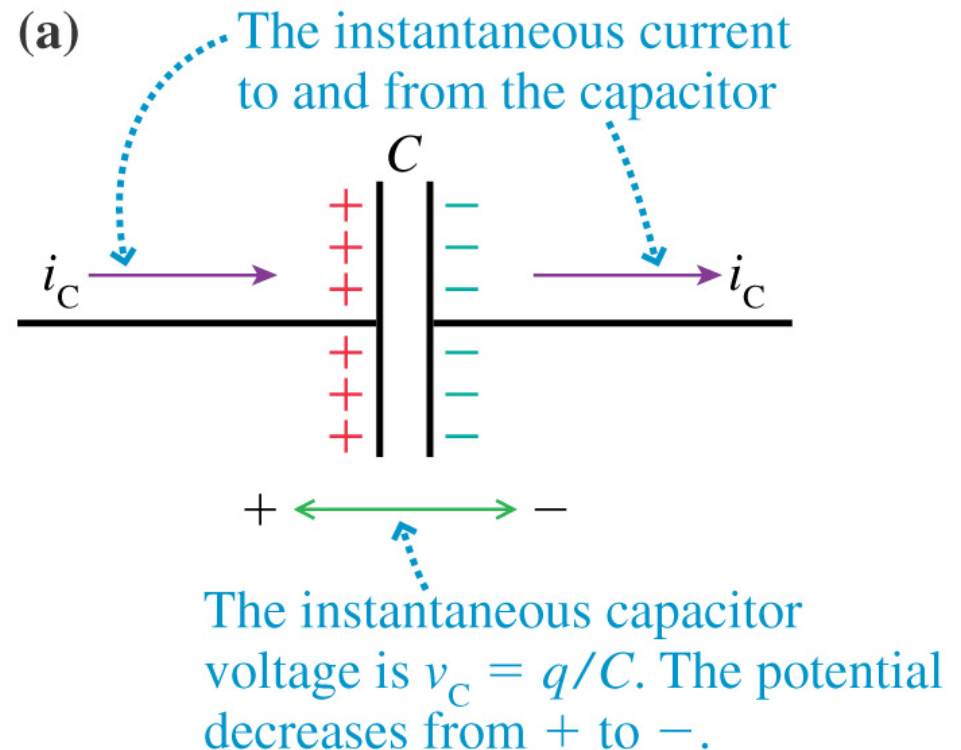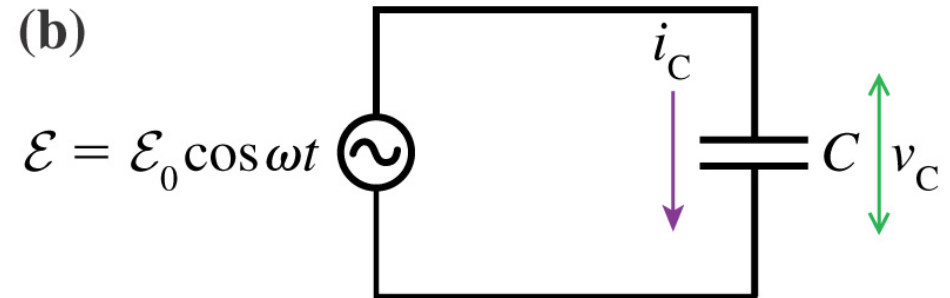
$$i = \frac{dq}{dt} = -\omega C V_c \sin \omega t$$






# AC circuits with capacitors

- I can also write

$$i = \omega C V_c \cos\left(\omega t + \frac{\pi}{2}\right)$$

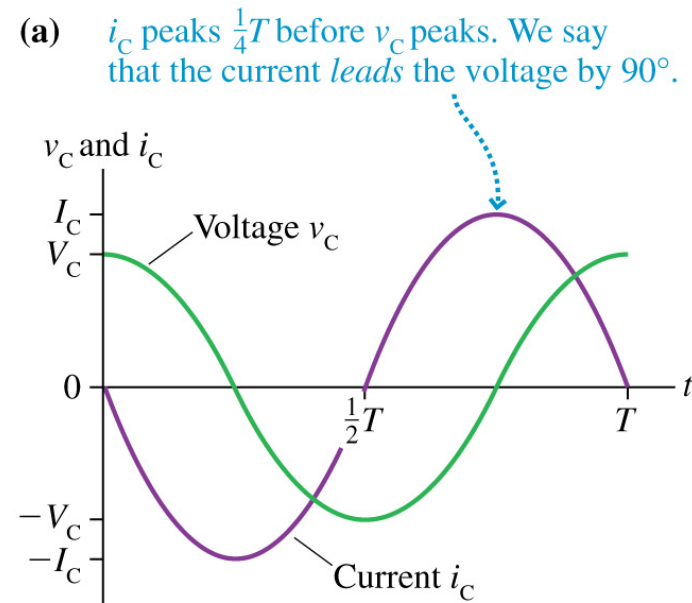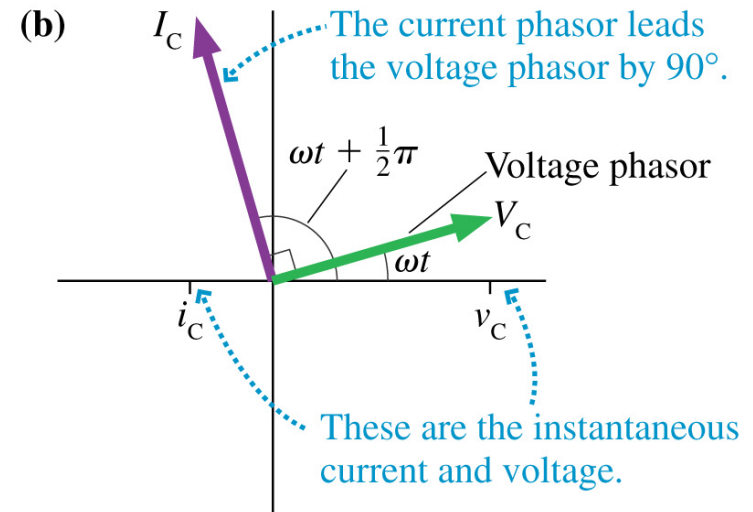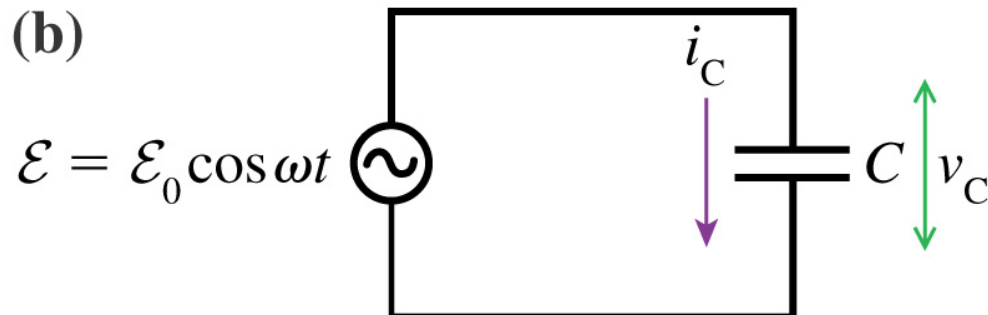- The AC current through a capacitor leads the voltage by  $90^\circ$



# AC circuits with capacitors

- We can define the capacitive reactance  $X_c$  as

$$X_c = \frac{1}{\omega C}$$


$$I_c = \frac{V_c}{X_c}$$

$$V_c = I_c X_c$$

- Note that the reactance relates the peak voltage and the peak current and not the instantaneous voltage and current

$$v_c \neq i_c X_c$$


- The unit of reactance is  $\Omega$

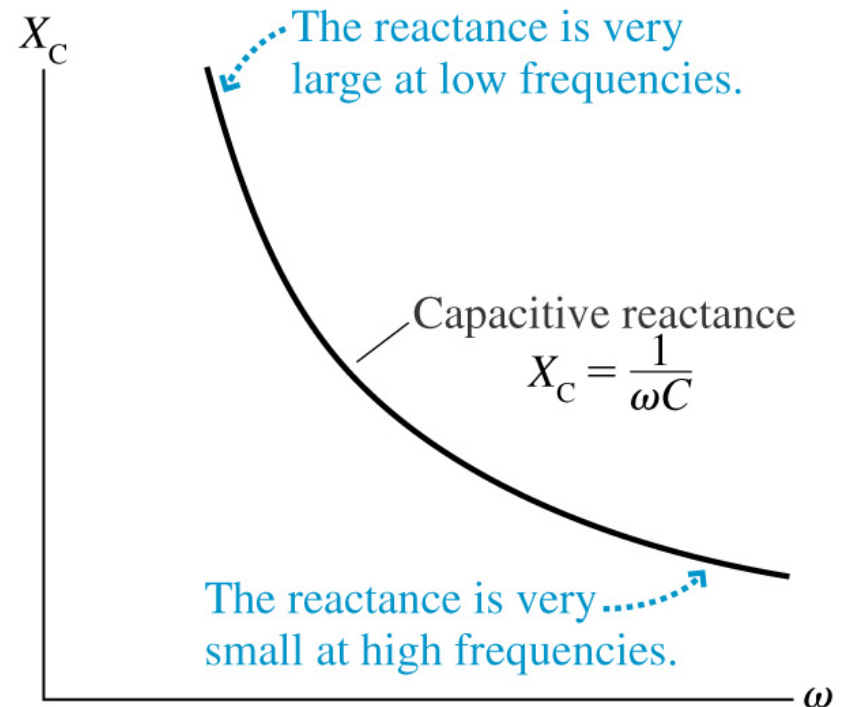
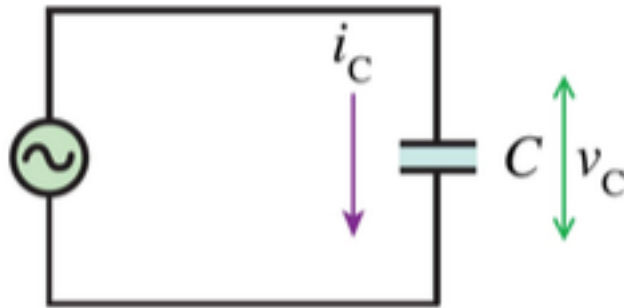
# iclicker question

---

- A capacitor is attached to an AC voltage source. How could you double the current in the circuit?




- A. Double the capacitance.
- B. Double the voltage.
- C. Double the frequency.
- D. All of the above.

$$I_C =$$
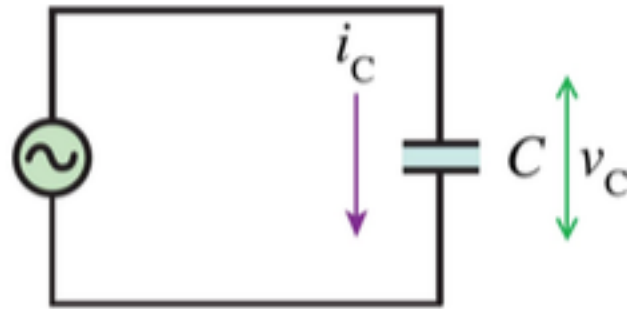
# iclicker question

- A capacitor is attached to an AC voltage source. How could you double the current in the circuit?



$$I_C = \frac{V_C}{X_C}$$

$$X_C = \frac{1}{\omega C}$$

- A. Double the capacitance.
- B. Double the voltage.
- C. Double the frequency.
- D. All of the above.



$$I_C = \frac{V_C}{X_C} = \omega C V_C$$

**Answer: D, The capacitive reactance,  $X_C$ , is  $(2\pi fC)^{-1}$  so doubling the capacitance OR the voltage OR the frequency would all work.**
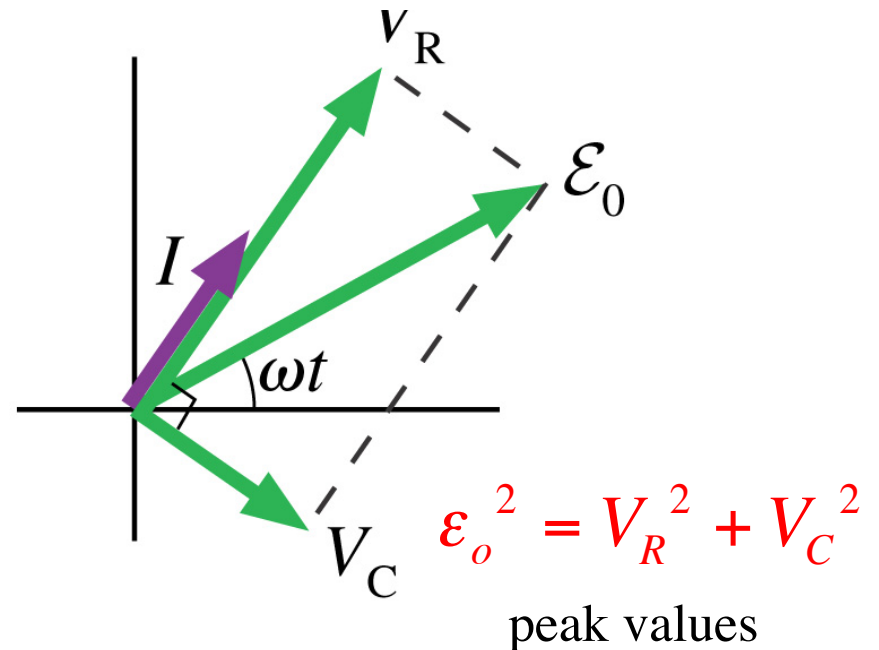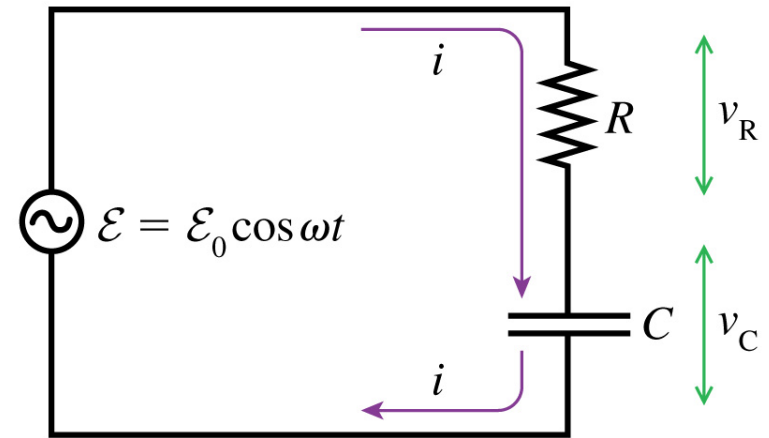
# Circuits with resistors and capacitors

- If the frequency is low, then we expect  $X_C$  to be larger than  $R$ , while if the frequency is high we expect  $X_C$  to be smaller than  $R$
- For the phasor for this circuit,  $I$  and  $V_R$  are in phase,  $V_C$  is  $90^\circ$  behind  $I$
- $v_R + v_C = \varepsilon$  (at any point in time), so draw the emf phasor as the vector sum of  $V_R$  and  $V_C$

◆  $\varepsilon = \varepsilon_0 \cos \omega t$



# Circuits with resistors and capacitors

- Calculate the current

$$\begin{aligned}\epsilon_o^2 &= V_R^2 + V_C^2 = (IR)^2 + (IX_C)^2 = (R^2 + X_C^2)I^2 \\ &= \left( R^2 + \frac{1}{\omega^2 C^2} \right) I^2\end{aligned}$$



- Thus, I can write the peak current as

$$I = \frac{\epsilon_o}{\sqrt{R^2 + X_C^2}} = \frac{\epsilon_o}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

- The peak voltages are

$$V_R = IR = \frac{\epsilon_o R}{\sqrt{R^2 + X_C^2}} = \frac{\epsilon_o R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$
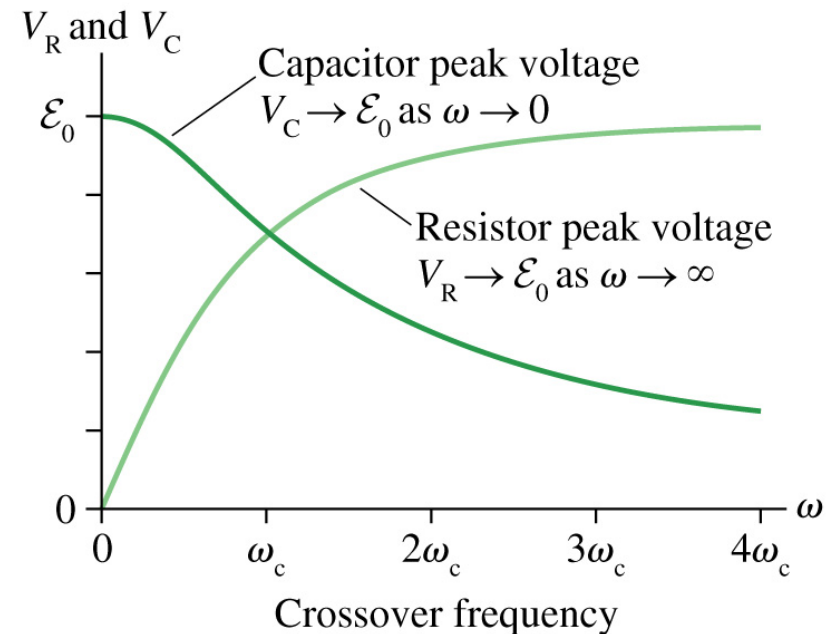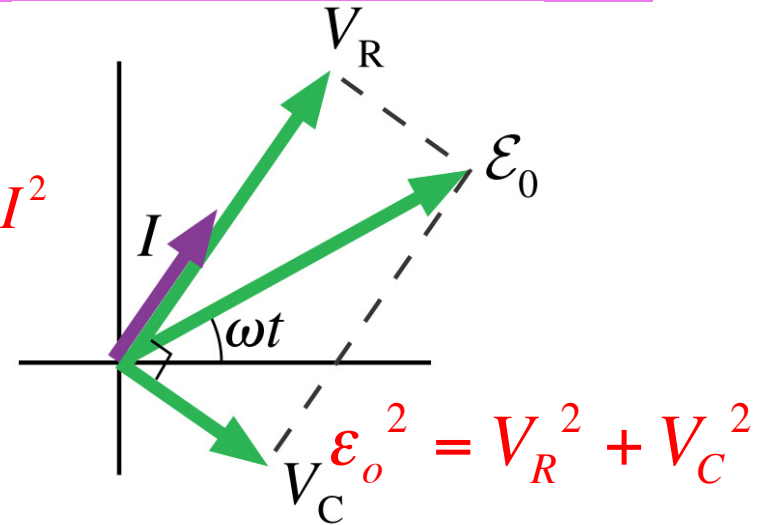
$$V_C = IX_C = \frac{\epsilon_o X_C}{\sqrt{R^2 + X_C^2}} = \frac{\epsilon_o X_C}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$






# iclicker

Does  $V_R + V_C = \mathcal{E}_0$ ?

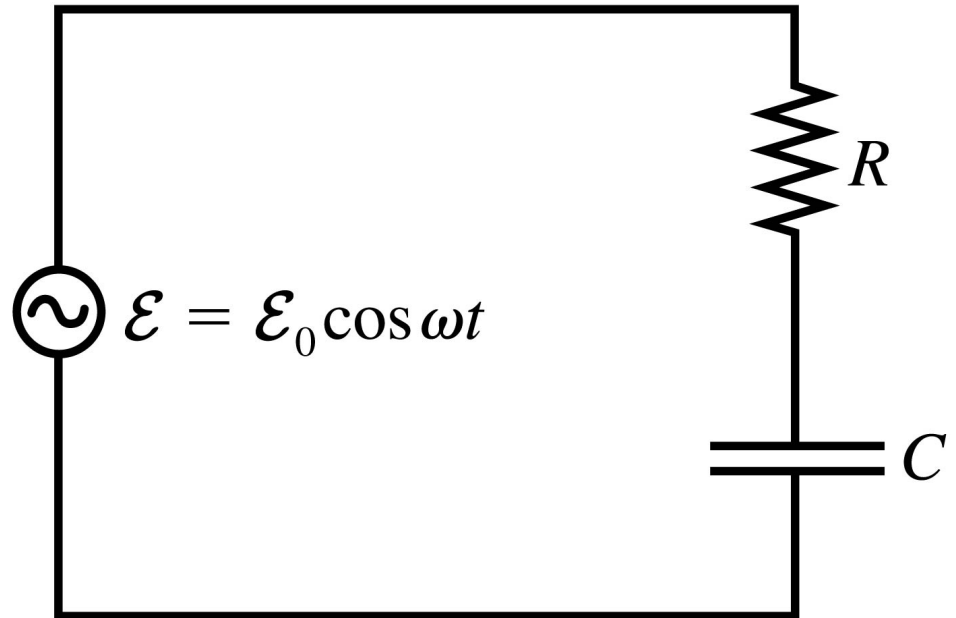
- A. Yes.
- B. No.
- C. Can't tell without knowing  $\omega$ .



# iclicker

Does  $V_R + V_C = \mathcal{E}_0$ ?

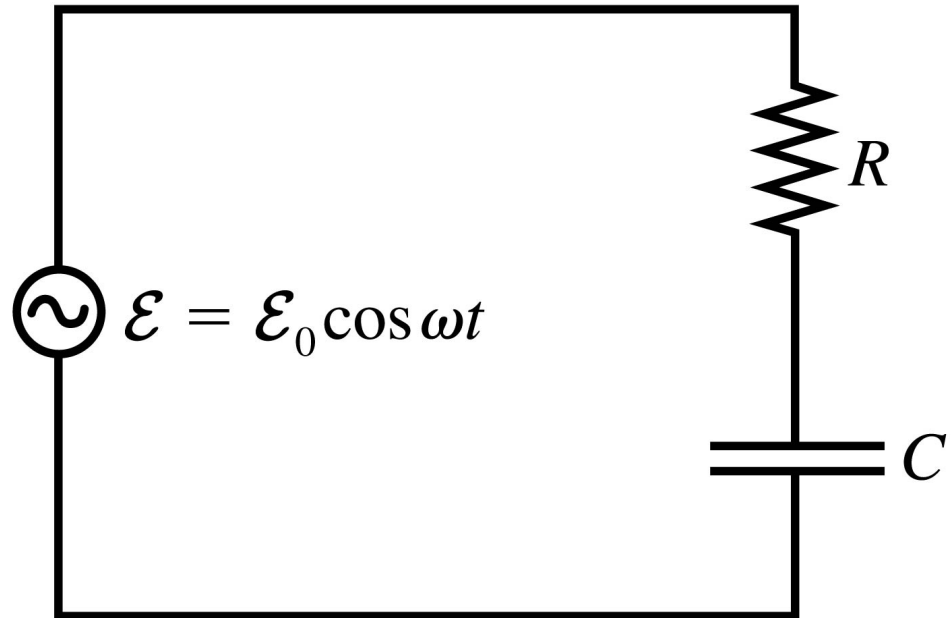- A. Yes.
- B. **No.**
- C. Can't tell without knowing  $\omega$  out knowing  $\omega$ .




Instantaneous voltages add.


Peak voltages don't because the voltages are not in phase.
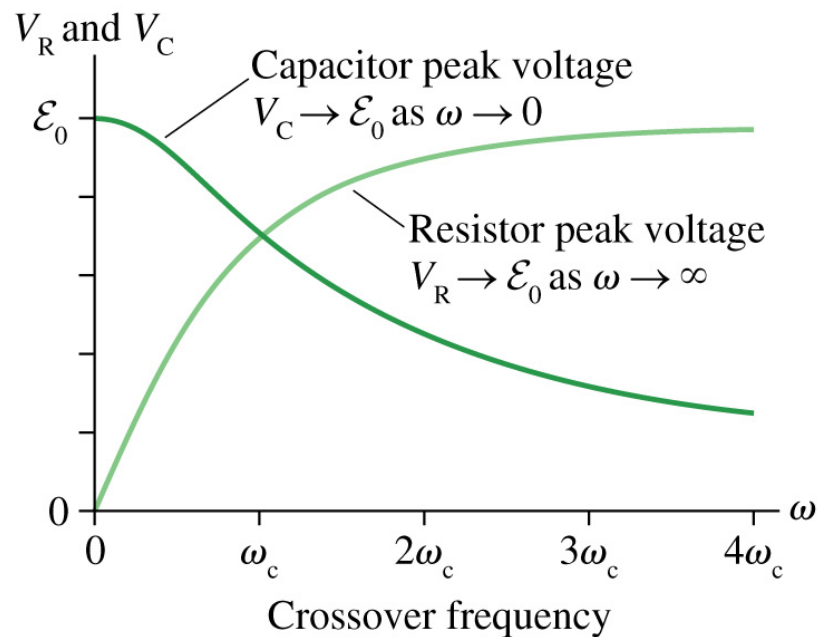
# Filters

- A low pass filter transmits a signal with a low frequency but blocks a signal with a high frequency
- And vice versa for a high pass filter




(a) Low-pass filter

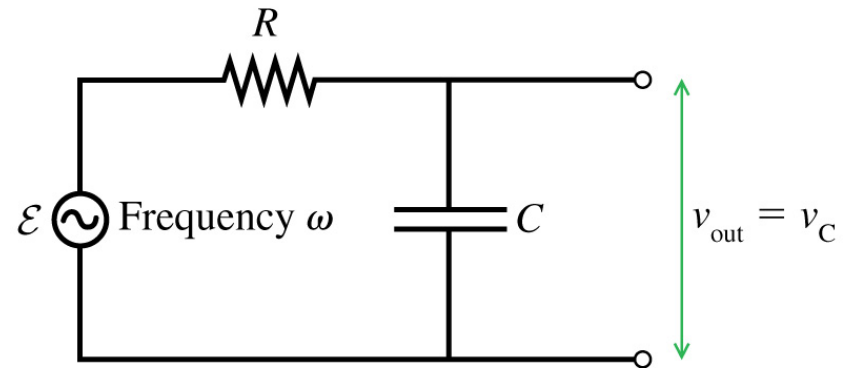

Transmits frequencies  $\omega < \omega_c$  and  
blocks frequencies  $\omega > \omega_c$ .

(b) High-pass filter

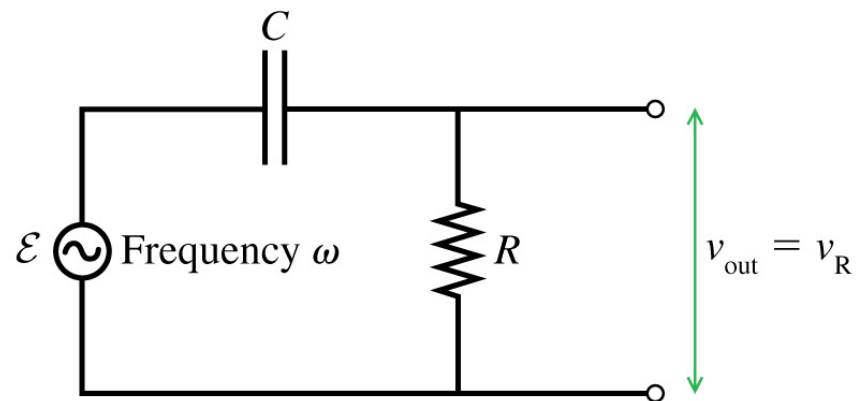

Transmits frequencies  $\omega > \omega_c$  and  
blocks frequencies  $\omega < \omega_c$ .