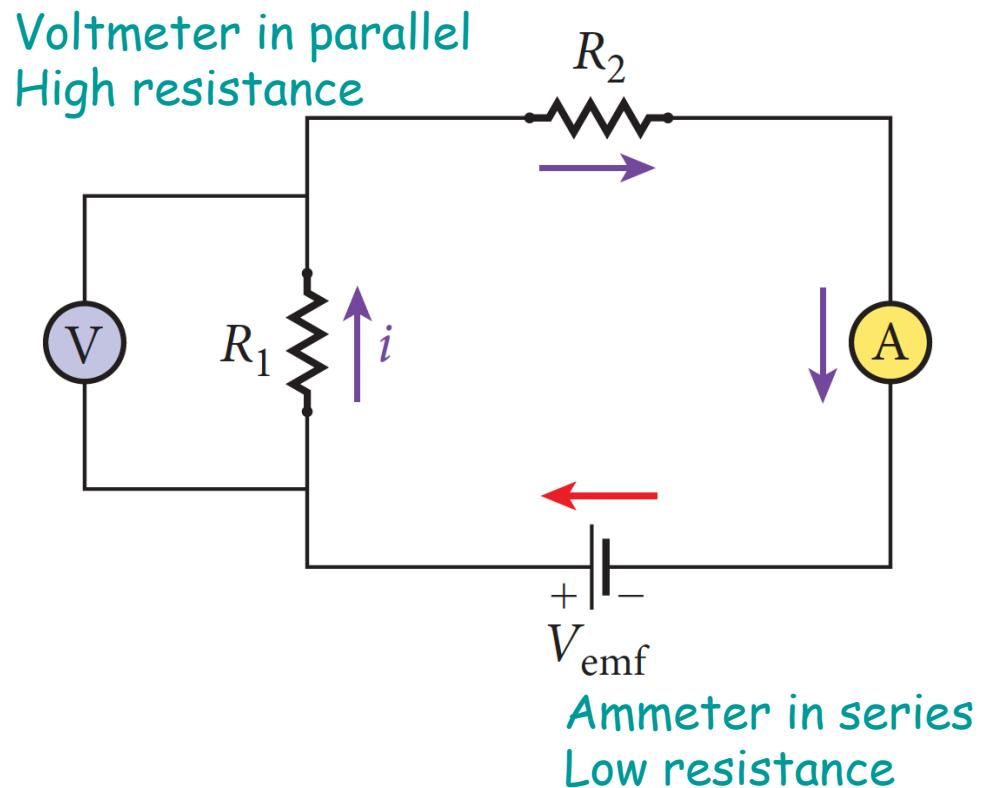




Direct Current Circuits

Ammeters and Voltmeters

- A device used to measure current is called an **ammeter**
- A device used to measure potential difference is called a **voltmeter**
- To measure the current, the ammeter must be placed in the circuit in *series*
- To measure the potential difference, the voltmeter must be wired in *parallel* with the component across which the potential difference is to be measured



Real-life Voltmeter in a Simple Circuit



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

- Consider a simple circuit consisting of a source of emf with potential difference $V_{\text{emf}} = 150. \text{ V}$ and a resistor with resistance $R = 100 \text{ k}\Omega$.
- A voltmeter with resistance $R_V = 10.0 \text{ M}\Omega$ is connected across the resistor.


PROBLEM 1:

- What is the current in the circuit before the voltmeter is connected?

SOLUTION 1:

- Ohm's Law allows us to calculate the current before:
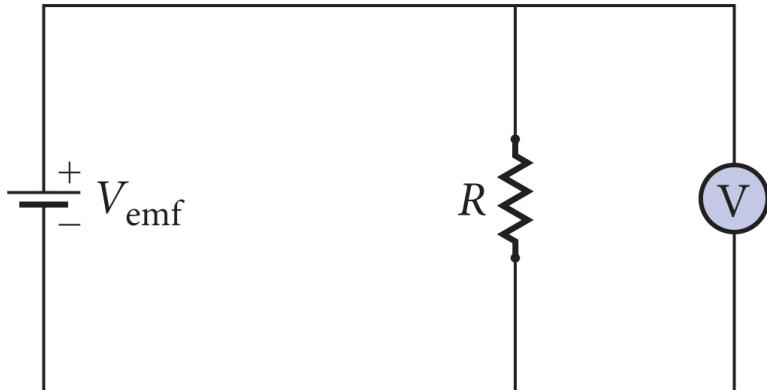
$$i = \frac{V_{\text{emf}}}{R} = \frac{150. \text{ V}}{100 \cdot 10^3 \Omega} = 1.50 \cdot 10^{-3} \text{ A} = 1.50 \text{ mA}$$



Real-life Voltmeter in a Simple Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

PROBLEM 2:

- What is the current in the circuit after the voltmeter is connected?


SOLUTION 2:

- The equivalent resistance of the resistor and the voltmeter connected in parallel is given by:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R} + \frac{1}{R_V}$$

- The equivalent resistance is:
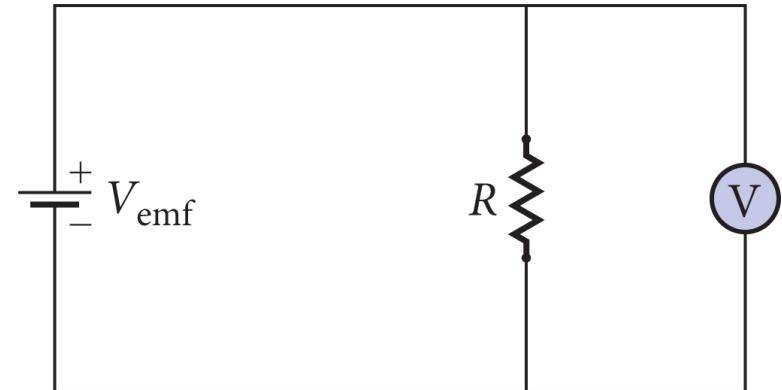
$$R_{\text{eq}} = \frac{R R_V}{R + R_V} = \frac{(100 \cdot 10^3 \Omega)(10.0 \cdot 10^6 \Omega)}{100 \cdot 10^3 \Omega + 10.0 \cdot 10^6 \Omega} = 9.90 \cdot 10^4 \Omega = 99.0 \text{ k}\Omega$$



Real-life Voltmeter in a Simple Circuit



- The current after connecting the voltmeter is:

$$i = \frac{V_{\text{emf}}}{R} = \frac{150. \text{ V}}{99.0 \cdot 10^4 \text{ } \Omega} = 1.52 \cdot 10^{-3} \text{ A} = 1.52 \text{ mA}$$

- So the current in the circuit increases by 0.02 mA, when the voltmeter is connected because the parallel combination of the resistor and the voltmeter has a lower resistance than that of the resistor alone.
- The effect is small.
- The larger the resistance of the voltmeter, the better.

RC Circuits




- So far we have dealt with circuits containing sources of emf and resistors
- The currents in these circuits did not vary in time
- Now we will study circuits that contain capacitors as well as sources of emf and resistors
- These **RC circuits** have currents that vary with time
- Consider a circuit with
 - a source of emf, V_{emf} ,
 - a resistor R ,
 - a capacitor C

Charging a Capacitor

- We start with the capacitor uncharged
- We close the switch and current begins to flow, building up opposite charges on the plates of the capacitor and creating a potential difference across the capacitor
- When the capacitor is fully charged, no more current flows
- The potential difference across the plates is equal to the potential difference provided by the source of emf
- The magnitude of the total charge on each plate is

$$q_{\text{tot}} = CV_{\text{emf}}$$

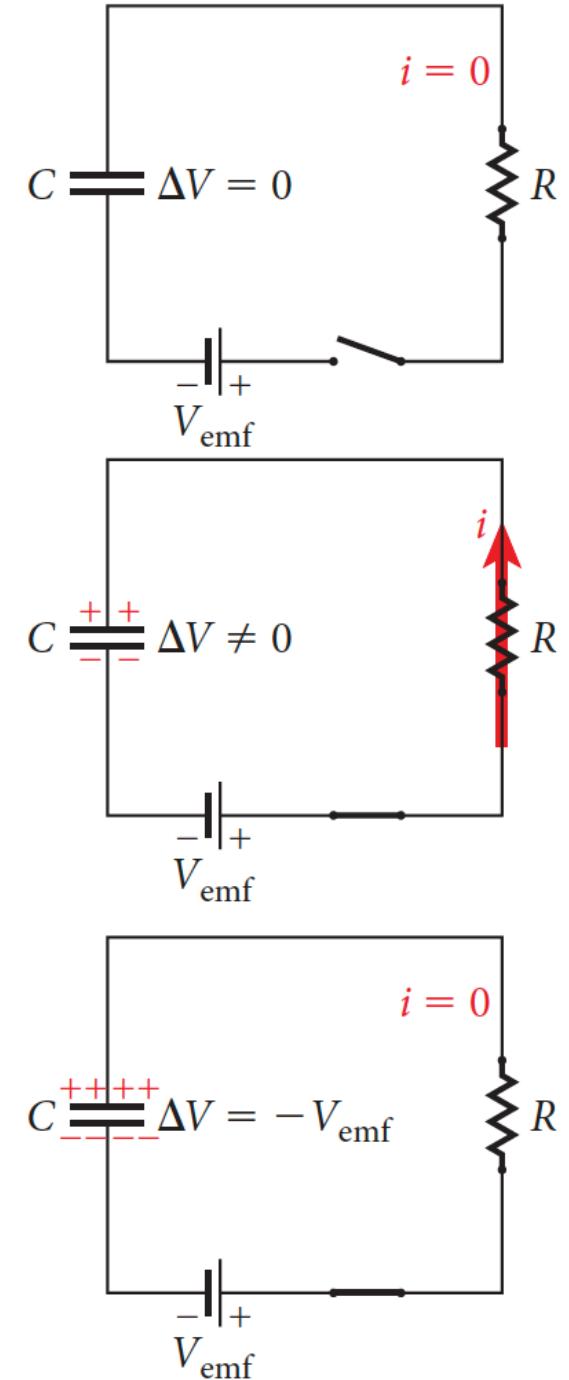

Charging a Capacitor

- While the capacitor is charging, we can analyze the current flowing by applying Kirchhoff's Loop Rule

$$V_{\text{emf}} - V_R - V_C = V_{\text{emf}} - i(t)R - \frac{q(t)}{C} = 0$$


- The change of the charge on the capacitor is the current

$$i(t) = \frac{dq(t)}{dt}$$

- We can rewrite our equation as

$$R \frac{dq(t)}{dt} + \frac{q(t)}{C} = V_{\text{emf}} \quad \text{or}$$
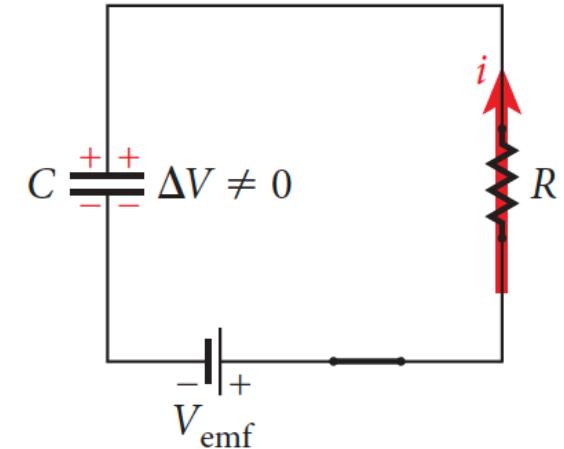
$$\frac{dq(t)}{dt} + \frac{q(t)}{RC} = \frac{V_{\text{emf}}}{R} \quad \text{Differential equation relating } q \text{ and } \frac{dq}{dt}$$



The term V_c is negative since the top plate of the capacitor is connected to the positive - higher potential - terminal of the battery. Thus analyzing counter-clockwise leads to a drop in voltage across the capacitor!



Charging a Capacitor

- The solution for this differential equation is

$$q(t) = q_{\max} \left(1 - e^{-\frac{t}{\tau}} \right)$$

- The constant τ is the **time constant** given by
$$\tau = RC$$
- The constant q_{\max} is given by

$$q_{\max} = CV_{\text{emf}}$$

- So we can write the solution to our differential equation

$$q(t) = CV_{\text{emf}} \left(1 - e^{-\frac{t}{RC}} \right)$$

Math Reminder: $\frac{d}{dx} e^{ax} = a \cdot e^{ax}$

Charging a Capacitor

- At $t = 0$ we have

$$q(0) = CV_{\text{emf}} \left(1 - e^{-\frac{0}{RC}} \right) = 0$$

- At $t = \infty$ we have

$$q(\infty) = CV_{\text{emf}} \left(1 - e^{-\frac{\infty}{RC}} \right) = CV_{\text{emf}}$$

- The current flowing through the circuit is the time derivative of the charge

$$i(t) = \frac{dq(t)}{dt} = \left(\frac{V_{\text{emf}}}{R} \right) e^{-\frac{t}{RC}}$$


- At $t = 0$ we have

$$i(0) = \frac{V_{\text{emf}}}{R}$$

- At $t = \infty$ we have

$$i(\infty) = \left(\frac{V_{\text{emf}}}{R} \right) e^{-\frac{\infty}{RC}} = 0$$



Charging a Capacitor

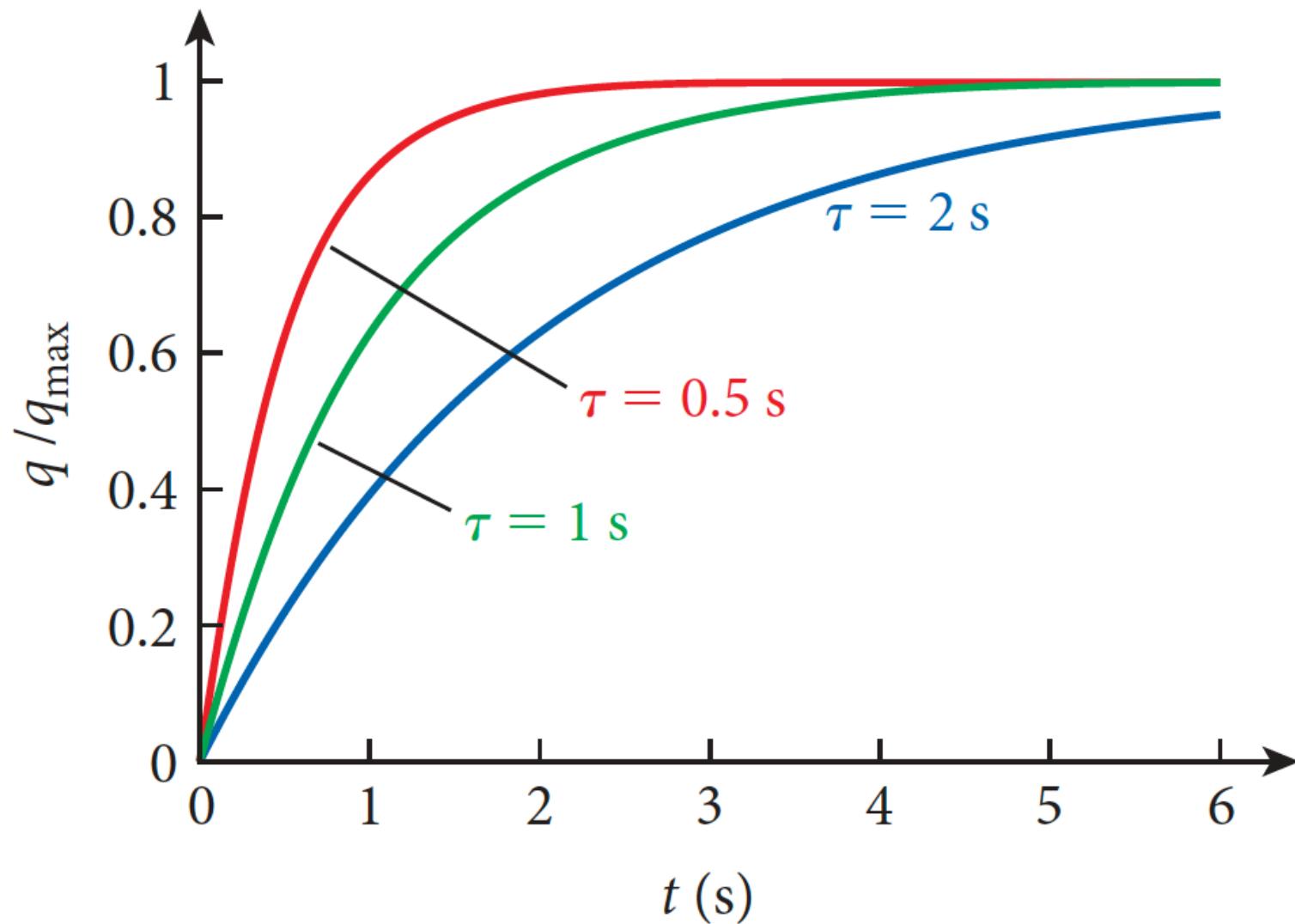

Discharging a Capacitor

- Now we consider a circuit containing only one resistor and a fully charged capacitor
- The charge on the capacitor is q_{\max}
- Now we short the resistor across the capacitor by moving the switch from position 1 to position 2
- Current flows until the capacitor is completely discharged
- While the capacitor is discharging, Kirchhoff's Loop Rule gives us
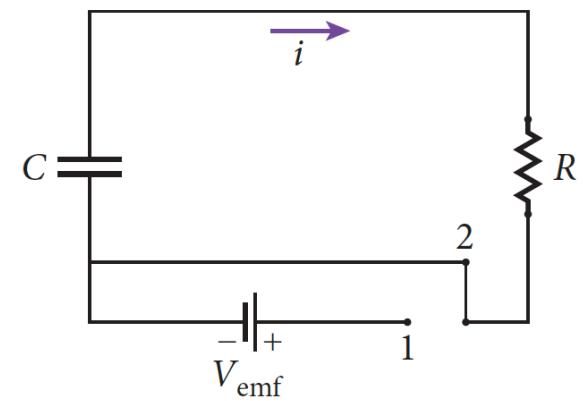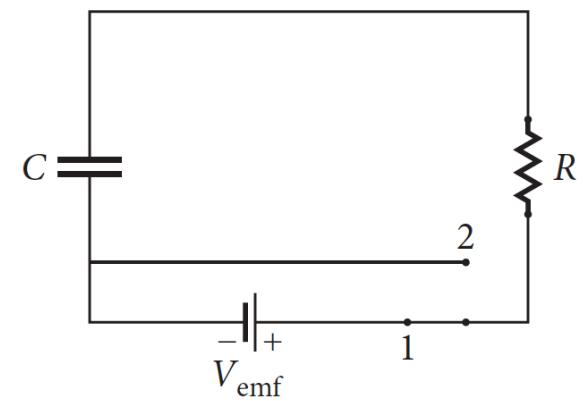
$$-i(t)R - V_C = -i(t)R - \frac{q(t)}{C} = 0$$



Discharging a Capacitor

- Using the definition of current, we can rewrite our equation as

$$R \frac{dq(t)}{dt} + \frac{q(t)}{C} = 0$$

- The solution to this differential equation is


$$q(t) = q_{\max} e^{-\frac{t}{RC}}$$

- At $t = 0$ we have

$$q(0) = q_{\max} e^{-\frac{0}{RC}} = q_{\max}$$

- At $t = \infty$ we have
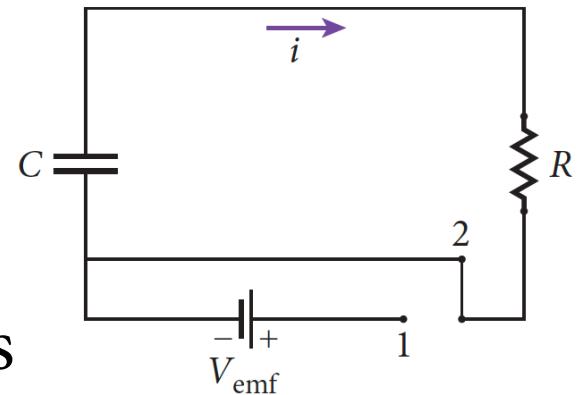
$$q(\infty) = q_{\max} e^{-\frac{\infty}{RC}} = 0$$





Discharging a Capacitor

- The current flowing through the circuit is the time derivative of the charge

$$i(t) = \frac{dq(t)}{dt} = -\frac{(q_{\max})}{RC} e^{-\frac{t}{RC}}$$


- At $t = 0$ we have

$$i(0) = -\frac{(q_{\max})}{RC} e^{-\frac{0}{RC}} = -\frac{(q_{\max})}{RC}$$

- At $t = \infty$ we have

$$i(t) = -\frac{(q_{\max})}{RC} e^{-\frac{\infty}{RC}} = 0$$

Discharging a Capacitor

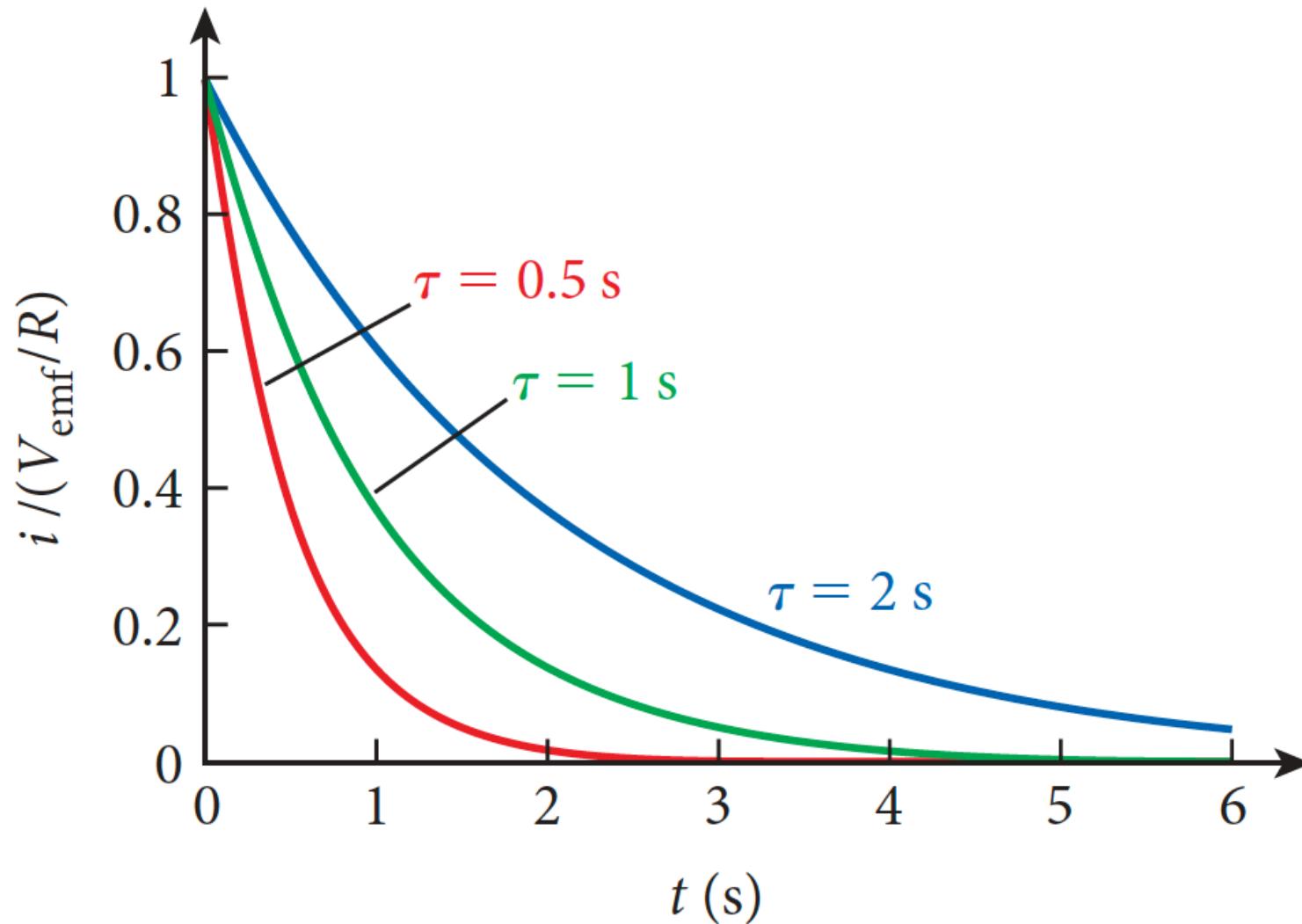



Time Required to charge a Capacitor

- Consider a circuit consisting of a 12.0 V battery, a 50.0 Ω resistor, and a 100.0 μF capacitor wired in series
- The capacitor is initially completely discharged
- **PROBLEM**
- How long after the circuit is closed will it take to charge the capacitor to 90% of its maximum charge?

SOLUTION

- The charge on the capacitor as a function of time is given by

$$q(t) = q_{\max} \left(1 - e^{-\frac{t}{RC}} \right)$$

Time Required to charge a Capacitor

- We want to know the time until $q(t)/q_{\max} = 0.90$

$$\left(1 - e^{-\frac{t}{RC}}\right) = \frac{q(t)}{q_{\max}} = 0.90 \quad \Rightarrow \quad 0.10 = e^{-\frac{t}{RC}}$$

- Taking the natural log of both sides gives us

$$\ln(0.10) = \ln\left(e^{-\frac{t}{RC}}\right) \quad \Rightarrow \quad \ln(0.10) = -\frac{t}{RC}$$

- So the time to discharge the capacitor to 90% of its maximum charge is

$$t = -RC\ln(0.10) = -(50.0 \Omega)(100.0 \cdot 10^{-6} \text{ F})(-2.30)$$

$$t = 0.0115 \text{ s} = 11.5 \text{ ms}$$


Math Reminder: $\ln(e^x) = x$

Summary: RC Circuit

- Charging a capacitor:

$$q(t) = q_0 \left(1 - e^{-\frac{t}{\tau}} \right)$$

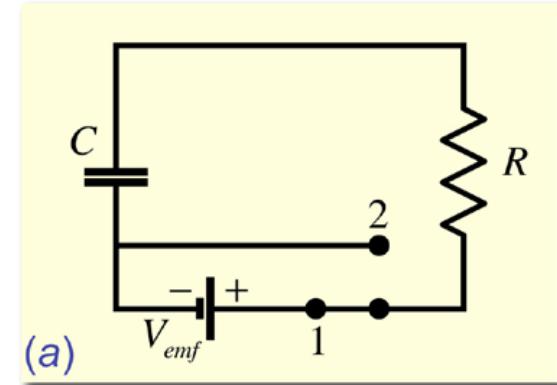
$$i = \frac{dq}{dt} = \left(\frac{V_{emf}}{R} \right) e^{\left(-\frac{t}{RC} \right)}$$



- Discharging a capacitor:

$$q = q_0 e^{\left(-\frac{t}{RC} \right)}$$
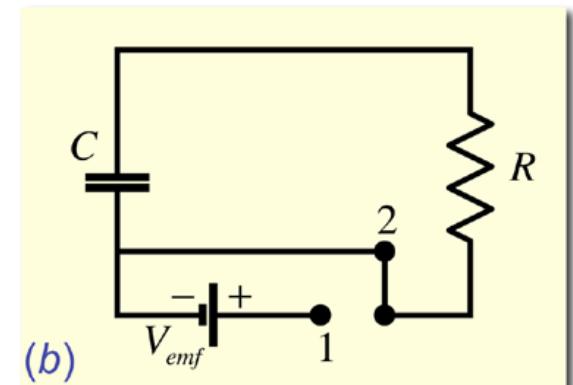
$$i = \frac{dq}{dt} = \left(\frac{q_0}{RC} \right) e^{\left(-\frac{t}{RC} \right)}$$



- Time constant:

$$\tau = RC$$

Rate of Energy Storage in a Capacitor



- A resistor with $R = 2.50 \text{ M}\Omega$ and a capacitor with $C = 1.25 \mu\text{F}$ are connected in series with a battery for which $V_{\text{emf}} = 12.0 \text{ V}$
- At $t = 2.50 \text{ s}$ after the circuit is closed, what is the rate at which energy is being stored in the capacitor?

SOLUTION

THINK


- When the circuit is closed, the capacitor begins to charge
- The rate at which energy is stored in the capacitor is given by the time derivative of the amount of energy stored in the capacitor, which is a function of the charge on the capacitor

Rate of Energy Storage in a Capacitor



SKETCH

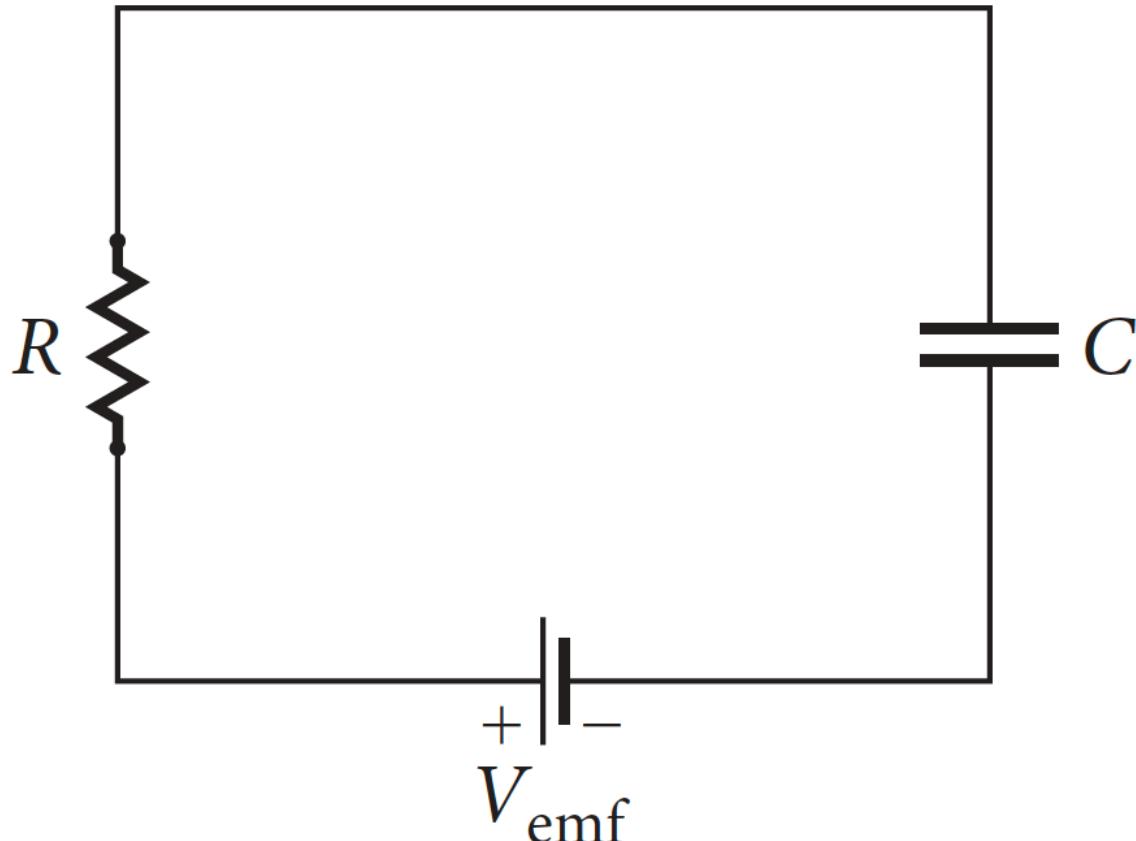- The circuit contains a battery, a resistor, and a capacitor in series.





RESEARCH

Rate of Energy Storage in a Capacitor

- The charge on the capacitor as a function of time is

$$q(t) = CV_{\text{emf}} \left(1 - e^{-\frac{t}{RC}} \right)$$

- The energy stored in a capacitor with charge q is

$$U = \frac{1}{2} \frac{q^2}{C}$$

- The time derivative of the stored energy is

$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{1}{2} \frac{q^2}{C} \right) = \frac{q(t)}{C} \frac{dq(t)}{dt}$$

- The time derivative of the charge is the current

$$i(t) = \frac{dq(t)}{dt} = \left(\frac{V_{\text{emf}}}{R} \right) e^{-\frac{t}{RC}}$$



Rate of Energy Storage in a Capacitor

SIMPLIFY

- Combining our equations

$$\frac{dU}{dt} = \frac{q(t)}{C} i(t) = \frac{CV_{\text{emf}} \left(1 - e^{-\frac{t}{RC}} \right)}{C} \left(\frac{V_{\text{emf}}}{R} \right) e^{-\frac{t}{RC}}$$

$$\frac{dU}{dt} = \frac{V_{\text{emf}}^2}{R} e^{-\frac{t}{RC}} \left(1 - e^{-\frac{t}{RC}} \right)$$

CALCULATE

- We first calculate the time constant

$$RC = (2.50 \cdot 10^6 \Omega)(1.25 \cdot 10^{-6} \text{ F}) = 3.125 \text{ s}$$



Rate of Energy Storage in a Capacitor

- Now we calculate the rate of change of energy stored in the capacitor

$$\frac{dU}{dt} = \frac{(12.0 \text{ V})^2}{2.50 \cdot 10^6 \Omega} e^{-\frac{2.50 \text{ s}}{3.125 \text{ s}}} \left(1 - e^{-\frac{2.50 \text{ s}}{3.125 \text{ s}}} \right) = 1.425 \cdot 10^{-5} \text{ W}$$

DOUBLE-CHECK (Energy Conservation)

- The current at $t = 2.50$ is

$$i(t) = \left(\frac{12.0 \text{ V}}{2.50 \cdot 10^6 \Omega} \right) e^{-\frac{2.50 \text{ s}}{3.125 \text{ s}}} = 2.16 \cdot 10^{-6} \text{ A}$$



Rate of Energy Storage in a Capacitor

- The rate of energy dissipation at $t = 2.50$ is

$$P = \frac{dU}{dt} = i^2 R = (2.16 \cdot 10^{-6} \text{ A})^2 (2.50 \cdot 10^6 \text{ } \Omega) = 1.16 \cdot 10^{-5} \text{ W}$$

- The rate at which the battery delivers energy to the circuit at $t = 2.50$ s is

$$P = \frac{dU}{dt} = iV_{\text{emf}} = (2.16 \cdot 10^{-6} \text{ A})(12.0 \text{ V}) = 2.59 \cdot 10^{-5} \text{ W}$$

- The energy supplied by the battery is equal to the sum of the energy dissipated in the resistor plus the energy stored in the capacitor