



Direct Current Circuits


Resistors in series and in parallel



- Resistors in series:

Replace two resistors in series by one resistor with equivalent resistance

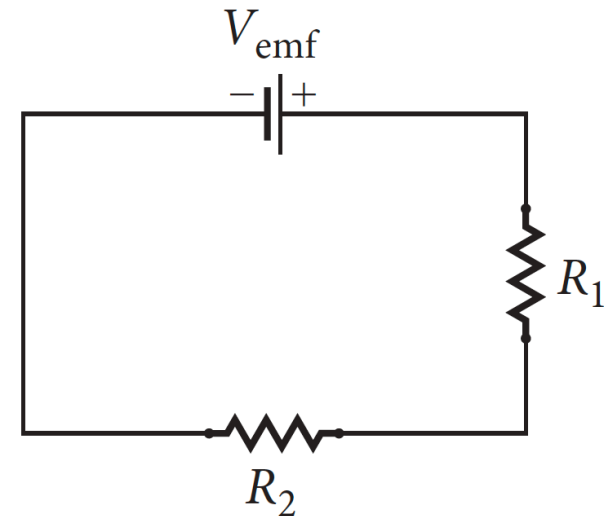
$$R_{\text{eq}} = R_1 + R_2 \quad R_{\text{eq}} = \sum_{i=1}^n R_i$$



- Resistors in parallel:

Replace two resistors in parallel by one resistor with equivalent resistance
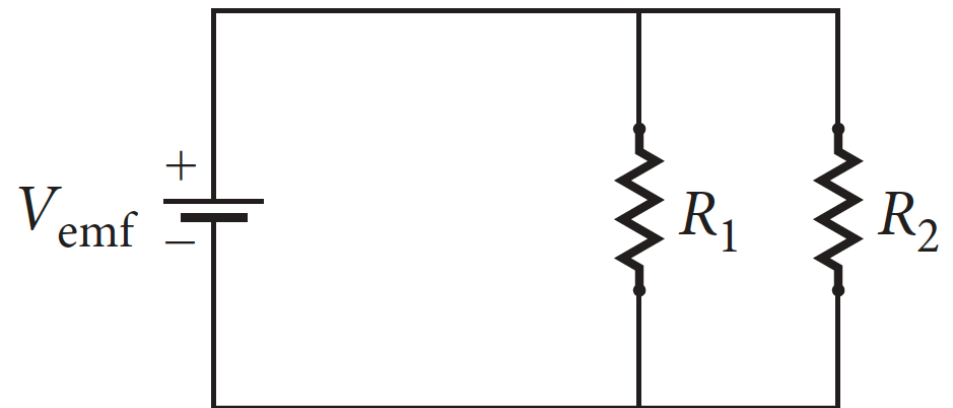
$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} \quad \frac{1}{R_{\text{eq}}} = \sum_{i=1}^n \frac{1}{R_i}$$



Energy and Power in Electric Circuits



- Energy in a circuit is given by

$$dU = dq\Delta V \quad \text{or} \quad dU = idt\Delta V$$

- Power is $P = dU / dt$, thus electric power is

$$P = i\Delta V = i^2 R = \frac{(\Delta V)^2}{R}$$

- i.e. power loss in a resistor is voltage drop across the resistor multiplied by current through the resistor
- The unit of power is the Watt (W)
- $1 \text{ W} = 1 \text{ A V} = 1 \text{ V}^2/\Omega = 1 \text{ A}^2\Omega$
- Thus energy is also in units of $1 \text{ J} = 1 \text{ W s}$

Circuits

- So far, simple circuits with one emf device only.
- Capacitors wired in parallel

$$C_{\text{eq}} = \sum_{i=1}^n C_i$$

- Capacitors wired in series

$$\frac{1}{C_{\text{eq}}} = \sum_{i=1}^n \frac{1}{C_i}$$

- Resistors wired in parallel

$$\frac{1}{R_{\text{eq}}} = \sum_{i=1}^n \frac{1}{R_i}$$



- Resistors wired in series

$$R_{\text{eq}} = \sum_{i=1}^n R_i$$

Complex Circuits



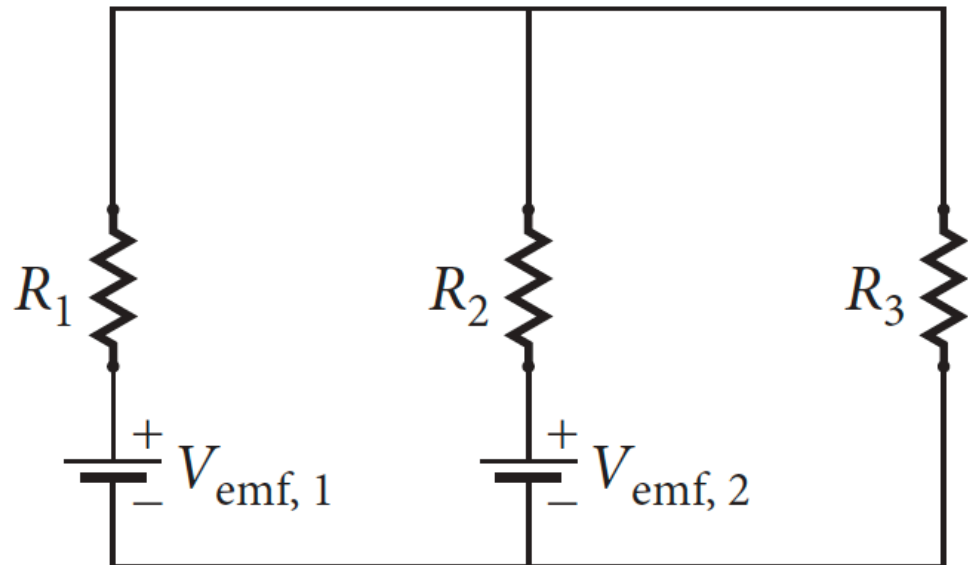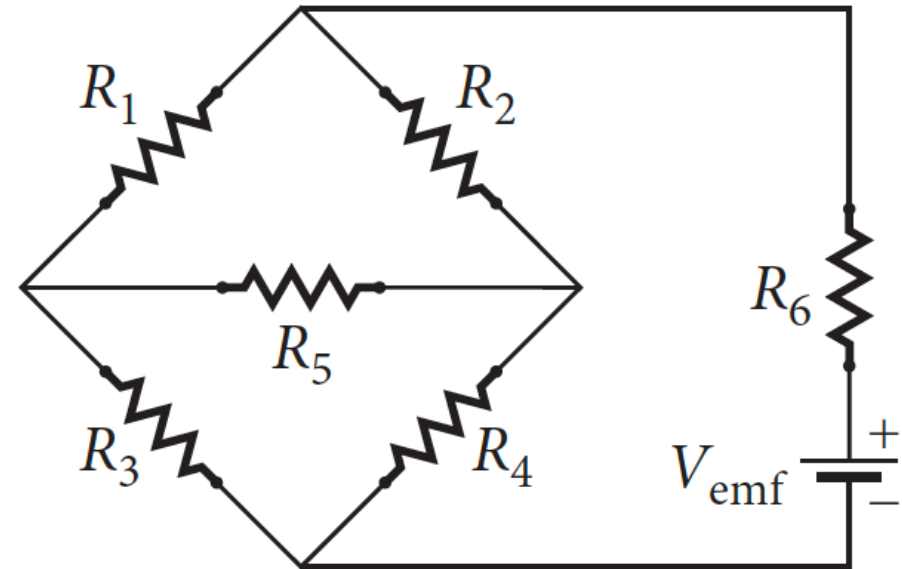- Some circuits cannot be resolved into series or parallel systems of capacitors or resistors and contain more than one source of emf.
- To handle these types of circuits, we will apply **Kirchhoff's Rules**



Kirchhoff's Junction Rule



- A **junction** is a place in a circuit where three or more wires are connected to each other
- Each connection between two junctions in a circuit is called a **branch**
- A branch can contain any number of different circuit elements and the wires between them
- Each branch can have a current flowing, and this current is the same everywhere in the branch
- This leads to Kirchhoff's Junction Rule:


The sum of the currents entering a junction must equal the sum of the currents leaving the junction.

Kirchhoff's Junction Rule

- We assign a positive sign to currents entering the junction and a negative sign to currents exiting the junction: Kirchhoff's Junction Rule is then

$$\text{Junction: } \sum_{k=1}^n i_k = 0$$

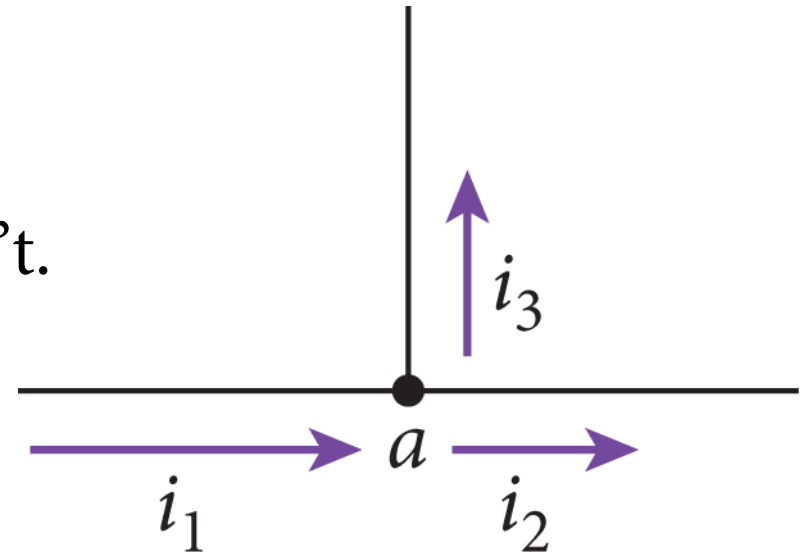
- Consider junction a , how do we know which currents enter and exit a junction? We don't.
- Simply assign a direction for each current
- If the assigned direction is wrong, we will get a negative number for that particular current.



Kirchhoff's Junction Rule


- Kirchhoff's Junction Rule is a direct consequence of the **conservation of electric charge**
- Junctions do not have the capability of storing charge
- Thus, charge conservation requires that all charges streaming into a junction also leave the junction
- At each junction in a multiloop circuit, the current flowing into must equal the current flowing out of the junction
- Example: Single junction, a , with a current, i_1 , entering and two currents, i_2 and i_3 , leaving the junction
- In this case,
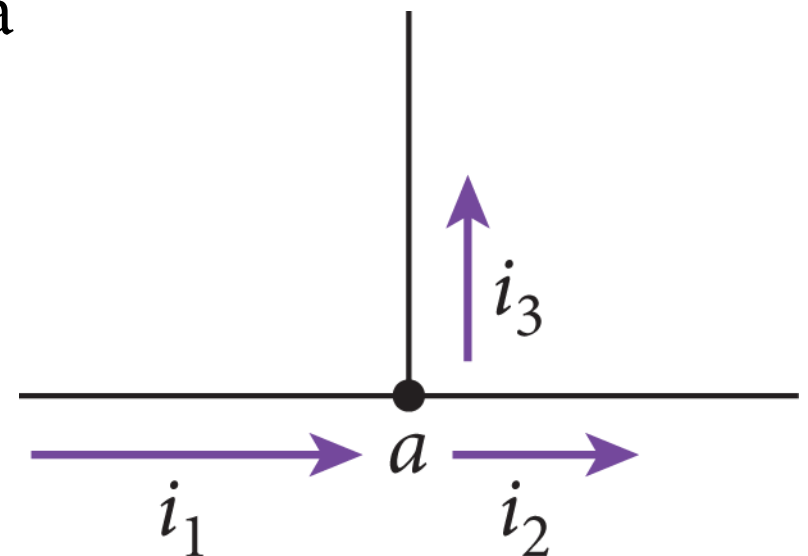
$$\sum_{k=1}^3 i_k = i_1 - i_2 - i_3 = 0 \Rightarrow i_1 = i_2 + i_3$$



Kirchhoff's Loop Rule

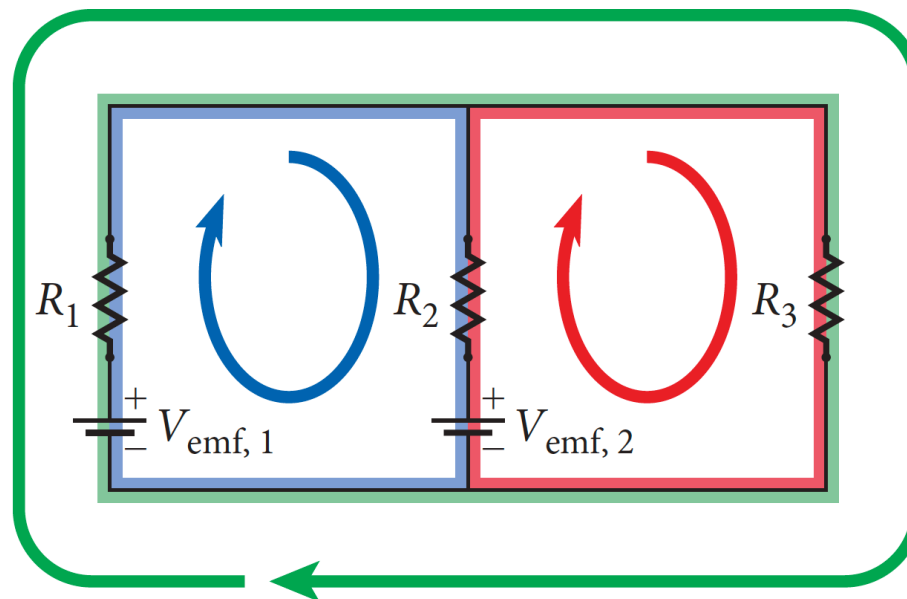- A loop in a circuit is any set of connected wires and circuit elements forming a closed path
- If you follow a loop, eventually you will get to the same point from which you started
- For example, in the circuit diagram shown below, three possible loops can be identified





Kirchhoff's Loop Rule

- You can move through any loop in a circuit in either a clockwise or a counterclockwise direction
- The direction of the path taken around the loop is irrelevant as long as your choice is followed consistently all the way around the loop!
- Summing the potential differences from all circuit elements encountered along any given loop yields the total potential difference of the complete path along the loop.
- **Kirchhoff's Loop Rule** then states:

The potential difference around a complete circuit loop must sum to zero.

Kirchhoff's Loop Rule




- Kirchhoff's Loop Rule is a direct consequence of the concept of electric potential
- This means that the electric potential energy of a conduction electron at a point in the circuit has one specific value
- Kirchhoff's Loop Rule is simply a consequence of the law of conservation of energy
- Application of Kirchhoff's Loop Rule requires conventions for determining the potential drop across each element of the circuit
- This depends on the assumed direction of the current and the direction of the analysis

Sign Convention for Potential Changes




Element	Direction of Analysis	Potential Change	
R	Same as current	$-iR$	(a)
R	Opposite to current	$+iR$	(b)
V_{emf}	Same as emf	$+V_{emf}$	(c)
V_{emf}	Opposite to emf	$-V_{emf}$	(d)

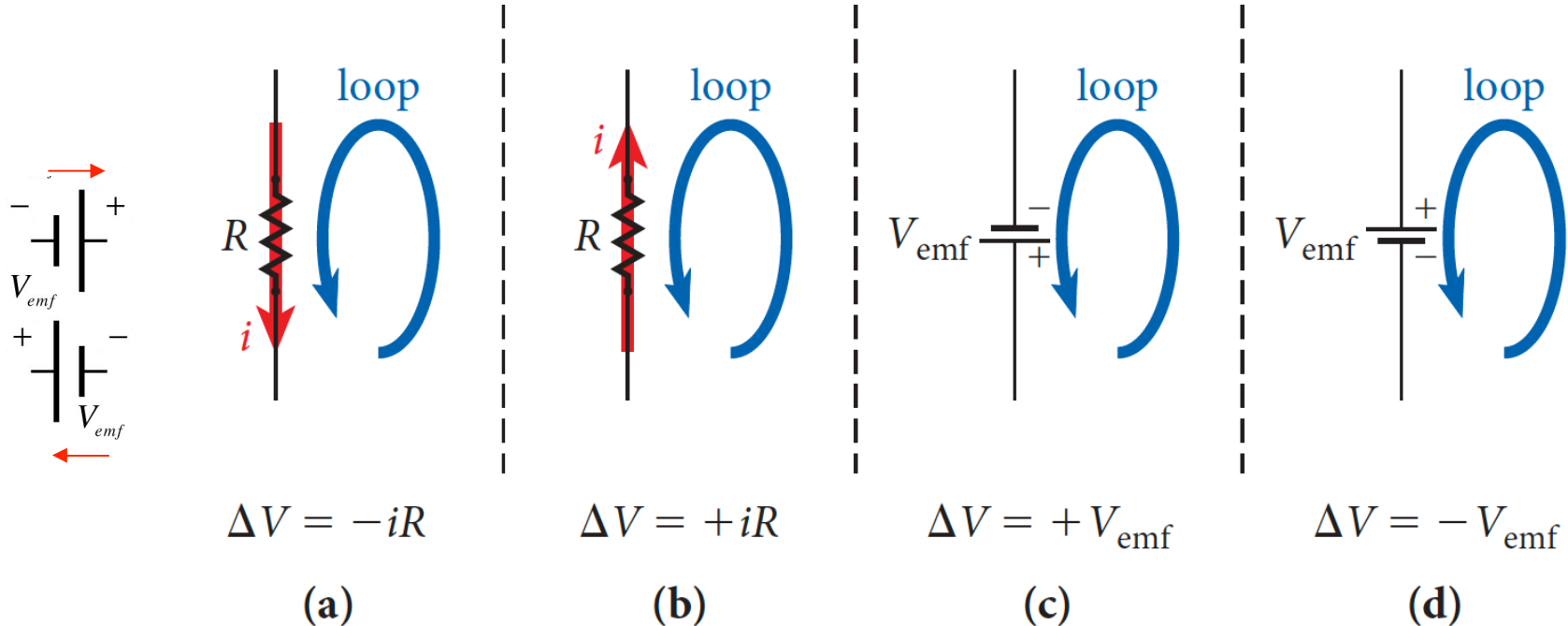

Kirchhoff's Loop Rule

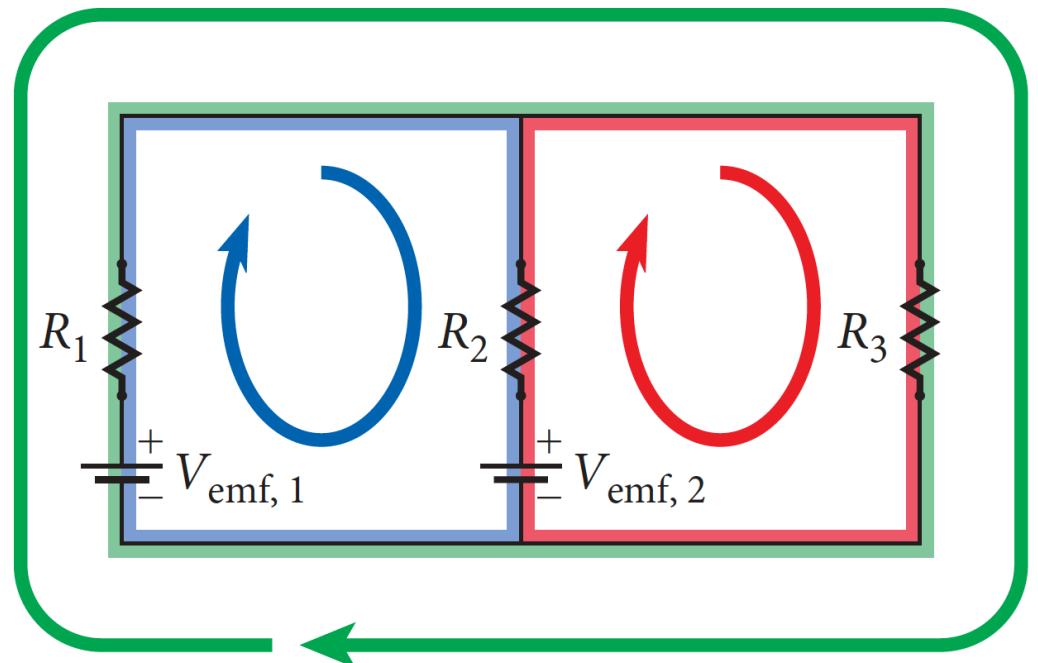- The potential difference around a complete circuit loop must sum to zero.
- A loop in a circuit is any set of connected wires and circuit elements forming a closed path.
- The sign for voltage sources and resistors depends on the analysis direction and the current direction




Kirchhoff's Loop Rule

- The potential difference around a complete circuit loop must sum to zero.
- A loop in a circuit is any set of connected wires and circuit elements forming a closed path.
- The sign for voltage sources and resistors depends on the analysis direction and the current direction


$$V_{emf,1} - i_1 R_1 + i_3 R_2 - V_{emf,2} = 0$$

$$V_{emf,2} - i_3 R_2 - i_2 R_3 = 0$$

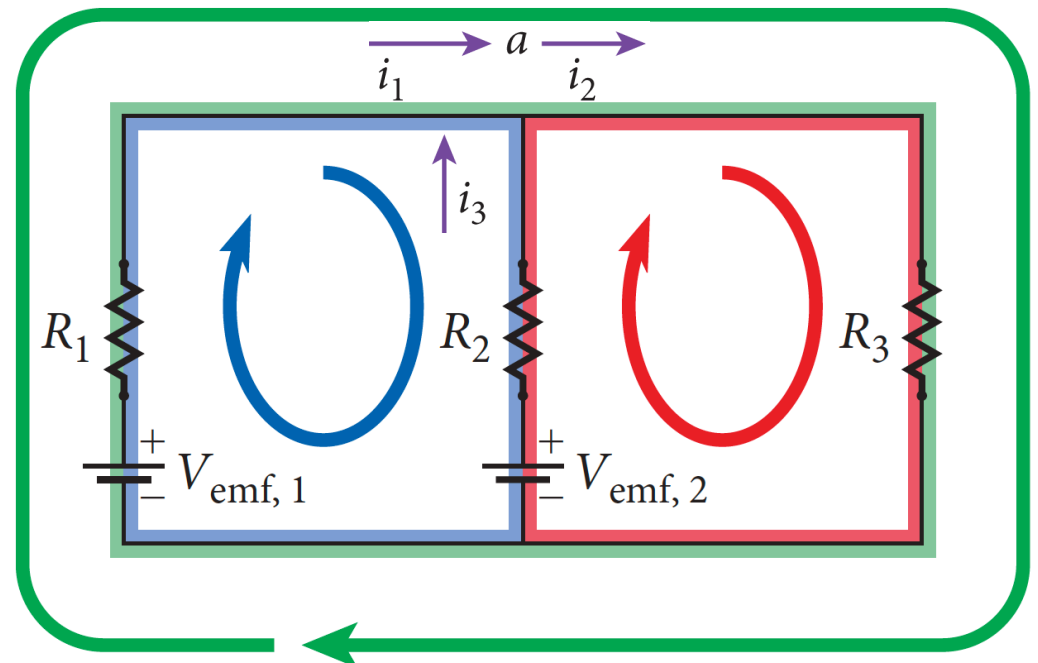


Kirchhoff's Loop Rule


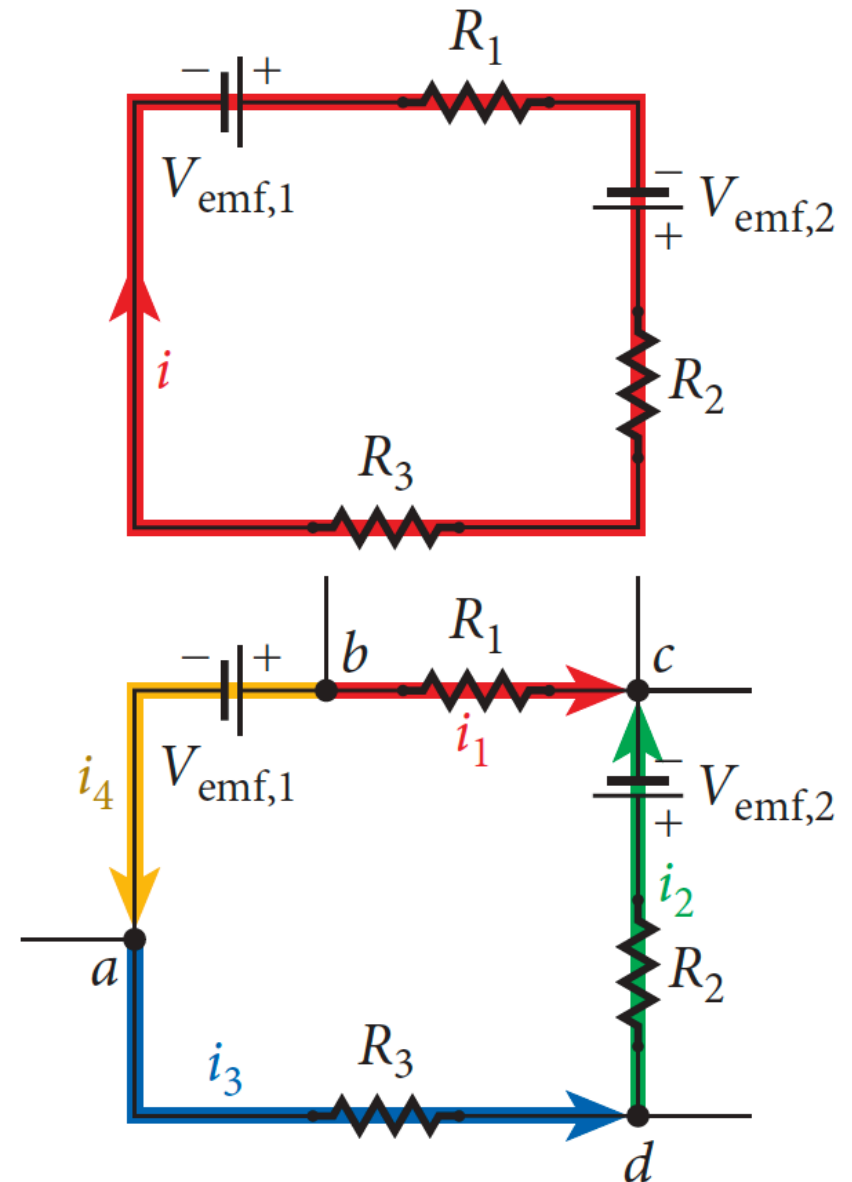
- Let's look at the previous circuit in a standard representation as a single isolated loop
- The current is the same everywhere in the loop
- Now break the loop up into four branches with four junctions, each of which can have a different current flowing through it
- Kirchhoff's Loop Rule still holds



Single-Loop Circuits

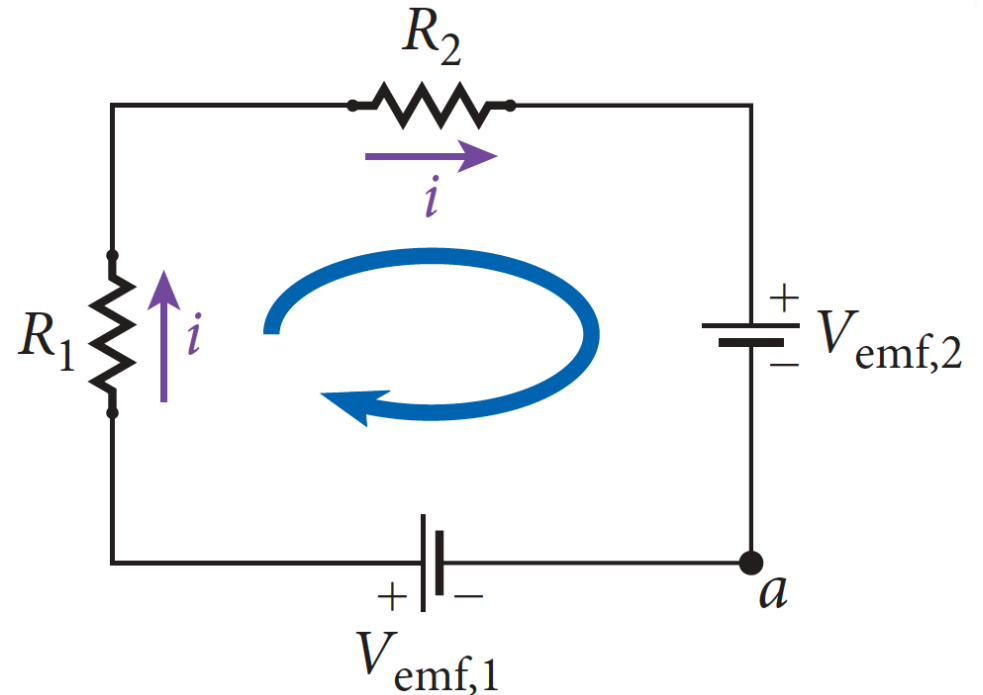- Consider a circuit containing two sources of emf and two resistors connected in series in a single loop
- There are no junctions so entire circuit consists of one branch
- The current is the same everywhere in the loop as illustrated by the purple arrow



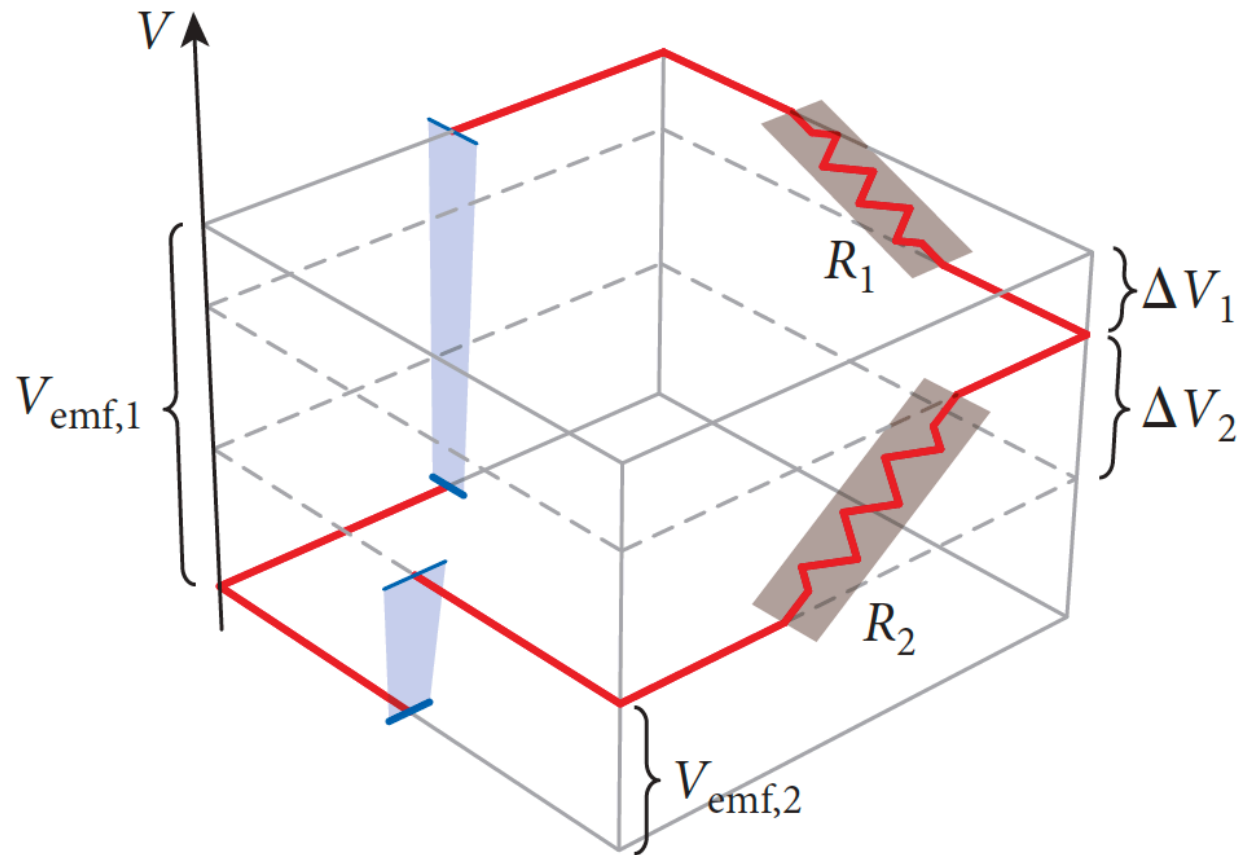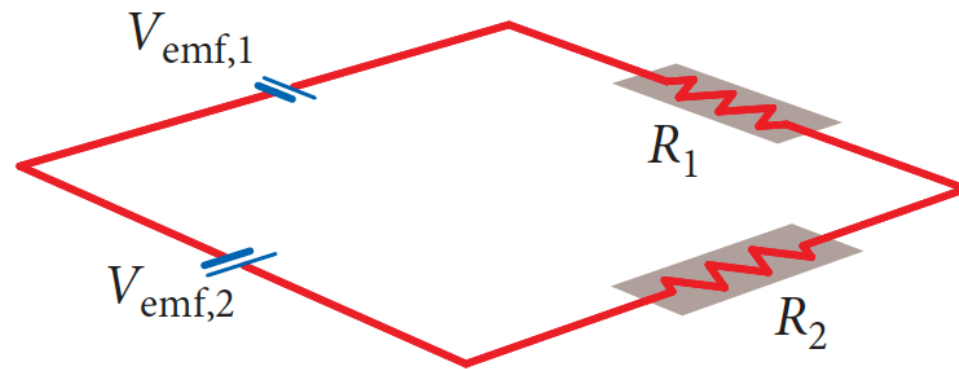


Analysis of Single-loop Circuits



- Choose a direction for the current
- We can determine if our assumption for the direction of the current is correct after the analysis is complete
- Resulting current positive
 - Current is flowing in the same direction as we had chosen
- Resulting current negative
 - Current is flowing in the direction opposite to what we had chosen
- We can choose the direction in which we analyze the circuit
 - Any direction we choose will give us the same information

Single-Loop Circuits

- Let's start at point a and move around the loop in a clockwise direction
- The first component is $V_{\text{emf},1}$, which produces a positive potential gain of $V_{\text{emf},1}$
- Next is resistor R_1 which produces a potential drop given by $-\Delta V_1 = iR_1$
- The next component is resistor R_2 , which produces a potential drop given by $-\Delta V_2 = iR_2$
- Next we encounter a second source of emf, $V_{\text{emf},2}$, which produces a potential drop rather than a potential gain

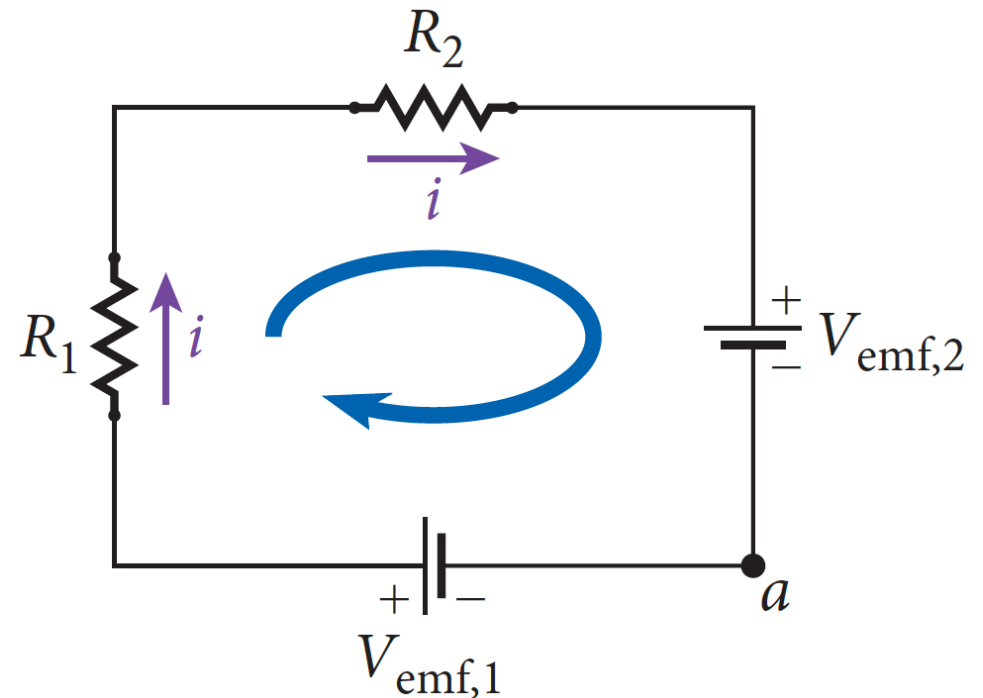

Single-Loop Circuits

- We sum the potential changes around the loop



$$V_{\text{emf},1} - \Delta V_1 - \Delta V_2 - V_{\text{emf},2} = 0 \Rightarrow$$

$$V_{\text{emf},1} - iR_1 - iR_2 - V_{\text{emf},2} = 0$$

- Now let's analyze the loop by going around the loop in the opposite direction

$$+V_{\text{emf},2} + iR_2 + iR_1 - V_{\text{emf},1} = 0$$

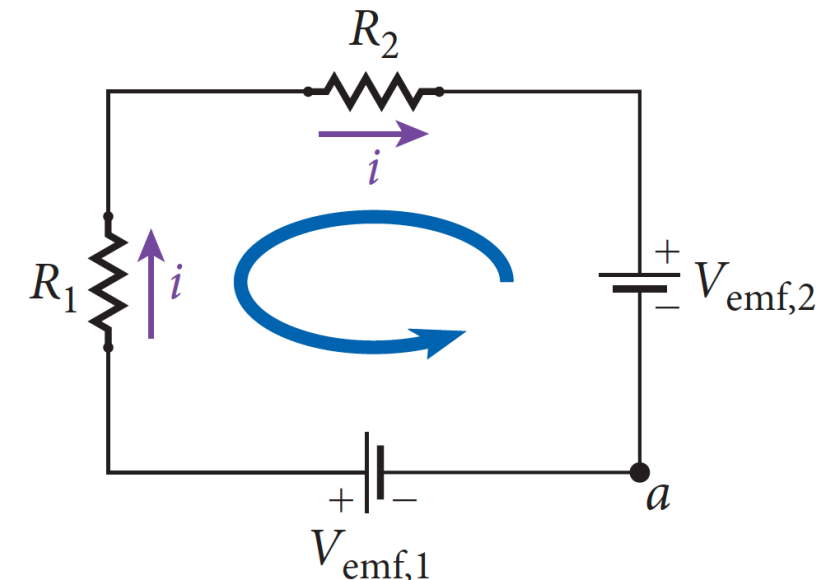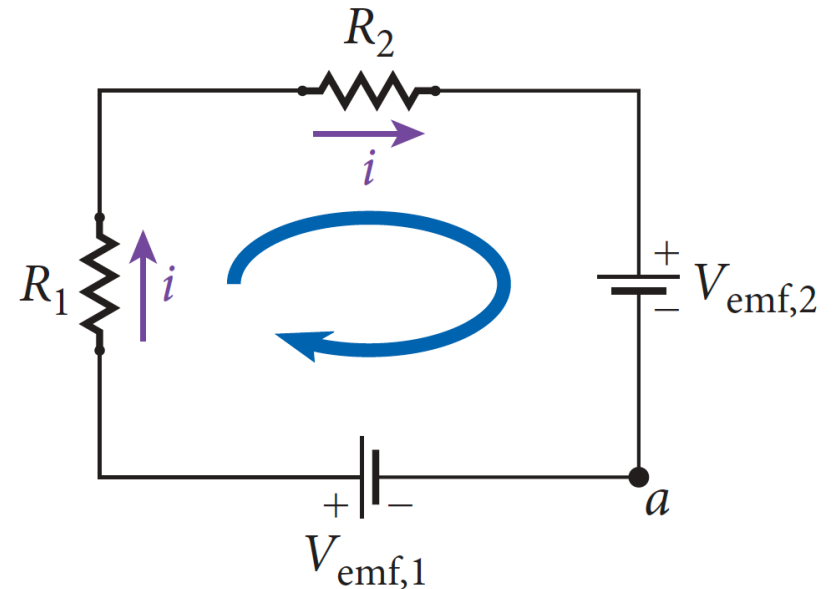- Clockwise and counterclockwise loop directions give the same information



Multi-loop Circuits




- To analyze multi-loop circuits, we must apply both Kirchhoff's Loop Rule and Kirchhoff's Junction Rule
- To analyze a multi-loop circuit
 - Identify all complete loops and all junction points in the circuit
 - Apply Kirchhoff's Rules to these parts of the circuit separately
- Analyzing the single loops and the junctions will give us a set of coupled equations in several unknown variables
- We can solve these equations to get the quantities of interest using various methods
 - Direct substitution
 - Matrices and determinants

Kirchhoff's Rules – A Radio Circuit



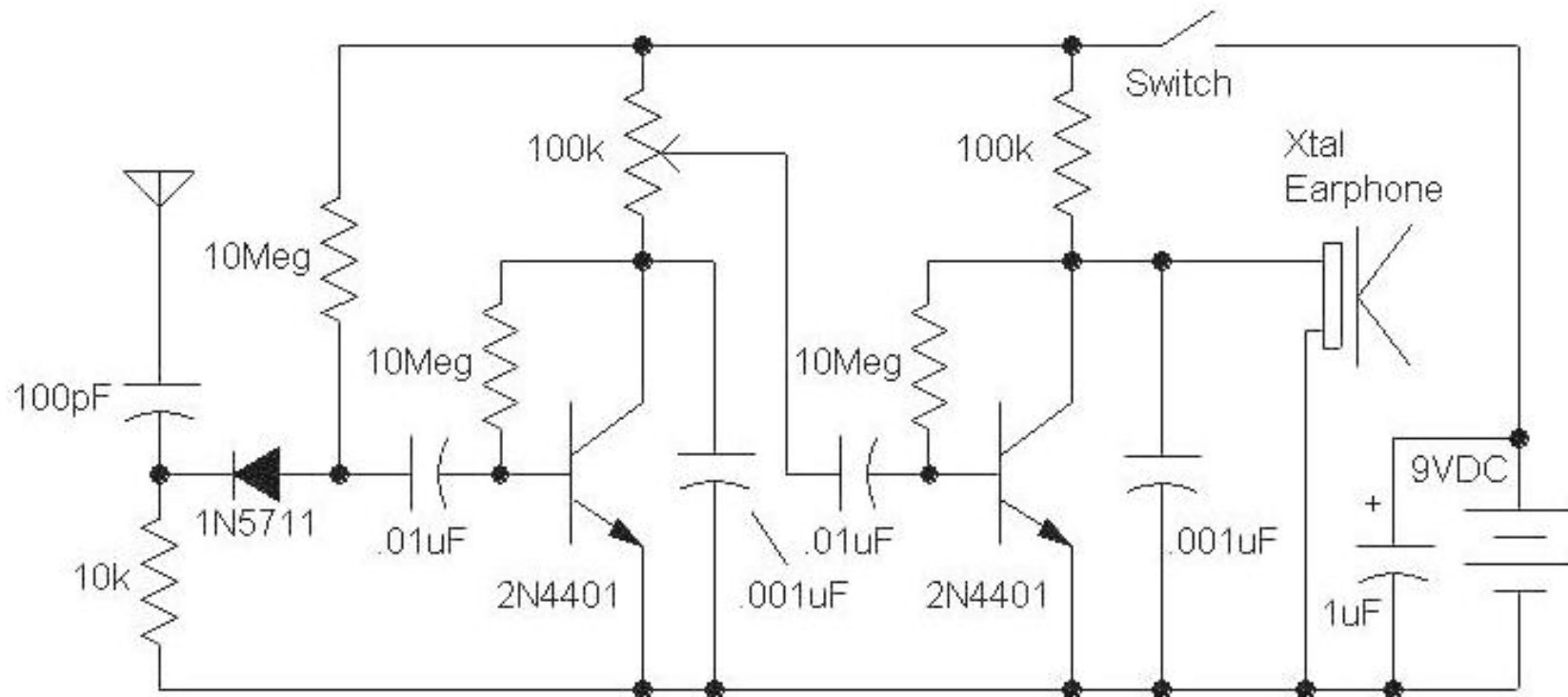- More complicated circuits can be understood by studying all loops and all junctions
- The diagram below shows one of the simplest practically useful circuit, a tunable AM radio



A Complicated Circuit With IC Chip

