




Direct Current Circuits

Kirchhoff's Junction Rule

- The sum of the currents entering a junction must equal the sum of the currents leaving the junction.


$$\text{Junction: } \sum_{k=1}^n i_k = 0$$

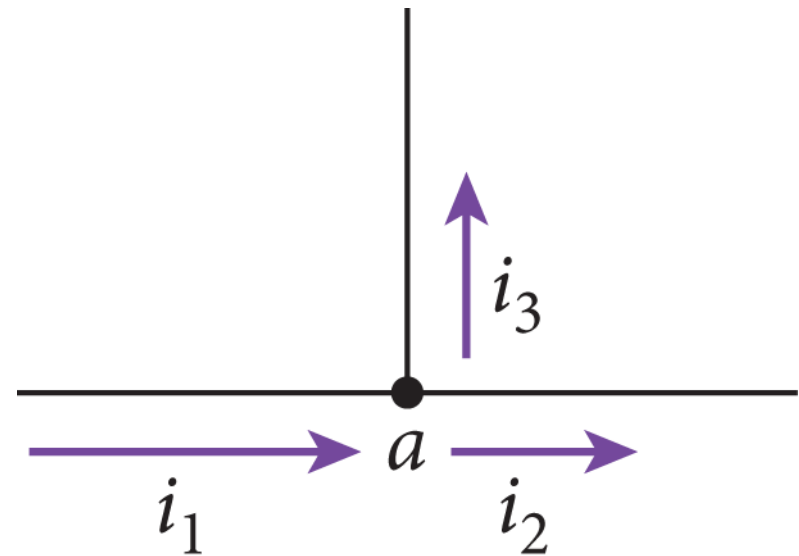- A junction is a place in a circuit where three or more wires are connected to each other
- To start, assume direction for each currents:
 - Positive result: current flows in the assumed direction
 - Negative result: current flows in the opposite direction



Kirchhoff's Loop Rule

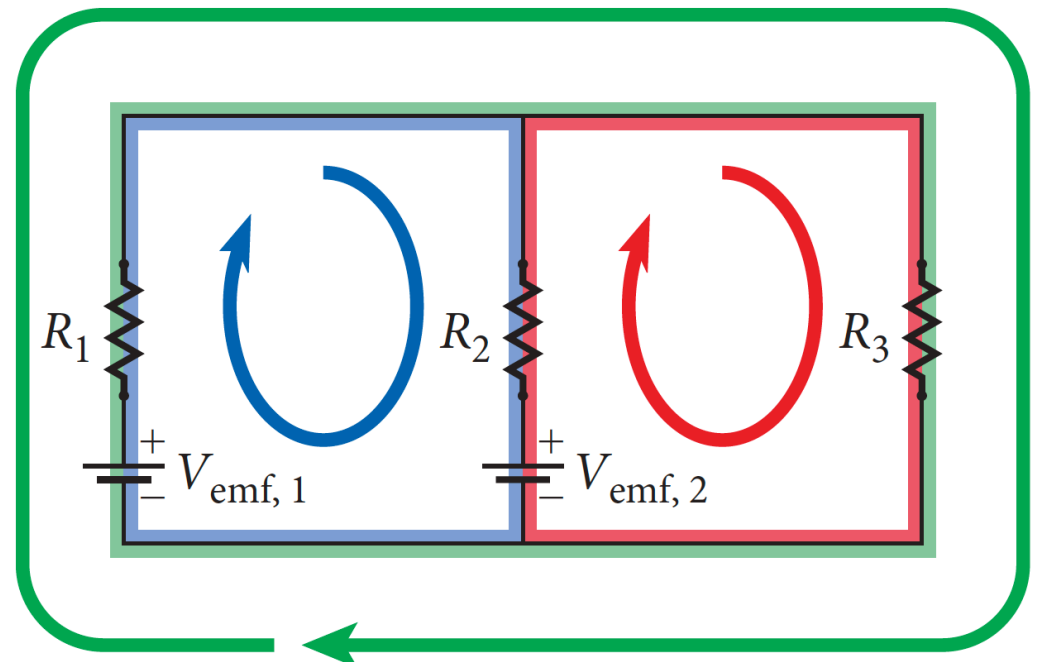- **The potential difference around a complete circuit loop must sum to zero.**
- A loop in a circuit is any set of connected wires and circuit elements forming a closed path.
- The sign for voltage sources and resistors depends on the analysis direction and the current direction




Kirchhoff's Loop Rule

- The potential difference around a complete circuit loop must sum to zero.
- A loop in a circuit is any set of connected wires and circuit elements forming a closed path.
- The sign for voltage sources and resistors depends on the analysis direction and the current direction

$$V_{emf,1} - i_1 R_1 + i_3 R_2 - V_{emf,2} = 0$$


$$V_{emf,2} - i_3 R_2 - i_2 R_3 = 0$$

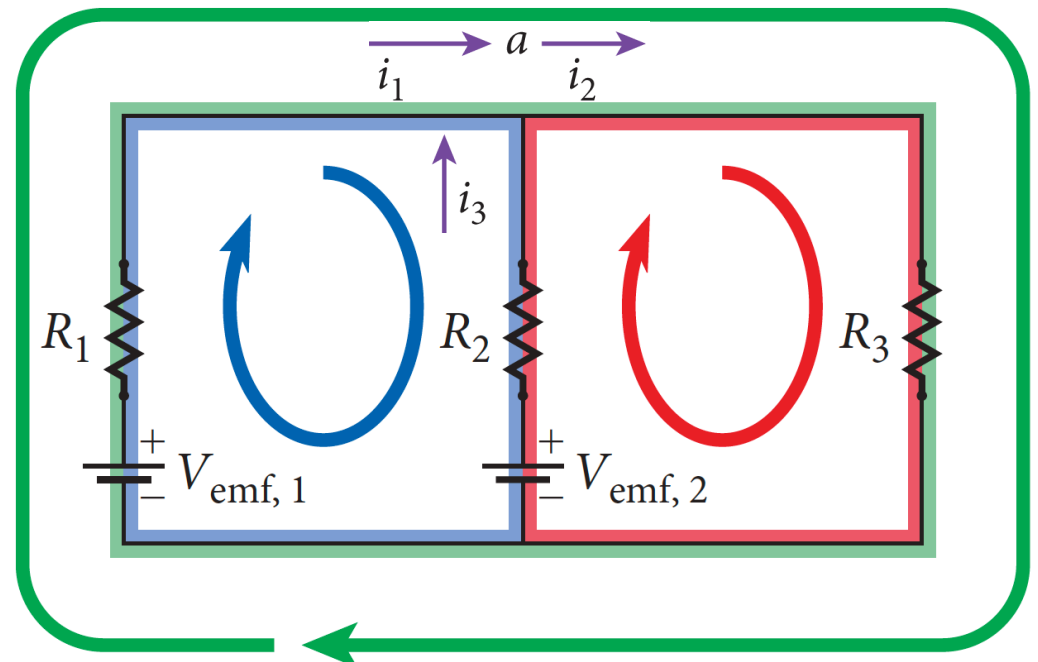

Sign Convention for Potential Changes



Element	Direction of Analysis	Potential Change	
R	Same as current	$-iR$	(a)
R	Opposite to current	$+iR$	(b)
V_{emf}	Same as emf	$+V_{emf}$	(c)
V_{emf}	Opposite to emf	$-V_{emf}$	(d)

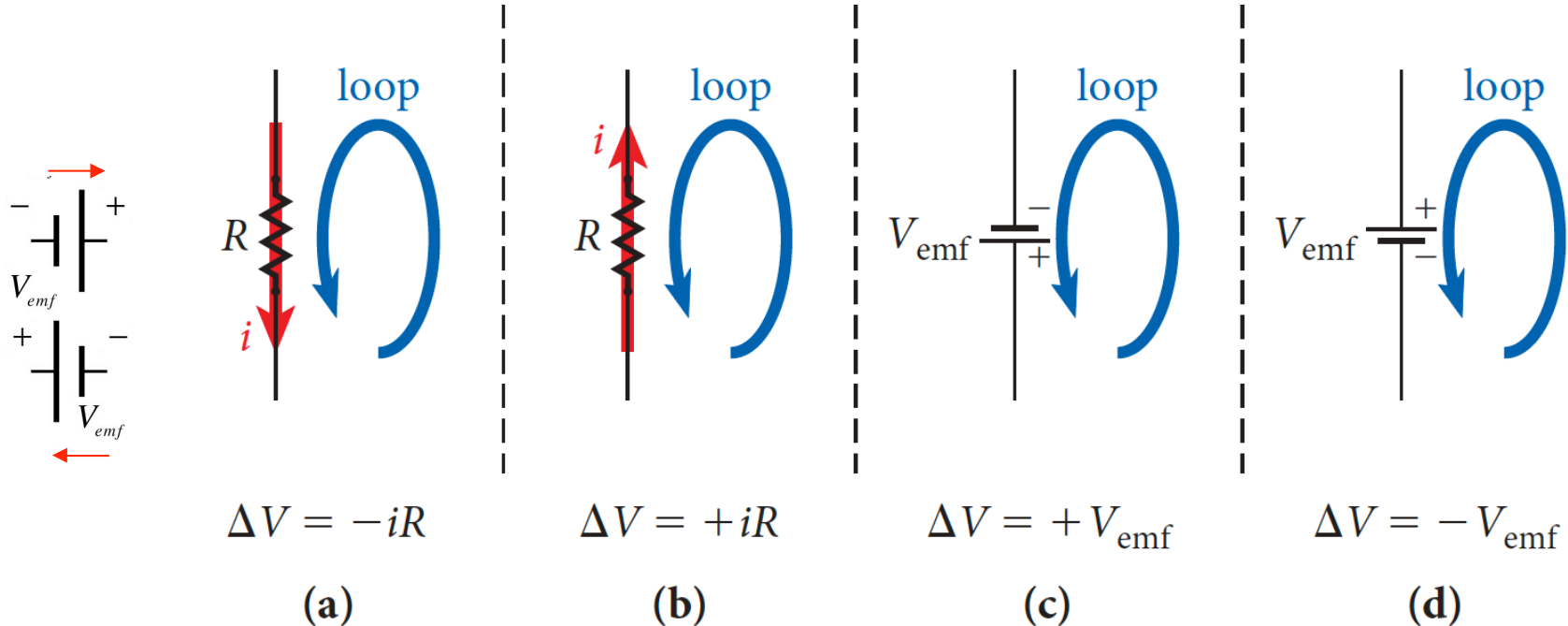

Analysis of Single-loop Circuits



- Choose a direction for the current
- We can determine if our assumption for the direction of the current is correct after the analysis is complete
- Resulting current positive
 - Current is flowing in the same direction as we had chosen
- Resulting current negative
 - Current is flowing in the direction opposite to what we had chosen
- We can choose the direction in which we analyze the circuit
 - Any direction we choose will give us the same information

Charging a Battery

- A 12.0 V battery with internal resistance $R_i = 0.200 \Omega$ is being charged by a battery charger that is capable of delivering a current of magnitude $i = 6.00 \text{ A}$

PROBLEM

- What is the minimum emf the battery charger must have to charge the battery?


SOLUTION

THINK

- The battery charger must have enough potential difference to overcome the potential difference of the battery and the potential drop across the internal resistance of the battery
- The battery charge must be connected so that its positive terminal is connected to the positive terminal of the battery

Charging a Battery

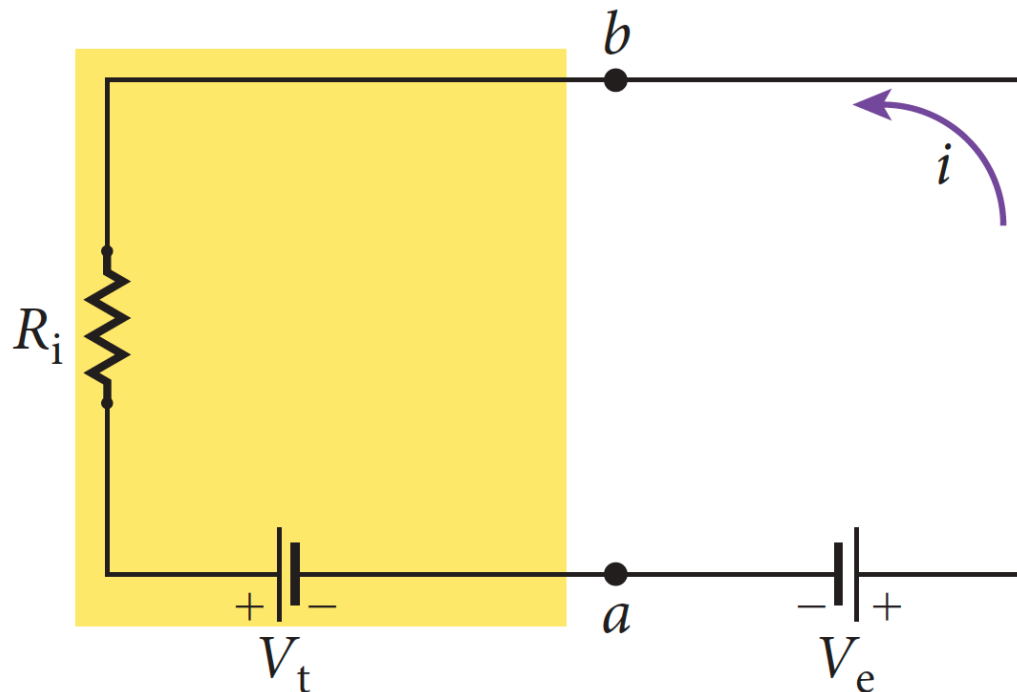- We treat the internal resistance of the battery as a resistor in a single loop circuit that contains two sources of emf with opposite polarities
- **SKETCH**



Charging a Battery

RESEARCH

- We apply Kirchhoff's Loop Rule
- We assume a current flowing in a counterclockwise direction
- The potential changes around the circuit must sum to zero
- Starting at point b we have
$$-iR_1 - V_t + V_e = 0$$

SIMPLIFY

- We solve this equation for the required potential difference of the charger
$$V_e = iR_1 + V_t$$

CALCULATE

- Putting in the numerical values

$$V_e = iR_1 + V_t = (6.00 \text{ A})(0.200 \text{ } \Omega) + 12.0 \text{ V} = 13.20 \text{ V}$$

Example – Battery Charger

- Two ideal batteries provide $V_1=12\text{V}$ and $V_2=6.0\text{V}$ and the resistors have $R_1=4.0\ \Omega$ and $R_2=8.0\ \Omega$.

(a) What is the current i ?


$$V_1 - iR_2 - iR_1 - V_2 = 0$$

$$i = \frac{12\ \text{V} - 6.0\ \text{V}}{4.0\ \Omega + 8.0\ \Omega} = 0.50\ \text{A}.$$

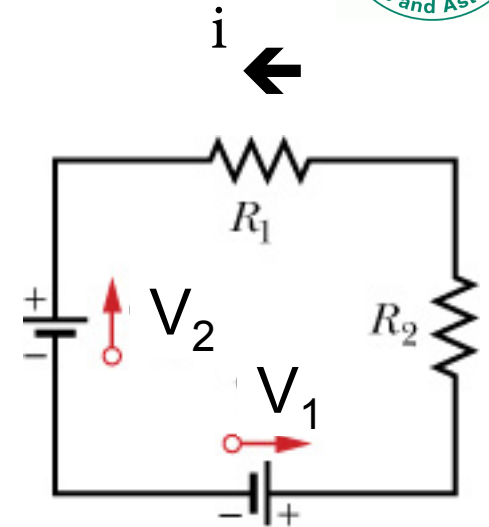(b) What is the power dissipated in R_1 and R_2 ?

$$P_1 = (0.5\ \text{A})^2 (4.0\ \Omega) = 1.0\ \text{W}$$

$$P_2 = (0.5\ \text{A})^2 (8.0\ \Omega) = 2.0\ \text{W}$$




Example – Battery Charger

- Two ideal batteries provide $V_1=12\text{V}$ and $V_2=6.0\text{V}$ and the resistors have $R_1=4.0\ \Omega$ and $R_2=8.0\ \Omega$.

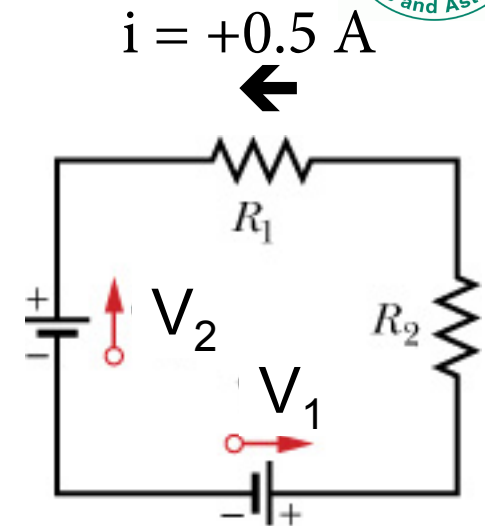(c) Is energy being supplied or absorbed by battery 1 and battery 2?


For battery 1, the emf arrow points in the same direction as the current: The battery supplies energy to the circuit.

For battery 2, the emf arrow points opposite to the current direction: The battery absorbs energy from the circuit, it is being charged!



Multi-loop Circuit

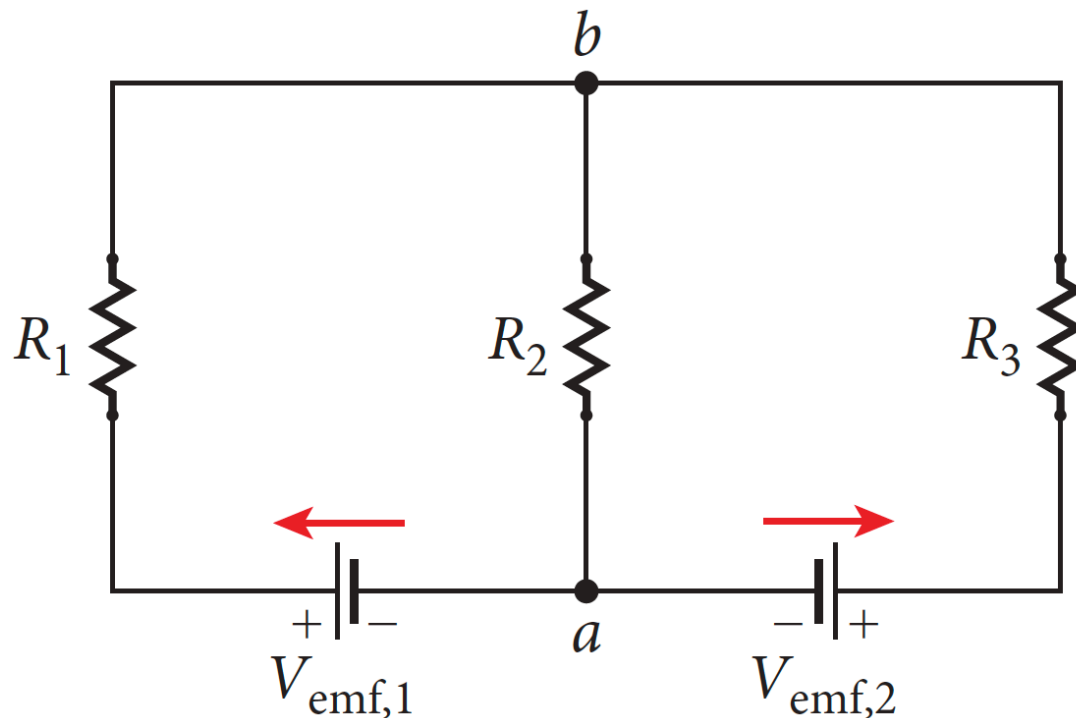
- Consider a circuit that has three resistors, R_1 , R_2 , and R_3 and two sources of emf, $V_{\text{emf},1}$ and $V_{\text{emf},2}$



- This circuit cannot be resolved into simple series or parallel structures

Multi-loop Circuit

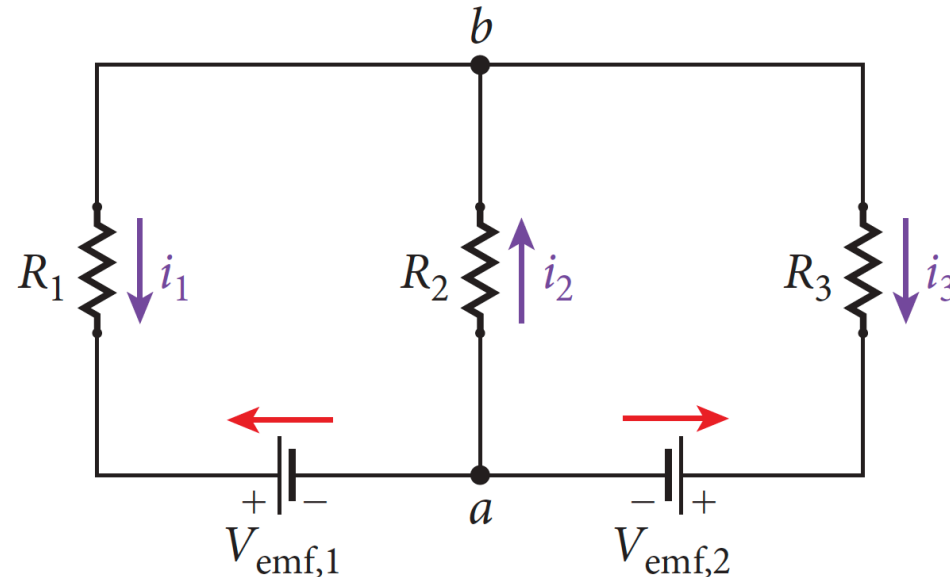- To analyze this circuit, we need to assign currents flowing through the resistors
- We can choose the directions of these currents arbitrarily




- Junction b gives us

$$i_2 = i_1 + i_3$$
- Junction a gives us

$$i_1 + i_3 = i_2$$
- Which gives us no new information

Multi-loop Circuit

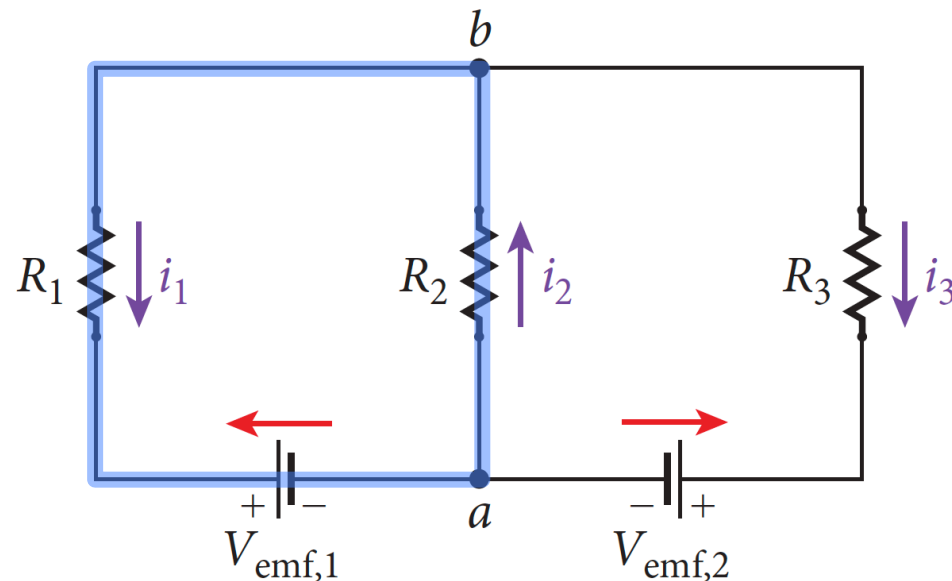
- At this point we have one equation and three unknowns from Kirchhoff's Junction Rule
- To get the necessary two additional equations we apply Kirchhoff's Loop Rule
- Start with left half of circuit analyzing the loop in a counterclockwise direction starting at b



$$-i_1 R_1 - V_{\text{emf},1} - i_2 R_2 = 0 \Rightarrow i_1 R_1 + V_{\text{emf},1} + i_2 R_2 = 0$$

Multi-loop Circuit

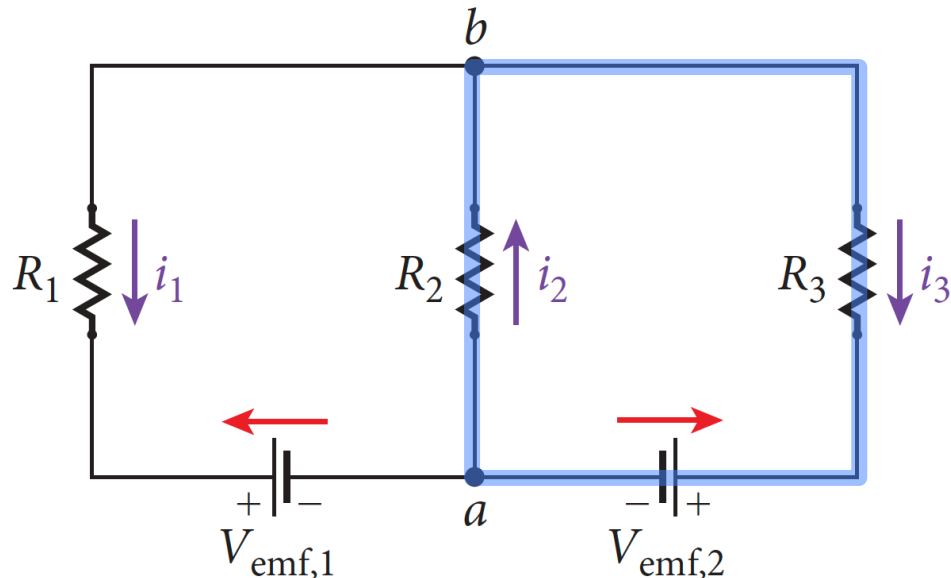- Now analyze the right half of the circuit in a clockwise direction starting at b



$$-i_3 R_3 - V_{\text{emf},2} - i_2 R_2 = 0 \Rightarrow i_3 R_3 + V_{\text{emf},2} + i_2 R_2 = 0$$

- We can analyze the outer loop also, but we will not gain any additional information

Multi-loop Circuit

- Our three unknowns are i_1 , i_2 , and i_3 and our three equations are

$$\left. \begin{aligned} i_2 &= i_1 + i_3 \\ i_1 R_1 + V_{\text{emf},1} + i_2 R_2 &= 0 \\ i_3 R_3 + V_{\text{emf},2} + i_2 R_2 &= 0 \end{aligned} \right\} \Rightarrow \begin{cases} i_1 - i_2 + i_3 = 0 \\ i_1 R_1 + i_2 R_2 = -V_{\text{emf},1} \\ i_2 R_2 + i_3 R_3 = -V_{\text{emf},2} \end{cases} \quad \begin{pmatrix} 1 & -1 & 1 \\ R_1 & R_2 & 0 \\ 0 & R_2 & R_3 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 0 \\ -V_{\text{emf},1} \\ -V_{\text{emf},2} \end{pmatrix}$$

- Use Cramer's Rule to get i_1

$$i_1 = \frac{\begin{vmatrix} 0 & -1 & 1 \\ -V_{\text{emf},1} & R_2 & 0 \\ -V_{\text{emf},2} & R_2 & R_3 \end{vmatrix}}{\begin{vmatrix} 1 & -1 & 1 \\ R_1 & R_2 & 0 \\ 0 & R_2 & R_3 \end{vmatrix}} = \frac{-R_2 V_{\text{emf},1} + R_2 V_{\text{emf},2} - R_3 V_{\text{emf},1}}{R_2 R_3 + R_1 R_2 + R_1 R_3} = -\frac{(R_2 + R_3) V_{\text{emf},1} - R_2 V_{\text{emf},2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

- Can do the same for i_2 and i_3 (in the book)

Math Reminder: Cramer's Rule



$$\begin{cases} ax + by + cz = j \\ dx + ey + fz = k \\ gx + hy + iz = l \end{cases} \quad x = \frac{\begin{vmatrix} j & b & c \\ k & e & f \\ l & h & i \end{vmatrix}}{\begin{vmatrix} a & b & c \\ d & e & f \\ g & h & i \end{vmatrix}}, \quad y = \frac{\begin{vmatrix} a & j & c \\ d & k & f \\ g & l & i \end{vmatrix}}{\begin{vmatrix} a & b & c \\ d & e & f \\ g & h & i \end{vmatrix}}, \quad \text{and } z = \frac{\begin{vmatrix} a & b & j \\ d & e & k \\ g & h & l \end{vmatrix}}{\begin{vmatrix} a & b & c \\ d & e & f \\ g & h & i \end{vmatrix}}.$$

$$\det(A) = \begin{vmatrix} a & b & c \\ d & e & f \\ g & h & i \end{vmatrix}$$

$$= a(ei - hf) - d(bi - hc) + g(bf - ec)$$

Ammeters and Voltmeters

- A device used to measure current is called an **ammeter**
- A device used to measure potential difference is called a **voltmeter**
- To measure the current, the ammeter must be placed in the circuit in *series*
- To measure the potential difference, the voltmeter must be wired in *parallel* with the component across which the potential difference is to be measured

