Given two 4-1 multiplexers and a single 2-1 multiplexer, build an 8-1 multiplexer without using any other components.