In the circuit below, two NAND gates are used to debounce a single-pole double-throw (SPDT) switch. Explain the operation of the circuit.